

# Sequential Circuits


Networks and Embedded Software

Module 3.3.2

by Wolfgang Neff

 
# Combinational Circuits

- Output depends on current input, only
  - System has no memory
  - History is of no importance



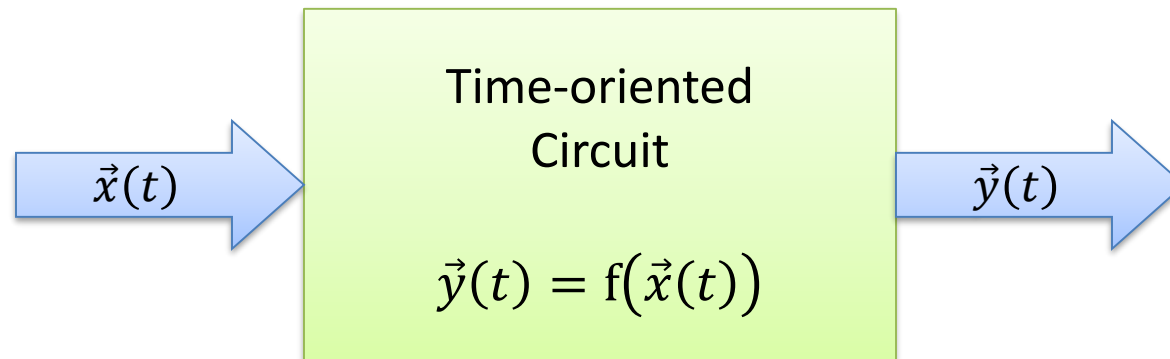
# Sequential Circuits (1)

- Output depends on previous inputs
  - System has a memory
  - History is important



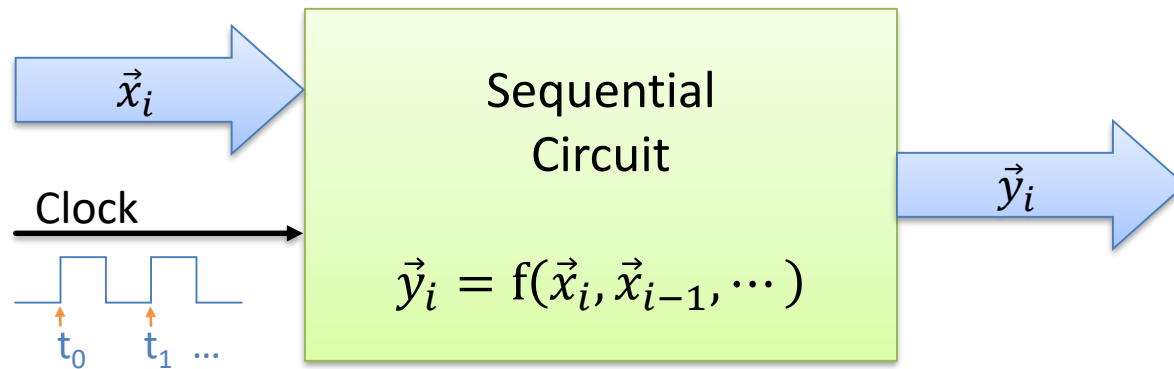
# Sequential Circuits (2)

- Time is provided by a clock
  - Time gets discretized
  - Input becomes a sequence of data



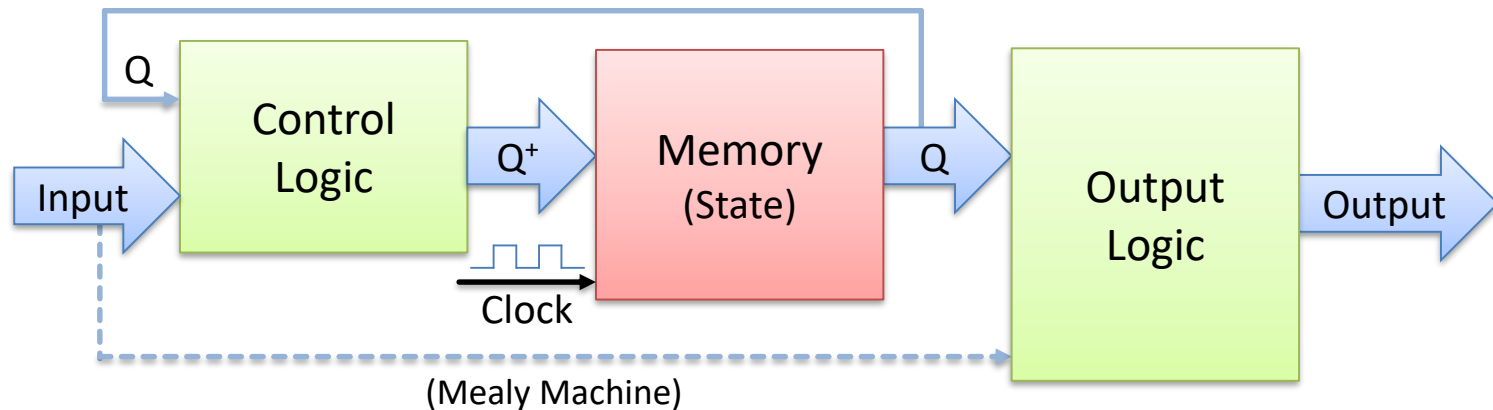
# Sequential Circuits (3)

- Two representations are frequently used
  - Mealy Machine (dashed arrow allowed)
  - Moore Machine (dashed arrow not allowed)


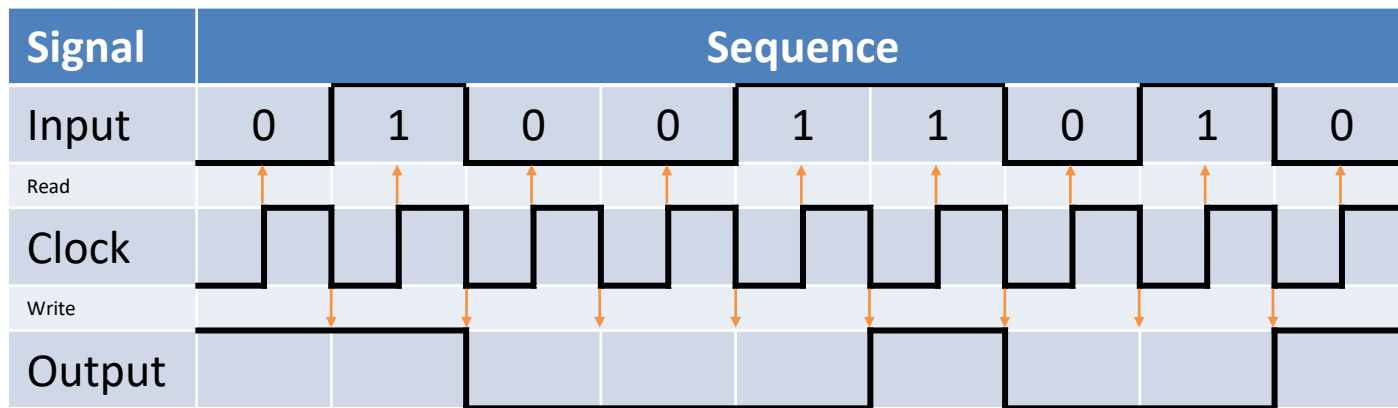
# Sequential Circuits (4)

- Timing
  - Control logic reads input on rising edge
  - Output logic writes output on falling edge



Pulse Diagram


# Sequential Circuits (5)

- States are handled by state machines (FSM)
- FSM are represented by state diagrams
- Finite state machines have

– States

– Transitions


– Conditions

 

State Diagram of a Switch

# Sequential Circuits (6)

- D flip-flops store the state

 

D	Q <sup>+</sup>
0	0
1	1

- *1D*: Synchronous data line controlled by clock 1
- *C1*: First clock signal for the circuit
- *R*: Asynchronous reset line
- *Q*: Stored data



# Sequential Circuits (7)

- Design process
  - Create state diagram
    - Number of states
    - Transitions and conditions
  - Encode states
    - One D flip-flops per bit
  - Design control logic
    - State/transition table
  - Design output logic


# Sequential Circuits (8)

- Example I

- Assignment

Design a sequential circuit which outputs 1 if an even number of 1 was read.

- State diagram

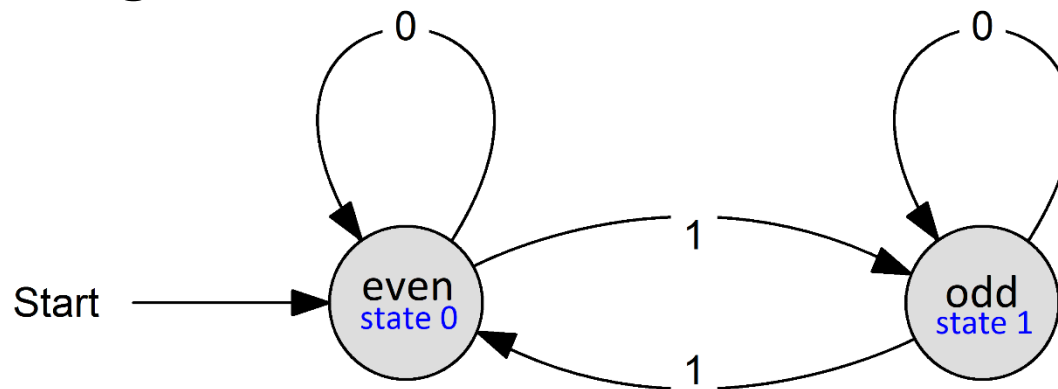

# Sequential Circuits (9)

- Example I (continued)
  - Number of states
    - Even, odd  $\rightarrow$  2 states  $\rightarrow$  1 bit  $\rightarrow$  1 D flip-flop
  - State table (transitions and conditions)

Q	a	Q <sup>+</sup>
Even (0)	0	Even (0)
Even (0)	1	Odd (1)
Odd (1)	0	Odd (1)
Odd (1)	1	Even (0)

$a$  Input  
 $Q$  Current State  
 $Q^+$  Next State

# Sequential Circuits (10)

- Example I (continued)


- Encoding of states

- Even bit count: 0, 2, 4, 6, ...
    - Odd bit count: 1, 3, 5, 7, ...

State	Encoding
Even	0
Odd	1

- Output logic


Q	y
0	1
1	0

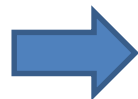  $y(Q) = \neg Q$

# Sequential Circuits (11)

- Example I (continued)
  - Control logic


Q	a	Q <sup>+</sup>
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q^+ = Q \oplus a$$


# Sequential Circuits (12)

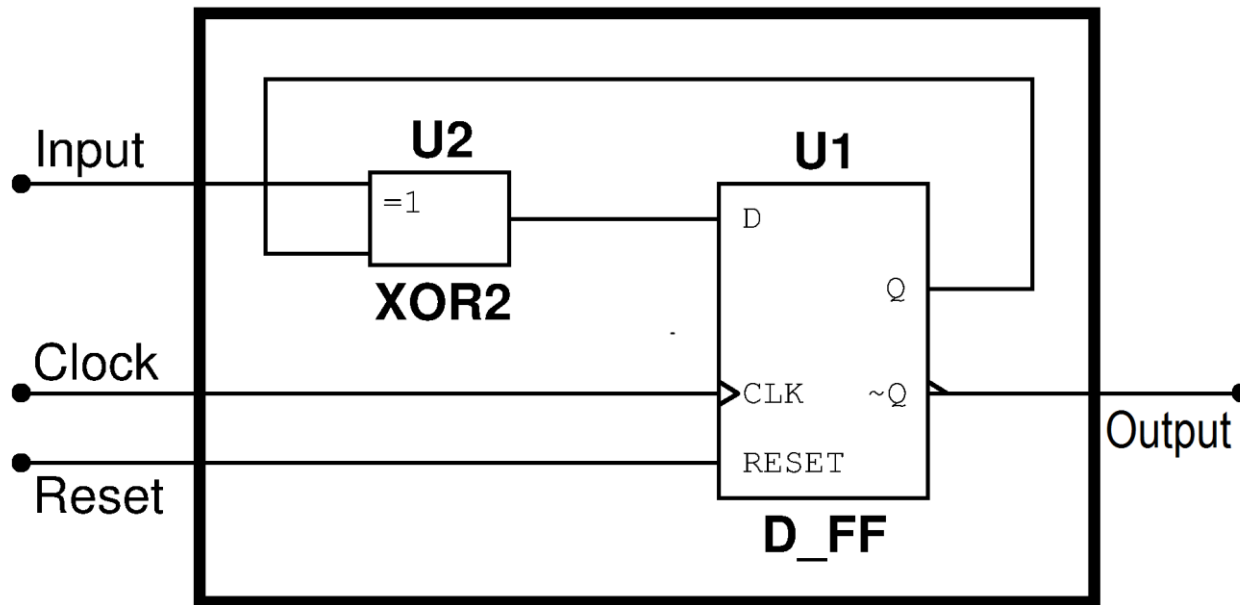- Example I (finished)
  - The resulting sequential circuit



# Sequential Circuits (13)

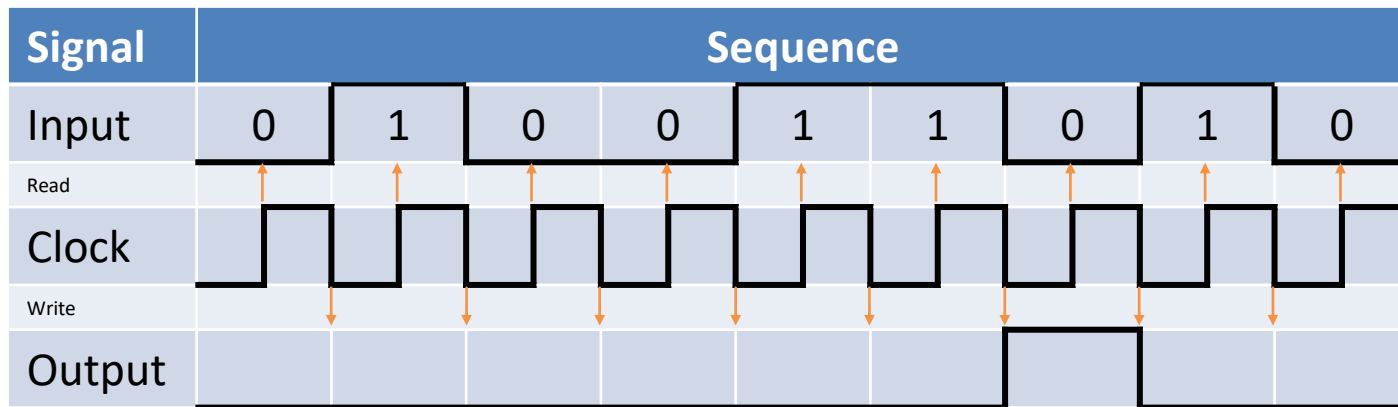
- Example II
    - Assignment
- Find two subsequent *1* in a bit sequence



Pulse Diagram

# Sequential Circuits (14)

 - Example II (continued)
  - Number of states
    - None, one, two ones  $\rightarrow$  3 states  $\rightarrow$  2 bits
  - State diagram





# Sequential Circuits (15)

- Example II (continued)
  - Control logic

$Q_1$	$Q_0$	$a$	$Q_1^+$	$Q_0^+$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	0	X	X
1	1	1	X	X



State	Encoding
None	$0 \rightarrow 00$
One	$1 \rightarrow 01$
Two	$2 \rightarrow 10$

$$Q_0^+ = a \wedge \neg Q_0 \wedge \neg Q_1$$
$$Q_1^+ = (a \wedge Q_1) \vee (a \wedge Q_0)$$

# Sequential Circuits (16)

- Example II (finished)

– Output logic

$Q_1$	$Q_0$	$y$
0	0	0
0	1	0
1	0	1
1	1	X

$$y = Q_1$$

