

Bit Streams


Networks and Embedded Software

Module 3.3.3 (optional)

by Wolfgang Neff


Serial / Parallel (1)

 - Bits can come parallel or serially
 - Parallel: all at a time
 - Serial: one after another



Serial / Parallel (2)

 - Serial-to-parallel converter
 - Converts serial signals to parallel signals
 - A parallel-to-serial converter does it in reverse




Serial / Parallel (3)

- Serial-to-parallel converter


- Implementation

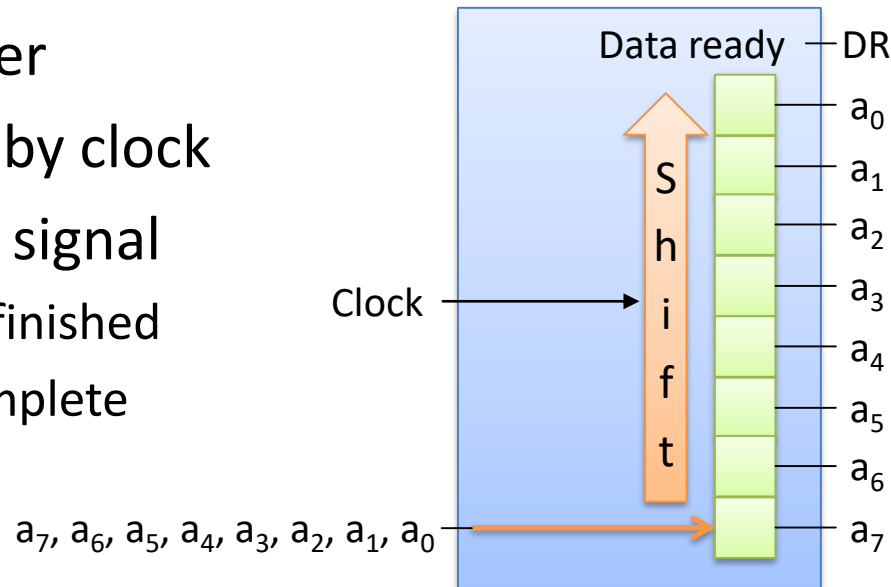- Shift register
- Controlled by clock
- Data ready signal
 - Shifting finished
 - Data complete



Serial / Parallel (4)

 - Serial bits are a sequence of pulses
 - Example: 10011



Serial / Parallel (5)

- Characteristics

- Period T : duration of one pulse

- Frequency f : number of pulses per second


- Example

- 50 kbps

- Bits per second


- $f = 50 \text{ kHz}$

- $T = 20 \mu\text{s}$

 


Serial / Parallel (6)

 - Square pulses are an ideal conception
 - High frequencies are cut off
 - Square pulses become fuzzy



SR Latch (1)

 
- Used to store information
 - Stores one bit
 - Control lines
 - S: Set bit
 - R: Reset bit
 - Stored information
 - Q: State



S	R	Q ⁺	Action
0	0	Q	Store
0	1	0	Reset
1	0	1	Set
1	1	X	Invalid

SR Latch (2)

 - Time diagram of an asynchronous SR latch
 - Clock signal is of no importance




Triggers (1)

- Control when data are read
 - Active state: input data is read
 - Passive state: input data is ignored
 - Level triggers
 - Active state depends on the level
 - Level 0 or 1 is active
 - Edge triggers
 - Active state depends on the level change
 - Edge 0→1 or edge 1→0 is active


Triggers (2)

- Graphical symbols

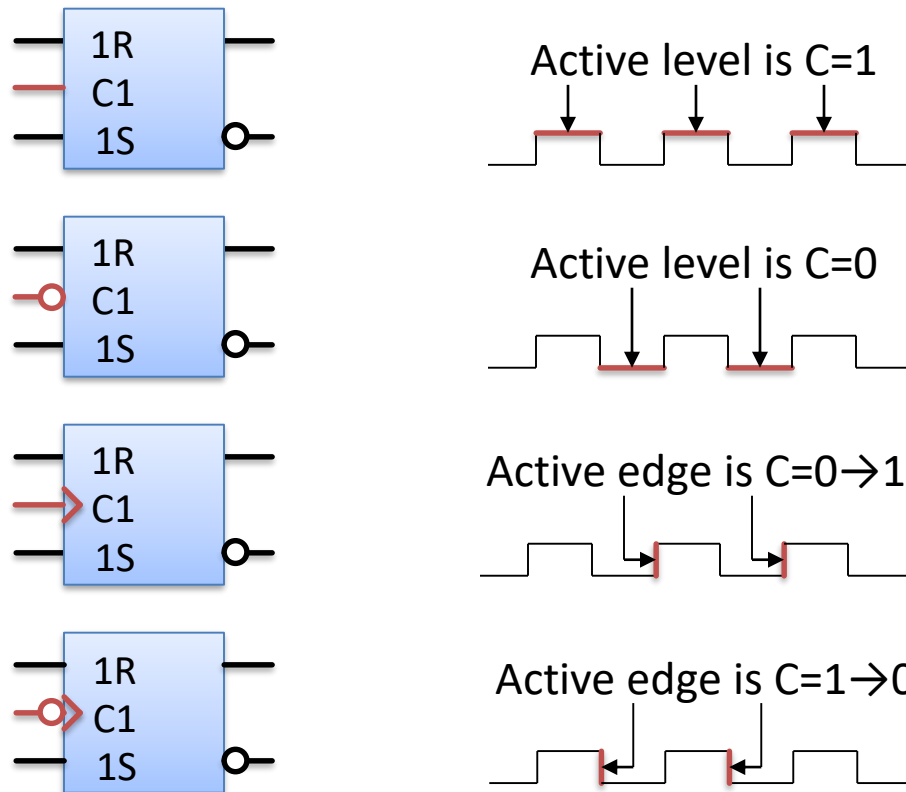


Triggers (3)

 - Time diagram of a synchronous SR latch
 - Active state: level 1




Triggers (4)

 - Time diagram of a synchronous SR latch
 - Active state: level 0



Triggers (5)

 - Time diagram of a synchronous SR latch
 - Active state: edge $0 \rightarrow 1$



Triggers (6)

- Time diagram of a synchronous SR latch
 - Active state: edge 1→0

