

Voltage Divider


Applied Mechatronics

First Grade Level

Wolfgang Neff

Voltage Divider (1)

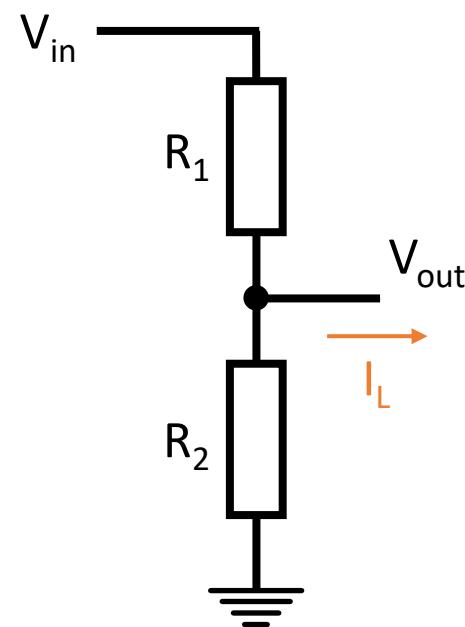- Mode of Operation
 - Reduce voltage with the aid of resistors
 - Two resistors in series
 - Two modes
 - Unloaded voltage divider
 - No current load on V_{out}
 - Loaded voltage divider
 - With current load on V_{out}



Voltage Divider (2)

- Unloaded voltage divider

- Given values

- R_1, R_2, V_{in}

- Required values

- V_{out}, I_V, P_{tot}

- Relations


- $R_{tot} = R_1 + R_2$

- $V_{in} = V_1 + V_2$

- $V_{out} = V_2$

- $I_V = \frac{V_{in}}{R_{tot}} = \frac{V_1}{R_1} = \frac{V_2}{R_2}$

- $P_{tot} = V_{in} \cdot I_V$

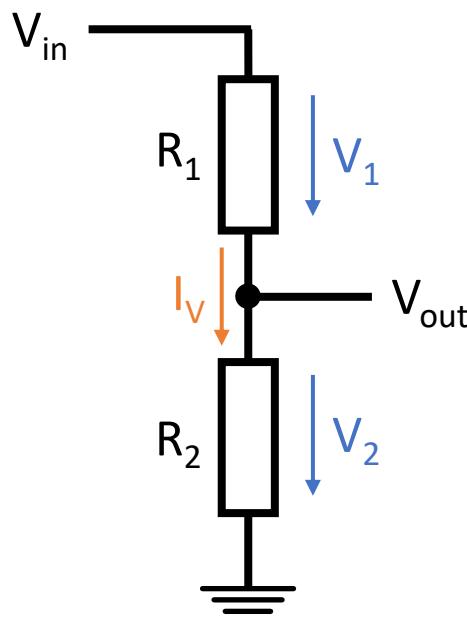

V_{in} : Input Voltage

V_{out} : Output Voltage

I_V : Vertical Current

R_{tot} : Total Resistance

P_{tot} : Total Power =
Power Loss

Voltage Divider (3)

- Unloaded voltage divider

- Derivation

- $\bullet \frac{V_{in}}{R_{tot}} = \frac{V_2}{R_2}$


- $\bullet V_2 = \frac{R_2}{R_{tot}} \cdot V_{in}$

- Formulas

- $\bullet V_{out} = \frac{R_2}{R_1+R_2} \cdot V_{in}$

- $\bullet I_V = \frac{V_{out}}{R_2}$

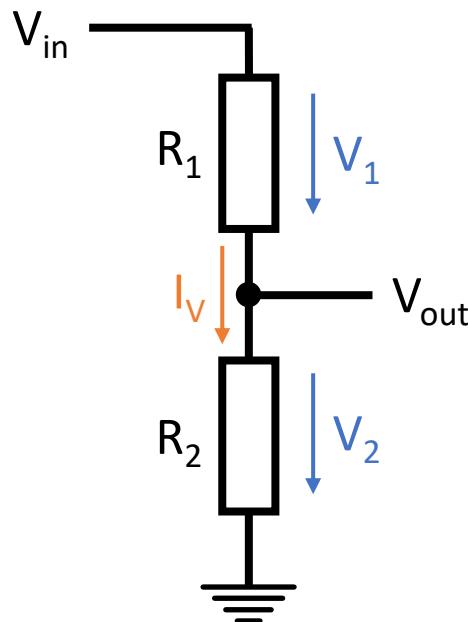- $\bullet P_{tot} = \frac{V_{out}}{R_2} \cdot V_{in}$



$$I_V = \frac{V_{in}}{R_{tot}}$$

$$I_V = \frac{V_2}{R_2}$$

Voltage Divider (4)

- Unloaded voltage divider


- Example

- Given values

- $V_{in} = 5 \text{ V}$
 - $R_1 = 100 \Omega$
 - $R_2 = 120 \Omega$

- Calculation

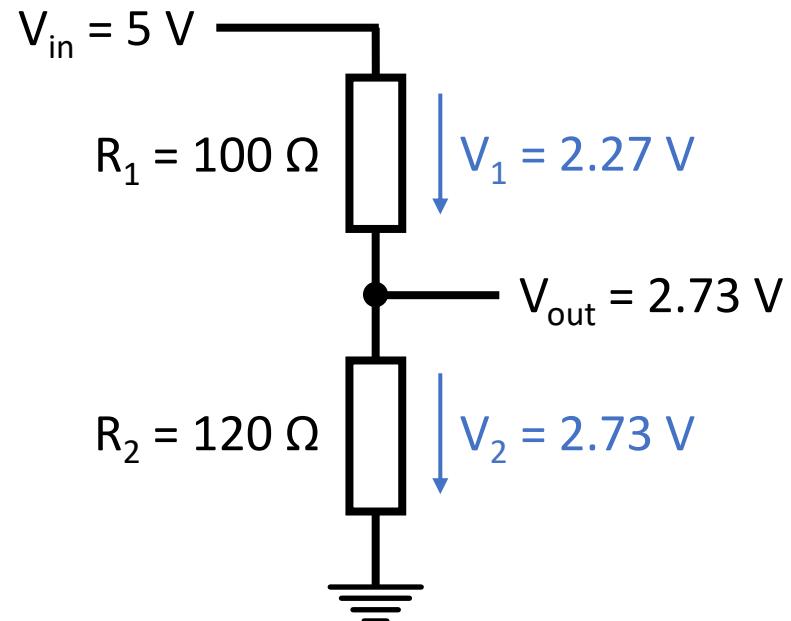- $$V_{out} = \frac{R_2}{R_1+R_2} \cdot V_{in}$$
$$= \frac{120 \Omega}{100 \Omega+120 \Omega} \cdot 5 \text{ V}$$
$$= 2.73 \text{ V}$$




Voltage Divider (5)

- Unloaded voltage divider

- Calculation

- $$\begin{aligned} I_V &= \frac{V_{out}}{R_2} \\ &= \frac{2.73 \text{ V}}{120 \Omega} \\ &= 23 \text{ mA} \end{aligned}$$

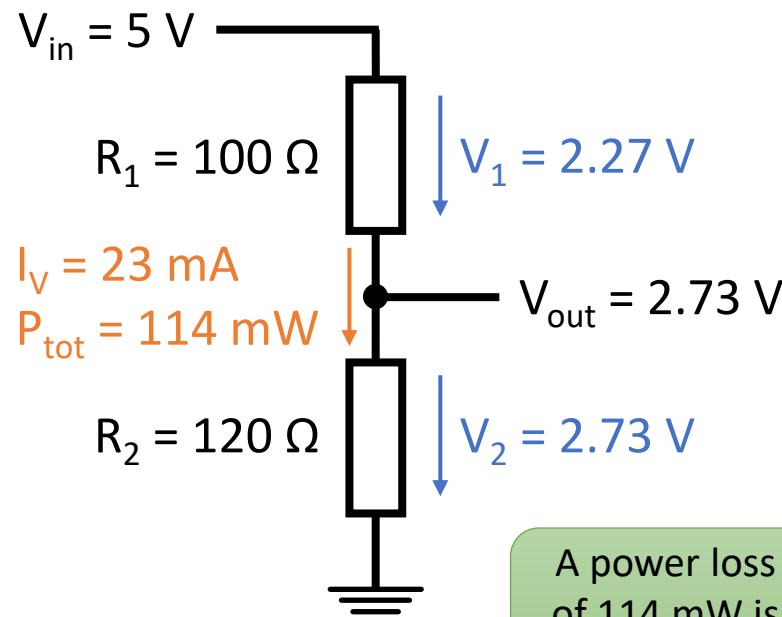- $$\begin{aligned} P_{tot} &= \frac{V_{out}}{R_2} \cdot V_{in} \\ &= \frac{2.73 \text{ V}}{120 \Omega} \cdot 5 \text{ V} \\ &= 114 \text{ mW} \end{aligned}$$



Voltage Divider (6)

- Voltage Divider with Amplifier
 - Loaded voltage divider are difficult to handle
 - Current load may be unknown
 - Current load may vary
 - An amplifier can eliminate the load

