

# Digital Circuits



Networks and Embedded Systems

First Grade Level

Wolfgang Neff
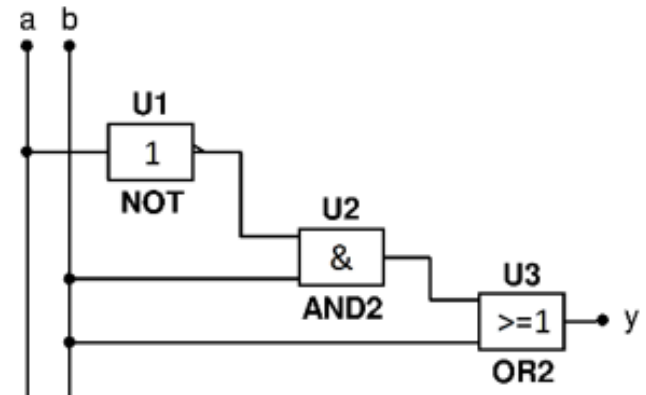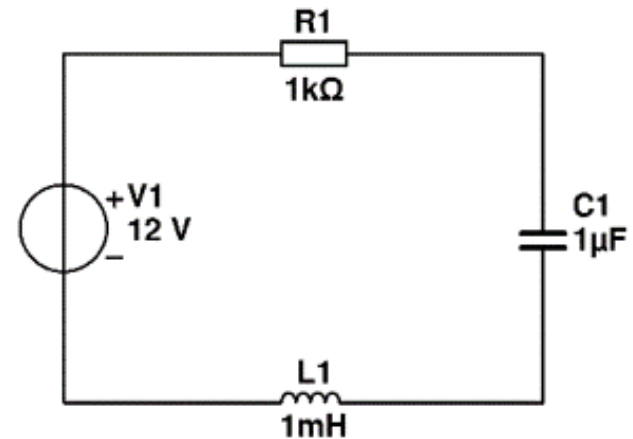
# Digital Circuits (1)

- Analog and Digital
  - Analog Circuits
    - Any voltage level allowed
  - Digital Circuits
    - Two voltage levels allowed
      - + and –
      - 1 and 0
      - H and L




# Digital Circuits (2)

- Basic Concept
  - Based on Boolean algebra
    - 0 → Low voltage
    - 1 → High voltage
    - Operator → Symbol
    - Function → Circuit
  - Terms
    - Logical functions → Switching function
    - Truth table → Switching table
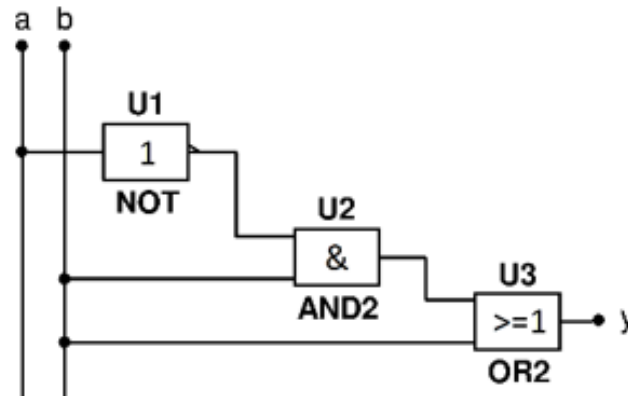
# Digital Circuits (3)


- Basic Concept (continued)
  - Truth function ...
    - $\varphi(a,b) = (\neg a \wedge b) \vee b$
  - ... represented graphically




# Digital Circuits (4)

- Graphic Symbols

- Buffer

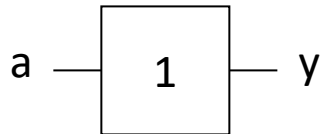


European Style  
(IEC 60617-12)

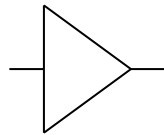

American Style  
(IEEE 315-1975)

a	y=a
0	0
1	1

- Negation (NOT,  $\neg$ )

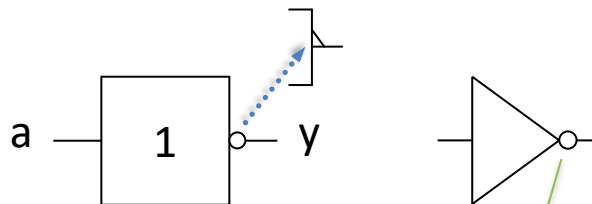


Inversion Circle

a	y= $\neg$ a
0	1
1	0

# Digital Circuits (5)


- Graphic Symbols (continued)

- Disjunction (OR,  $\vee$ )

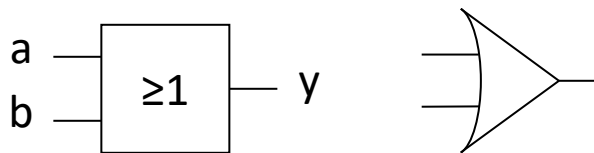

a	b	$y=a\vee b$
0	0	0
0	1	1
1	0	1
1	1	1

- Conjunction (AND,  $\wedge$ )


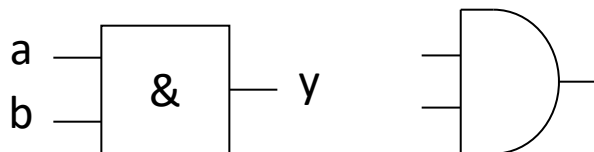


a	b	$y=a\wedge b$
0	0	0
0	1	0
1	0	0
1	1	1

# Digital Circuits (6)



- Graphic Symbols (continued)

- NOR ( $\downarrow$ )

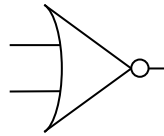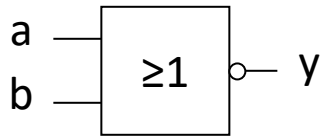

a	b	$y=a\downarrow b$
0	0	1
0	1	0
1	0	0
1	1	0

- NAND ( $\uparrow$ )

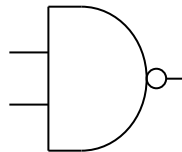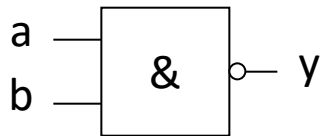


a	b	$y=a b$
0	0	1
0	1	1
1	0	1
1	1	0

# Digital Circuits (7)

- Graphic Symbols (finished)

  - XOR ( $\oplus$ )

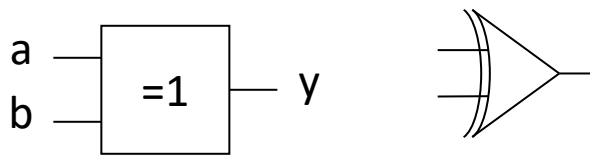


a	b	$y=a\oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

- Compound Gates

  - AND-Gate

- $y = a_0 \wedge a_1 \wedge a_2 \dots$

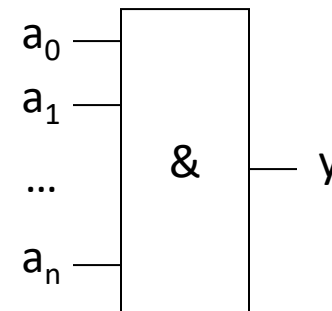- $(a_0, a_1, \dots) \mapsto \begin{cases} 1 & \text{if each } a_i = 1 \\ 0 & \text{else} \end{cases}$






# Digital Circuits (8)

- Compound Gates (continued)

- OR-Gate

- $y = a_0 \vee a_1 \vee a_2 \dots$

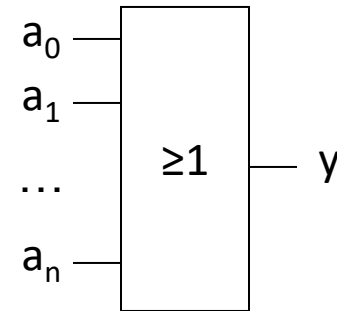
- $(a_0, a_1, \dots) \mapsto \begin{cases} 0 & \text{if each } a_i = 0 \\ 1 & \text{else} \end{cases}$



- Composition

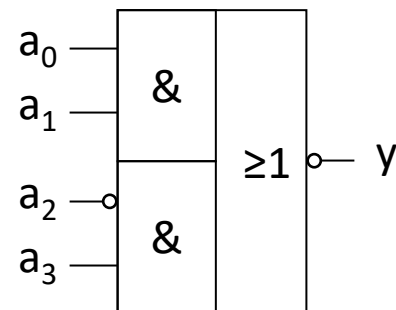- Example



- $\neg((a_0 \wedge a_1) \vee (\neg a_2 \wedge a_3))$



# Digital Circuits (9)

- Building Blocks



$$- y = \neg a \wedge b$$

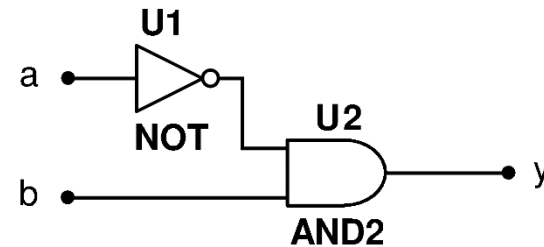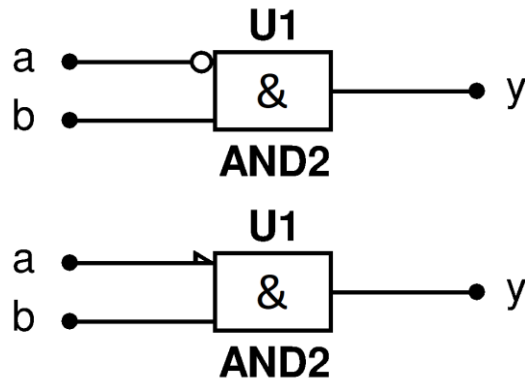

# Digital Circuits (10)

- Building Blocks (continued)



$$- y = \neg(a \wedge b)$$

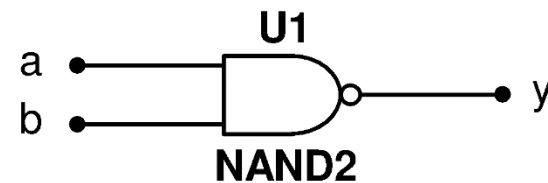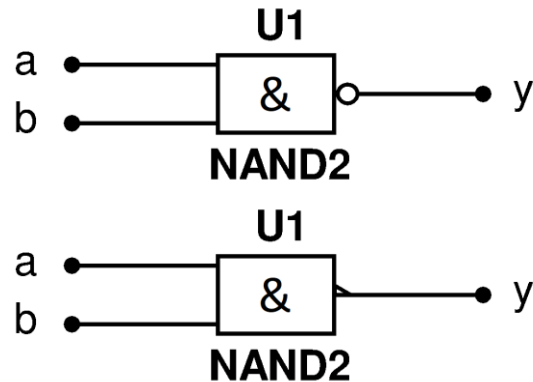

# Digital Circuits (11)



- Building Blocks (continued)

–  $y = (a \wedge b) \vee c$

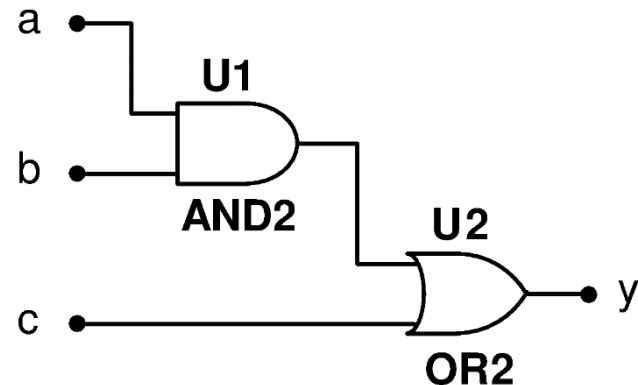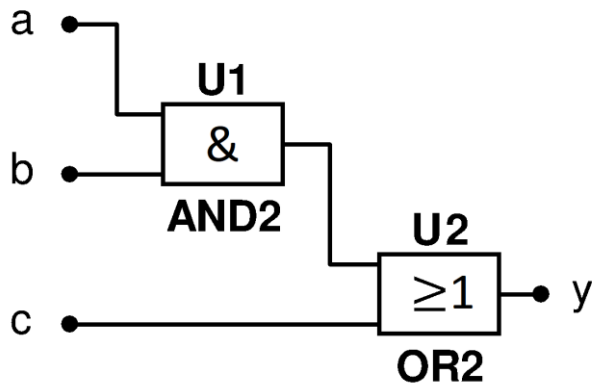
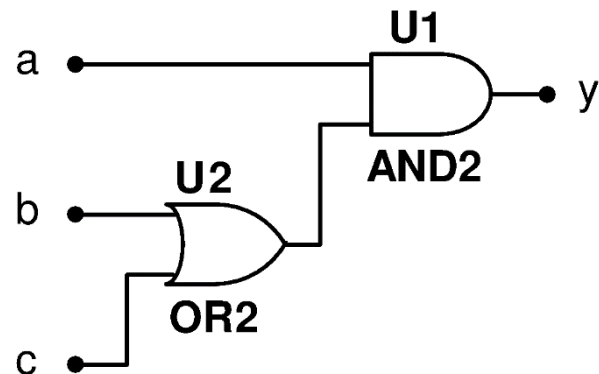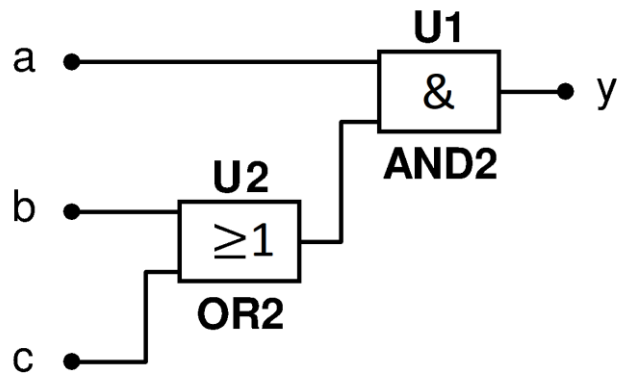
# Digital Circuits (12)

- Building Blocks (finished)
  - $y = a \wedge (b \vee c)$



# Digital Circuits (13)

- Example

$$y = (a \wedge \neg b) \vee \neg(c \wedge a) \vee c$$

