

# Combinatorial Circuits

Mechanical and Electrical Engineering

Second Grade Level

by Wolfgang Neff

# Combinatorial Circuits (1)

- Design of Combinatorial Circuits

- Problem: Please add two bits

- Hints

- If you add two numbers a carry can occur
      - You need not only determine the result but also the carry
      - On the other hand there can already be a carry when you add two numbers
      - You have to handle this carry, too
      - This type of circuit is called full adder

- Mathematical description of a full adder

- $\{0,1\} \times \{0,1\} \times \{0,1\} \mapsto \{0,1\} \times \{0,1\}$   
 $(a,b,c_i) \rightarrow (c_o,r)$

- $c_i$ : carry in;  $c_o$ : carry out;  $r$ : LSB of  $a+b$  (left most bit)

Or for short:  
 $\{0,1\}^3 \mapsto \{0,1\}^2$

# Combinatorial Circuits (2)

- Design of Combinatorial Circuits (continued)
  - Example of a Binary Addition

Bit position	3	2	1	0
1st Number (7)	0	1	1	1
2nd Number (5)	0	1	0	1
Carry	1	1	1	0
Result (12)	1	1	0	0


# Combinatorial Circuits (3)

- Design of Combinatorial Circuits (continued)
  - Truth table of a one bit full adder


a	b	$c_i$	$c_o$	y
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
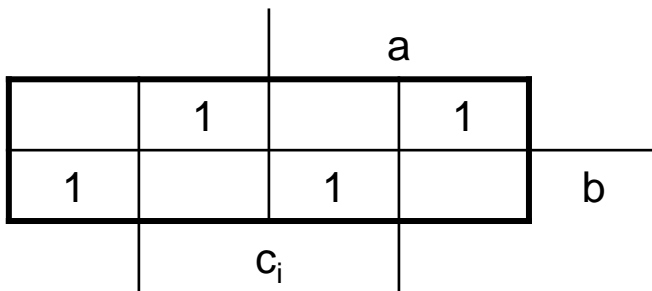
# Combinatorial Circuits (4)

- Design of Combinatorial Circuits (continued)
  - Switching function  $y(a,b,c_i)$



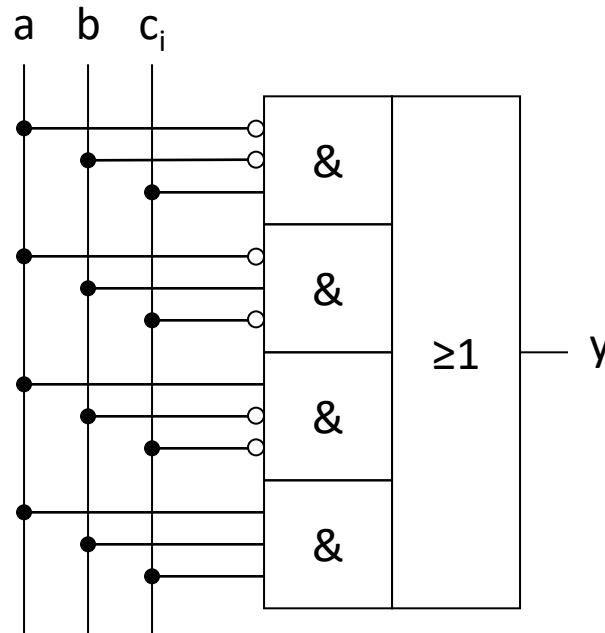
$$\begin{aligned}
 t_0 &= \neg a \wedge \neg b \wedge c_i \\
 t_1 &= \neg a \wedge b \wedge \neg c_i \\
 t_2 &= a \wedge \neg b \wedge \neg c_i \\
 t_3 &= a \wedge b \wedge c_i \\
 y &= t_0 \vee t_1 \vee t_2 \vee t_3
 \end{aligned}$$


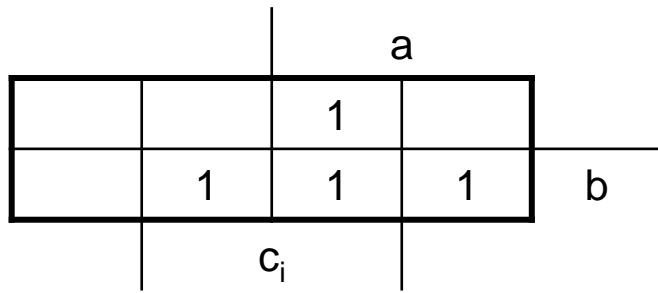
# Combinatorial Circuits (5)

- Design of Combinatorial Circuits (continued)
  - Switching function  $c_o(a,b,c_i)$




$$t_0 = a \wedge c_i$$

$$t_1 = b \wedge c_i$$



$$t_2 = a \wedge b$$

$$c_o = t_0 \vee t_1 \vee t_2$$

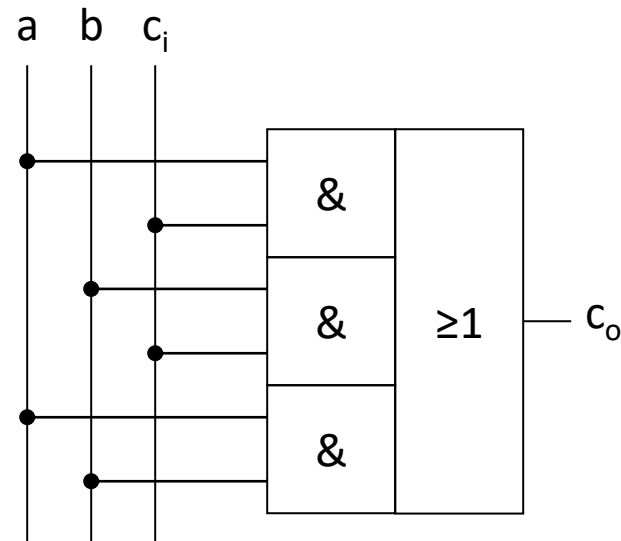

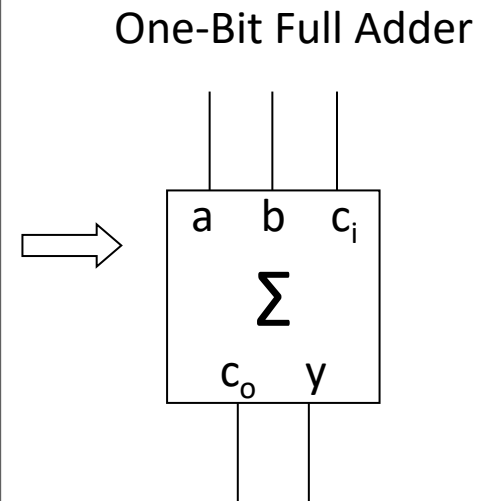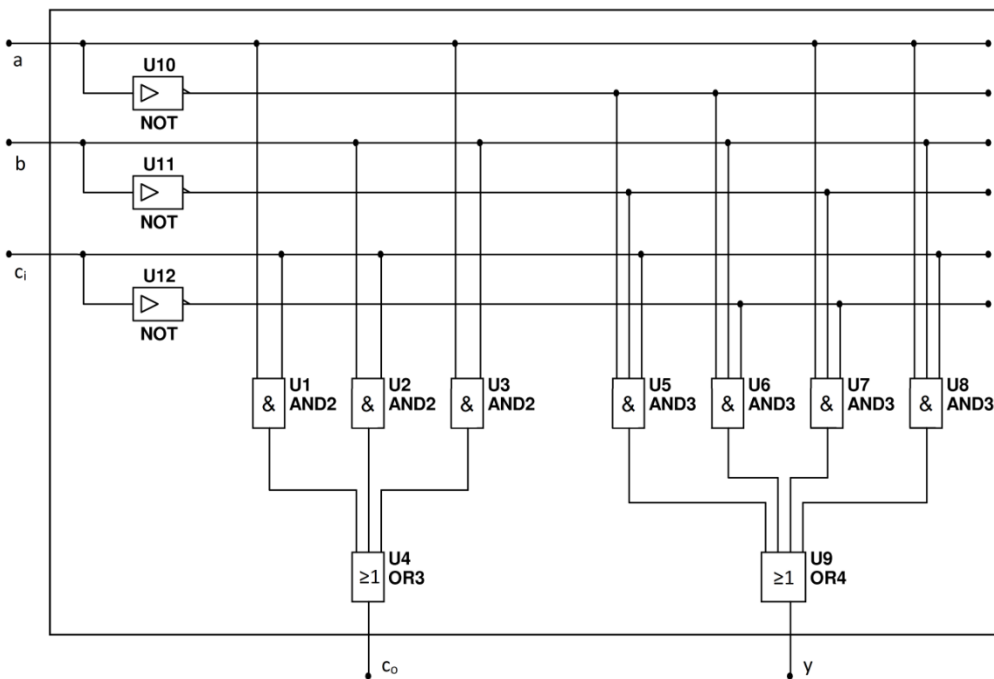
# Combinatorial Circuits (6)

- Design of Combinatorial Circuits (continued)
  - Both functions integrated in a circuit


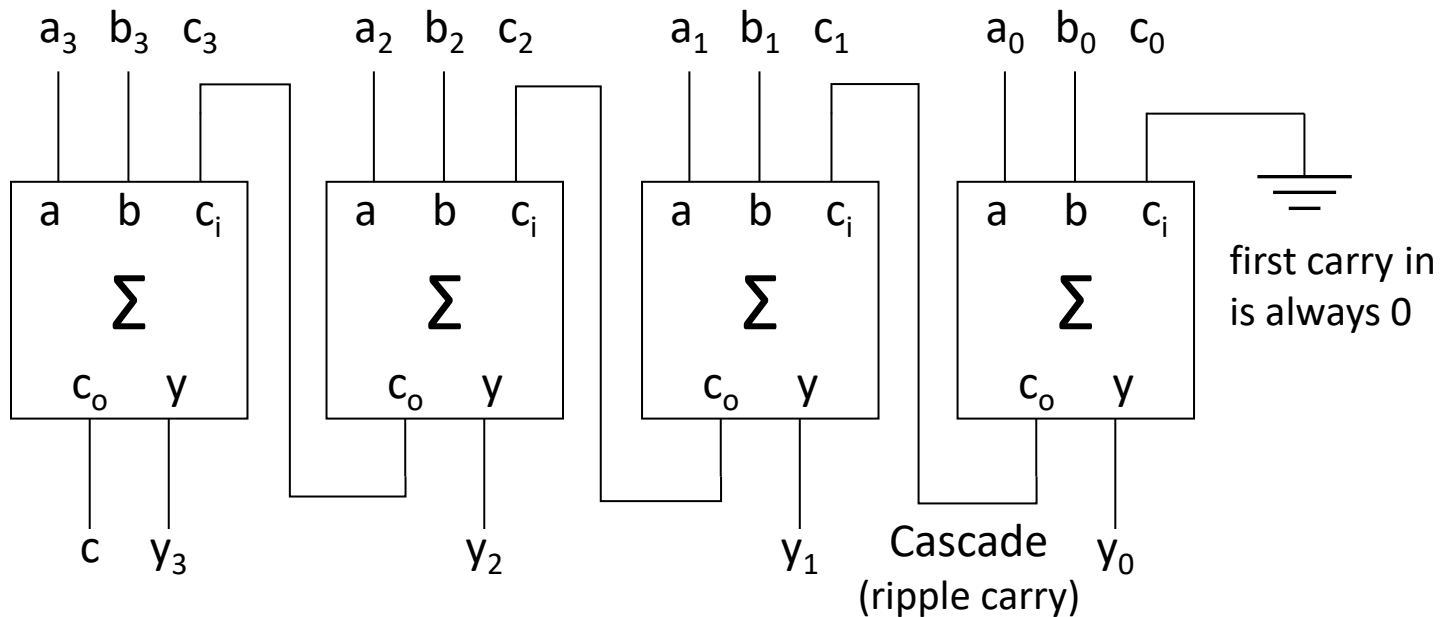
# Combinatorial Circuits (7)

- Design of Combinatorial Circuits (continued)
  - Four-bit Full Adder
    - Cascade of four one-bit full adders





# Combinatorial Circuits (8)

- Design of Combinatorial Circuits (finished)
  - Integrated four bit half adder

