

Series Resistors

Applied Mechatronics

First Grade Level


Wolfgang Neff

Series Resistors (1)

- Current Limiting Resistors
 - Devices can break if current is too high
 - Series resistors limit the current
 - They protect the device from damage
- Example LED
 - Supply voltage $V_S = 5 \text{ V}$
 - From datasheet for LED L-63ID
 - Typical forward voltage $V_F = 1.9 \text{ V}$
 - Typical forward current $I_F = 10 \text{ mA}$
 - Maximum forward current $I_F = 30 \text{ mA}$

Series Resistors (2)

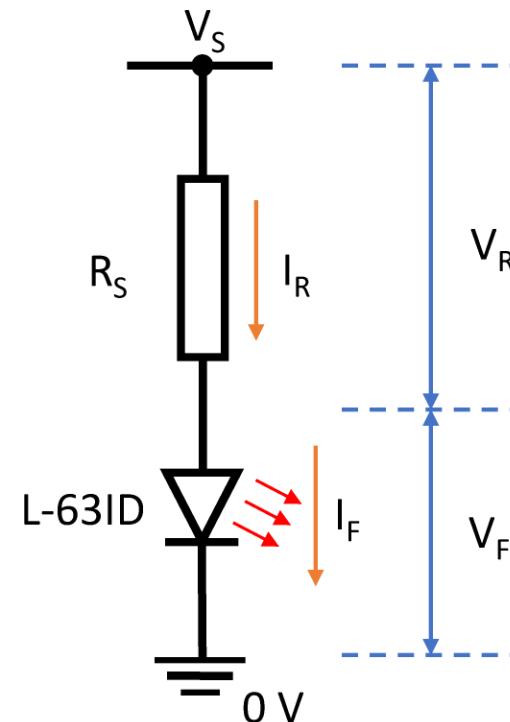- Derivation of the formula of the Series Resistor
 - Given values
 - I_F , V_F , V_S
 - Required values
 - R_S
 - Relations
 - $I_R = I_F$
 - $V_S = V_R + V_F$
 - $R_S = V_R / I_R$
 - Formula
 - $R_S = \frac{V_S - V_F}{I_F}$



Series Resistors (3)

- Calculation of the Series Resistor

- Given values

- $V_S = 5 \text{ V}$
- $V_F = 1.9 \text{ V}$
- $I_F = 10 \text{ mA}$


- Solution

- $$R_S = \frac{V_S - V_F}{I_F}$$

- $$R_S = \frac{5 \text{ V} - 1.9 \text{ V}}{10 \text{ mA}} = \frac{3.1 \text{ V}}{0.01 \text{ A}}$$


- $$R_S = 310 \Omega \rightarrow 330 \Omega$$

E12 Series of Resistors

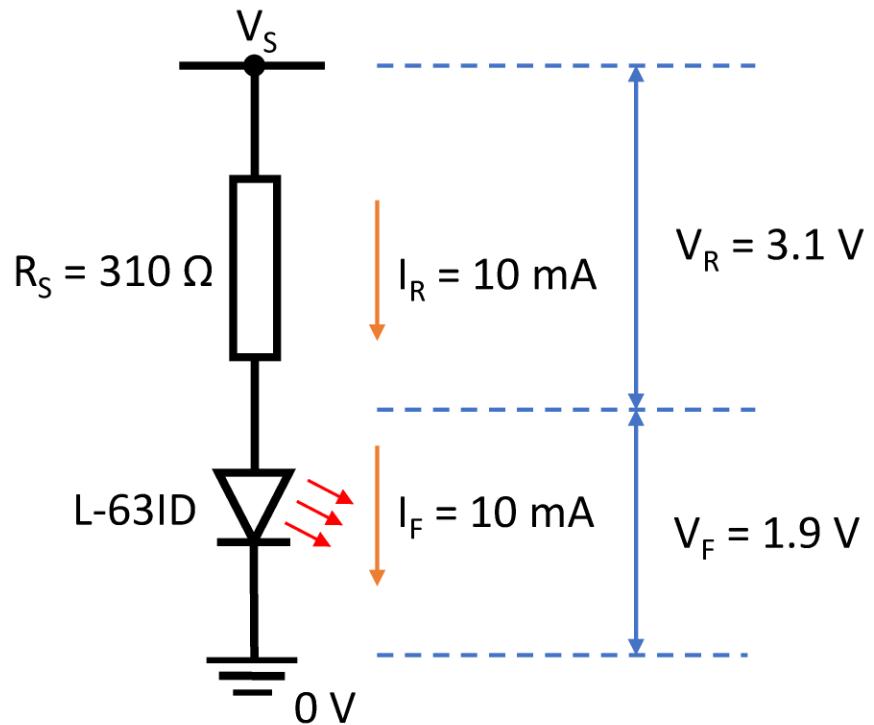

Series Resistors (4)

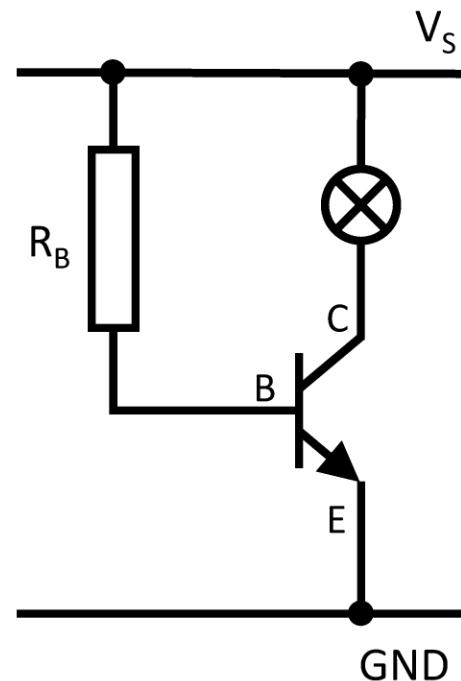
- Example Base Resistor
 - Supply voltage $V_S = 5 \text{ V}$
 - Load current $I_L = 350 \text{ mA}$
 - From datasheet for BC377-40
 - DC Current Gain $h_{FE} = 250$
 - Saturation Voltage $V_{BE} = 0.7 \text{ V}$



Series Resistors (5)

- Derivation of the formula of the Series Resistor

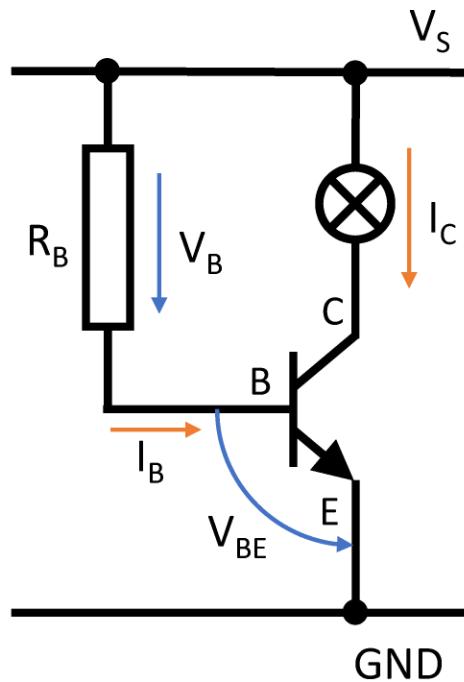- Given values
 - h_{FE} , I_C , V_{BE} , V_S
- Required values
 - I_B , R_B
- Relations
 - $I_c = h_{FE} \cdot I_B$
 - $V_S = V_B + V_{BE}$
 - $R_B = V_B / I_B$
- Formula
 - $R_B = \frac{V_S - V_{BE}}{I_C / h_{FE}} = h_{FE} \cdot \frac{V_S - V_{BE}}{I_C} = \frac{V_S - V_{BE}}{I_B}$



I_C : Collector Current = Load Current

I_B : Base Current

R_B : Base Resistor

V_B : Base Resistor Voltage

Series Resistors (6)


- Calculation of the Series Resistor

- Given values

- $V_S = 5 \text{ V}$
- $I_C = 350 \text{ mA}$
- $h_{FE} = 250$
- $V_{BE} = 0.7 \text{ V}$

- Solution

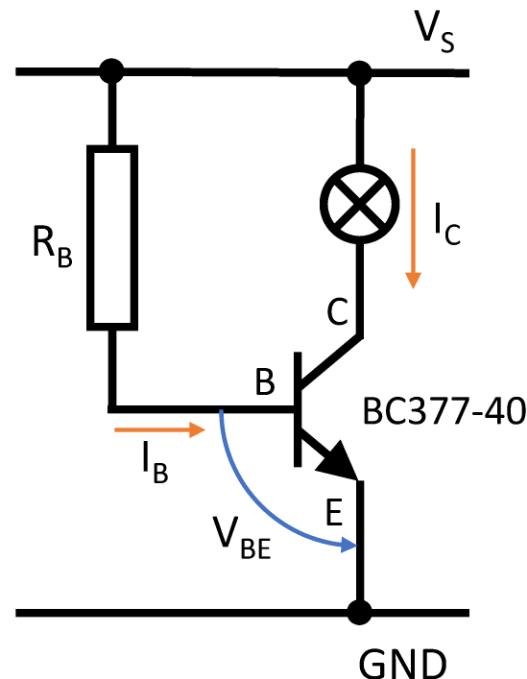- $I_B = \frac{I_C}{h_{FE}} = 1.4 \text{ mA}$
- $R_B = \frac{V_S - V_{BE}}{I_B}$
 $= 3071 \Omega \rightarrow 2.7 \text{ k}\Omega$



E12 Series