

Capacitors and Inductors


Electrical Engineering

Third Grade Level

Wolfgang Neff

Capacitors (1)

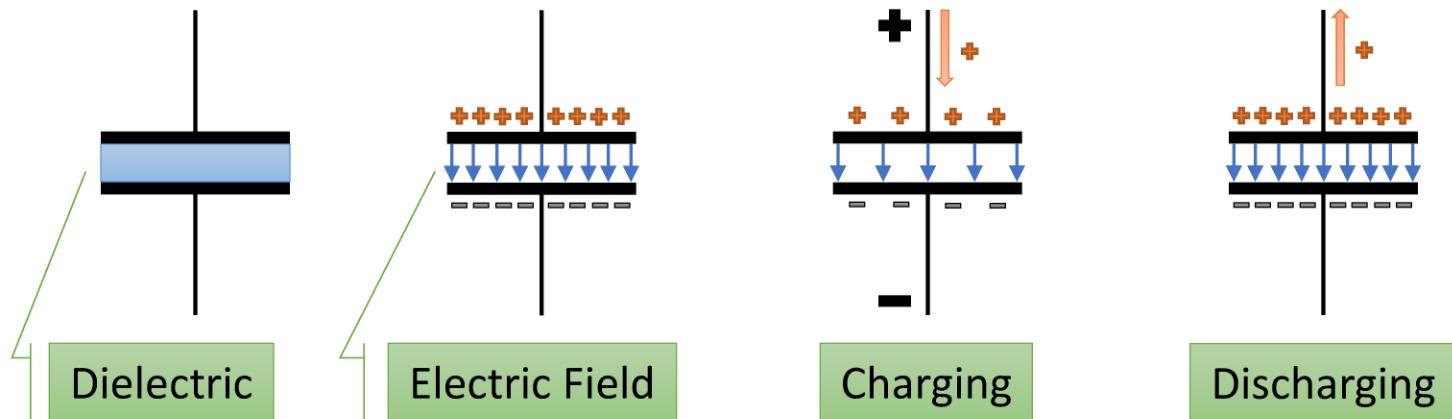- Basic Features
 - Accumulates electric charges on two surfaces
 - The surfaces are insulated from each other
 - Stores electrical energy in an electric field
 - It can be charged and discharged



Capacitors (2)

- Charging
 - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet I = \frac{dQ}{dt} = \dot{Q}$$

$$\bullet Q = C \cdot U$$


- Kirchhoff's circuit law

$$\bullet U_R + U_C - U = 0$$

$$\bullet R\dot{Q} + \frac{Q}{C} - U = 0$$



- Differential Equation
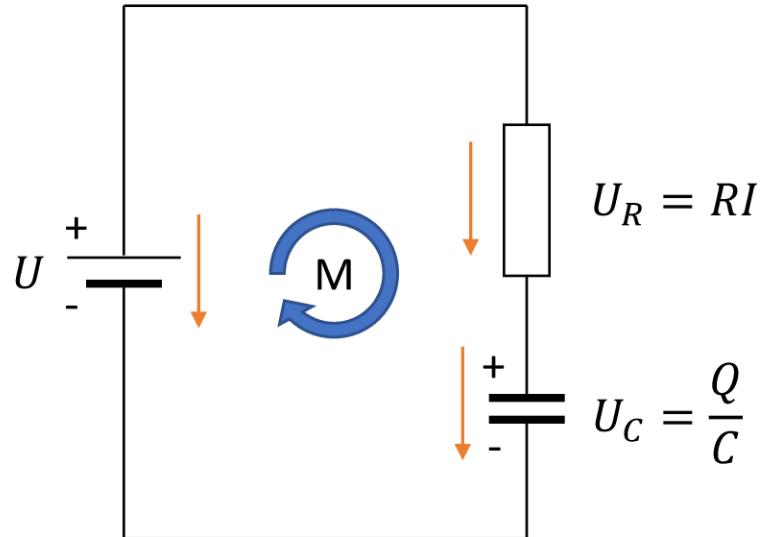
$$\bullet \dot{Q} = \frac{1}{R}U - \frac{1}{RC}Q$$



Capacitors (3)

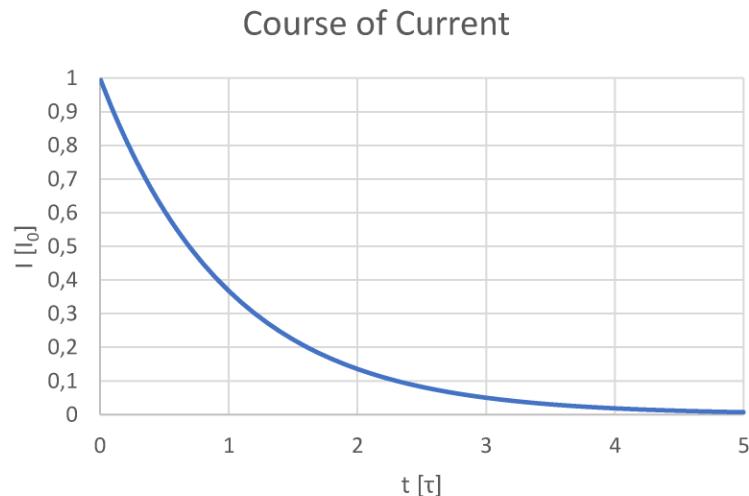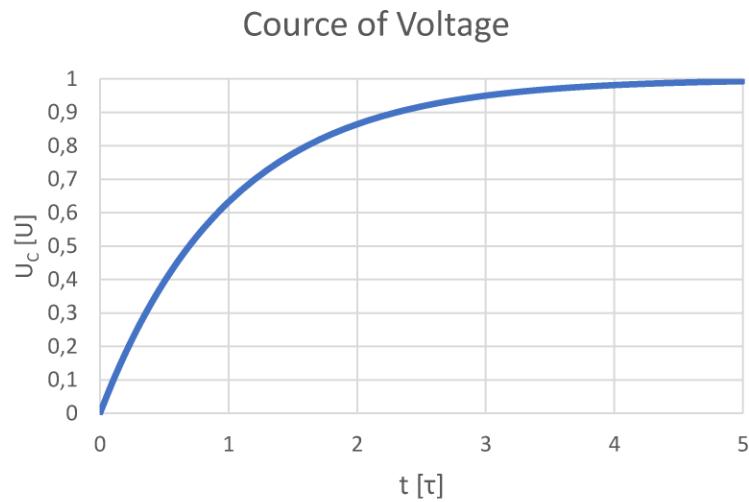- Charging (continued)
 - Solution of the equation
 - $Q = CU - CUe^{-\frac{1}{RC}t}$
 - $\tau = RC$ (time constant)
 - Course of the voltage
 - $U_C = \frac{Q}{C}$
 - $U_C = U(1 - e^{-\frac{t}{\tau}})$
 - Course of the current
 - $I = \dot{Q}$
 - $I = \frac{U}{R} e^{-\frac{t}{\tau}}$



Capacitors (4)

- Discharging
 - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet I = \frac{dQ}{dt} = \dot{Q}$$

$$\bullet Q = C \cdot U$$


- Kirchhoff's circuit law

$$\bullet -U_R + U_C = 0$$

$$\bullet -R\dot{Q} + \frac{Q}{C} = 0$$



- Differential Equation

$$\bullet \dot{Q} = -\frac{1}{RC}Q$$

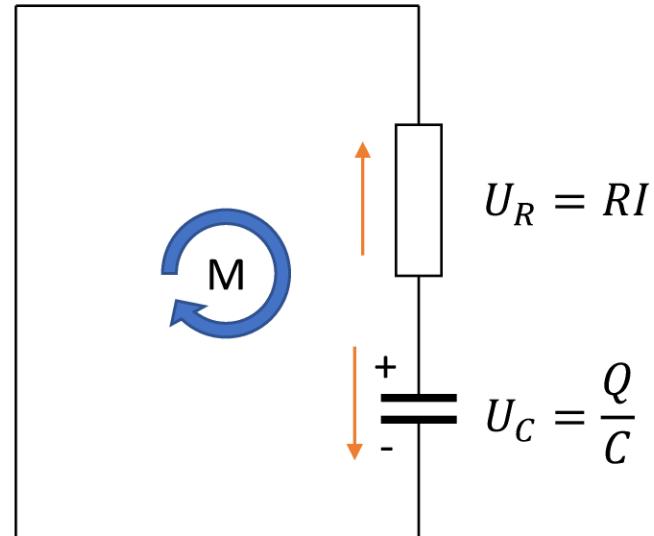

Capacitors (5)

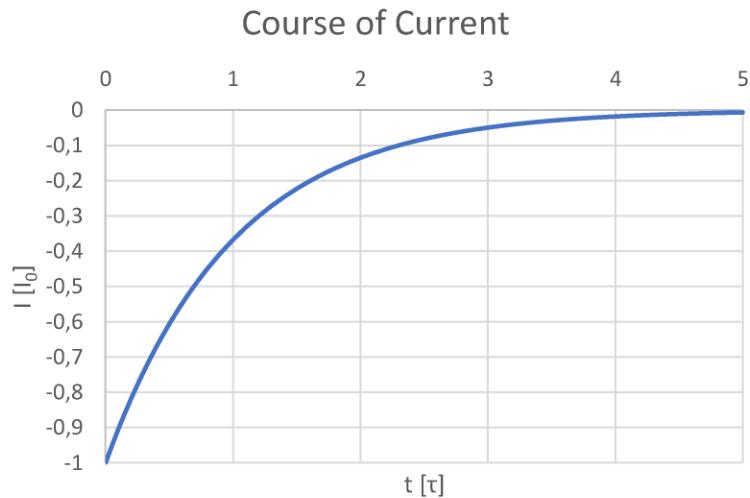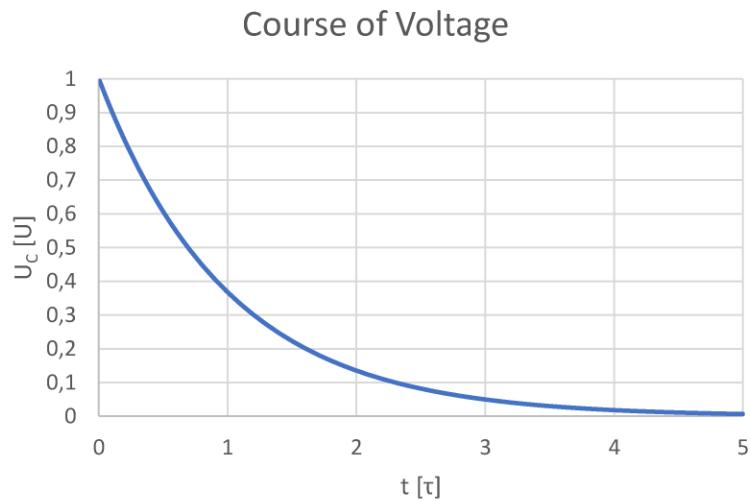- Discharging (continued)
 - Solution of the equation
 - $Q = CUe^{-\frac{1}{RC}t}$
 - $\tau = RC$ (time constant)
 - Course of the voltage
 - $U_C = \frac{Q}{C}$
 - $U_C = U(e^{-\frac{t}{\tau}})$
 - Course of the current
 - $I = \dot{Q}$
 - $I = -\frac{U}{R}e^{-\frac{t}{\tau}}$



Capacitors (6)


- Time Constant
 - $\tau = RC$
 - Half-value Time
 - $e^{-\frac{t_h}{\tau}} = \frac{1}{2}$
 - $t_h = \tau \ln 2$
 - $t_h = 0.69\tau$
 - Full Charge Time
 - $t_f = 5\tau$
 - $e^{-5} = 0.0067$
 - $1 - e^{-5} = 0.993$

τ	0	1	2	3	4	5
Charge	0%	63%	86%	95%	98%	99%
Discharge	100%	37%	14%	5%	2%	1%

τ	0.0	0.1	0.2	0.3	0.4	0.5
Charge	0%	10%	18%	26%	33%	39%
Discharge	100%	90%	82%	74%	67%	61%

Inductors (1)

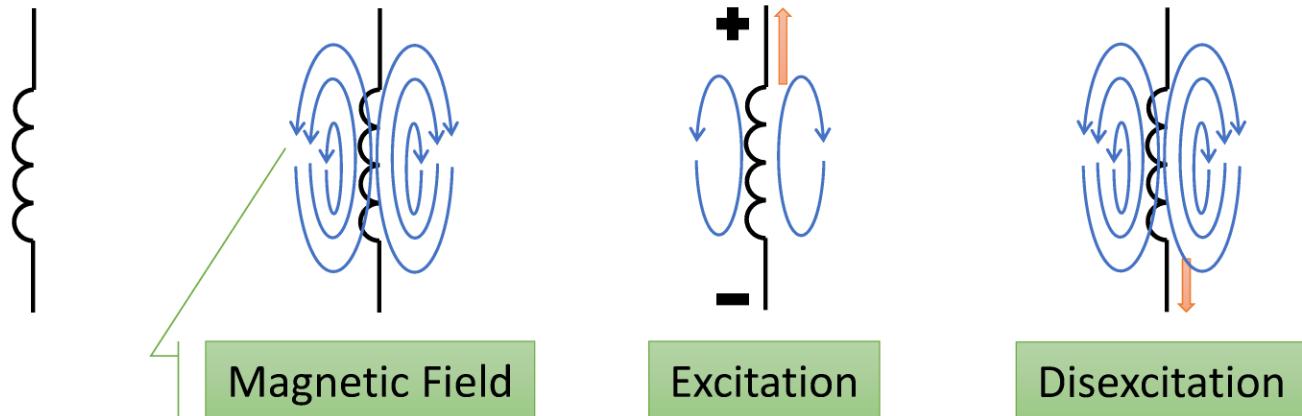- Basic Features
 - Stores electric energy when current flows through it
 - The energy gets stored in a magnetic field
 - A magnetic field can be excited and disexcited
 - The induced current opposes the change of the field



Inductors (2)

- Excitation
 - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet U_L = -L \frac{dI}{dt} = -LI\dot{}$$


- Kirchhoff's circuit law

$$\bullet U_R - U_L - U = 0$$

$$\bullet RI + LI\dot{} - U = 0$$



- Differential Equation
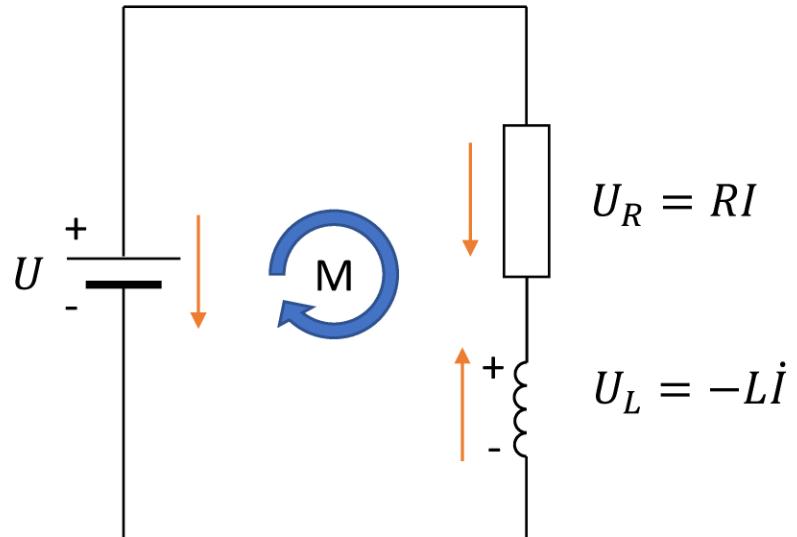
$$\bullet \dot{I} = \frac{1}{L}U - \frac{R}{L}I$$



Inductors (3)

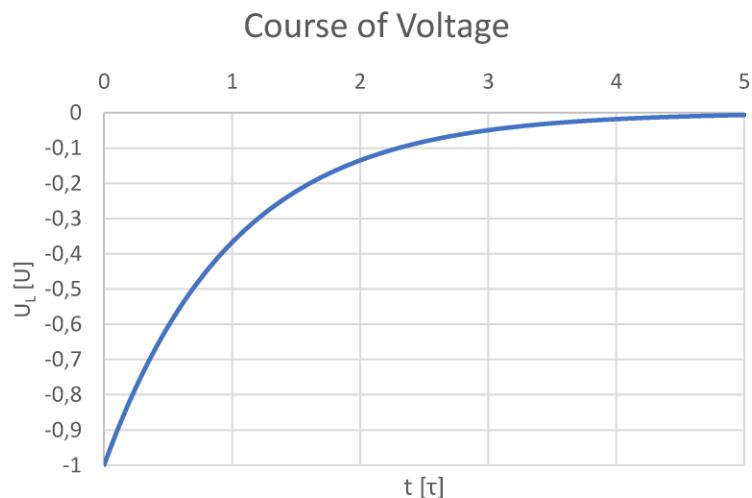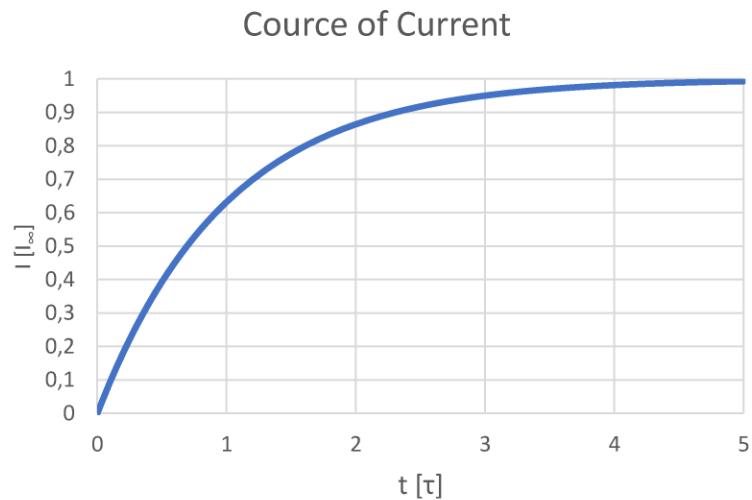- Excitation (continued)
 - Solution of the equation
 - $I = \frac{U}{R} \left(1 - e^{-\frac{R}{L}t}\right)$
 - $\tau = \frac{L}{R}$ (time constant)
 - Course of the current
 - $I = \frac{U}{R} \left(1 - e^{-\frac{t}{\tau}}\right)$
 - Course of the voltage
 - $U_L = -LI$
 - $U_L = -Ue^{-\frac{t}{\tau}}$



Inductors (4)

- Disexcitation
 - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet U_L = -L \frac{dI}{dt} = -LI\dot{}$$


- Kirchhoff's circuit law

$$\bullet U_R + U_L = 0$$

$$\bullet RI - LI\dot{ } = 0$$

- Differential Equation

$$\bullet \dot{I} = \frac{R}{L} I$$

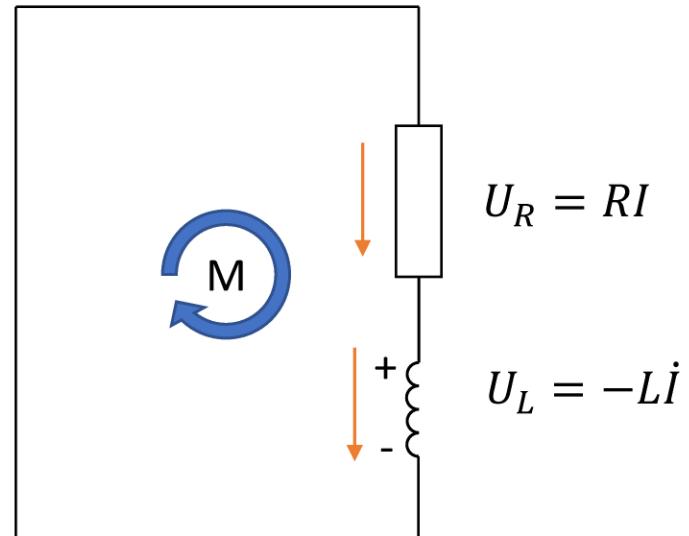

Capacitors (5)

- Disexcitation (continued)
 - Solution of the equation
 - $I = \frac{U}{R} e^{-\frac{R}{L}t}$
 - $\tau = \frac{L}{R}$ (time constant)
 - Course of the current
 - $I = \frac{U}{R} e^{-\frac{t}{\tau}}$
 - Course of the voltage
 - $U_L = -LI$
 - $U_L = U e^{-\frac{t}{\tau}}$

