



neff.site

© W. Neff


Voltage Divider

Electrical Engineering

Wolfgang Neff

Voltage Divider (1)

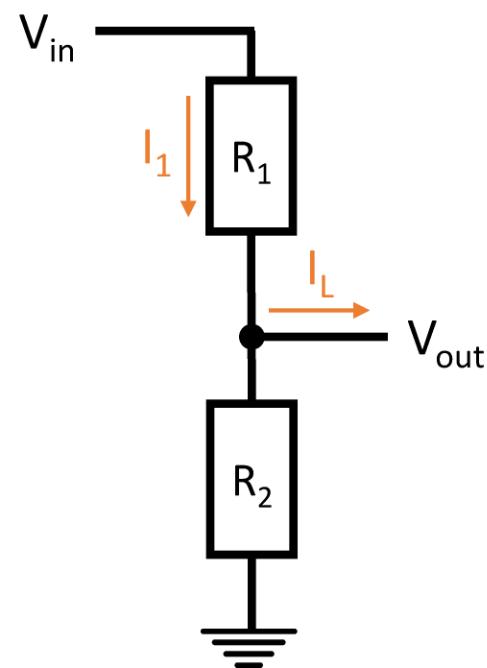
- Mode of Operation
 - Reduce voltage with the aid of resistors
 - Two resistors in series
 - Two modes
 - Unloaded voltage divider
 - $I_L = 0 \text{ A}$ ($I_L \leq 0.1 \cdot I_1$)
 - There is no load on V_{out}
 - Loaded voltage divider
 - $I_L > 0 \text{ A}$ ($I_L > 0.1 \cdot I_1$)
 - There is a load on V_{out}



Voltage Divider (2)

- Unloaded voltage divider

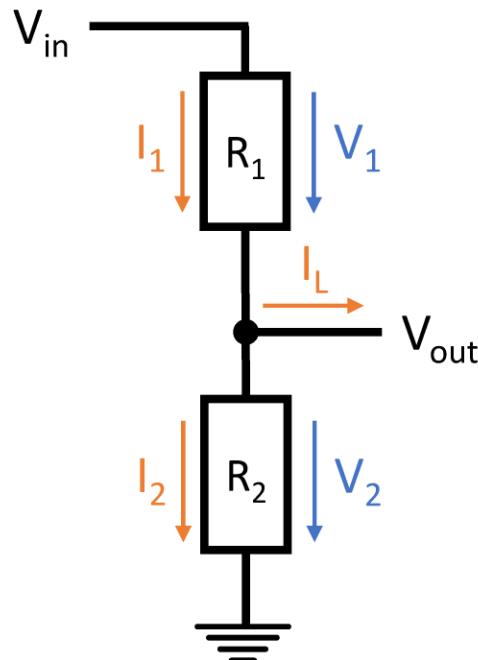- Given values
 - R_1, R_2, V_{in}
- Required values
 - V_{out}, I_V, P_{tot}
- Relations
 - $I_L = 0 \text{ A}$
 - $V_{out} = V_2$
 - $I_V = I_1 = I_2$
 - $R_{tot} = R_1 + R_2$
 - $P_{tot} = V_{in} \cdot I_V$



V_{in} : Input Voltage

V_{out} : Output Voltage

I_L : Load Current

I_V : Vertical Current

R_{tot} : Total Resistance

P_{tot} : Total Power Loss

Voltage Divider (3)

- Unloaded voltage divider (continued)

- Relations

- $I_2 = \frac{V_2}{R_2}$


- $\frac{V_2}{V_{in}} = \frac{R_2}{R_{tot}}$

- Formulas

- $V_{out} = \frac{R_2}{R_1+R_2} \cdot V_{in}$

- $I_V = \frac{V_{out}}{R_2}$

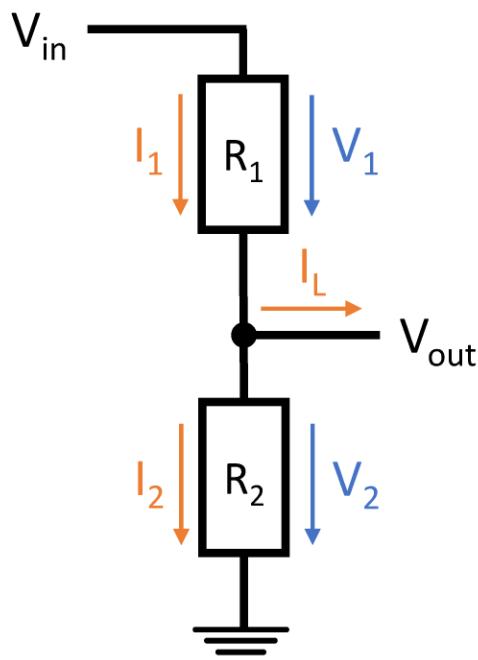- $P_{tot} = \frac{V_{in} \cdot V_{out}}{R_2}$



Voltage Divider (4)


- Unloaded voltage divider (example)

- Given values

- $V_{in} = 5 \text{ V}$
 - $R_1 = 100 \Omega$
 - $R_2 = 120 \Omega$

- Calculation

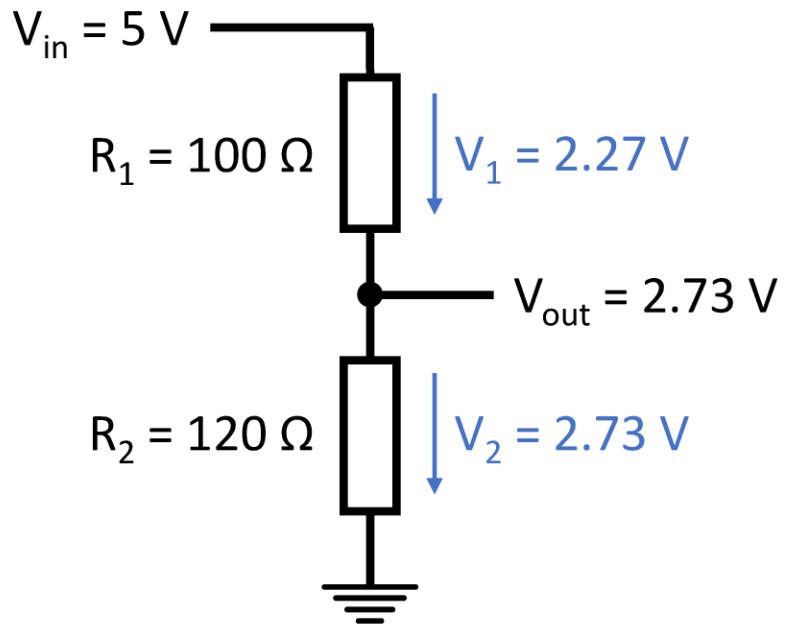- $$V_{out} = \frac{R_2}{R_1+R_2} \cdot V_{in}$$
$$= \frac{120 \Omega}{100 \Omega+120 \Omega} \cdot 5 \text{ V}$$
$$= 2.73 \text{ V}$$




Voltage Divider (5)

- Unloaded voltage divider (example continued)

- Calculation

$$\begin{aligned} I_V &= \frac{V_{out}}{R_2} \\ &= \frac{2.73 \text{ V}}{120 \Omega} \\ &= 23 \text{ mA} \end{aligned}$$
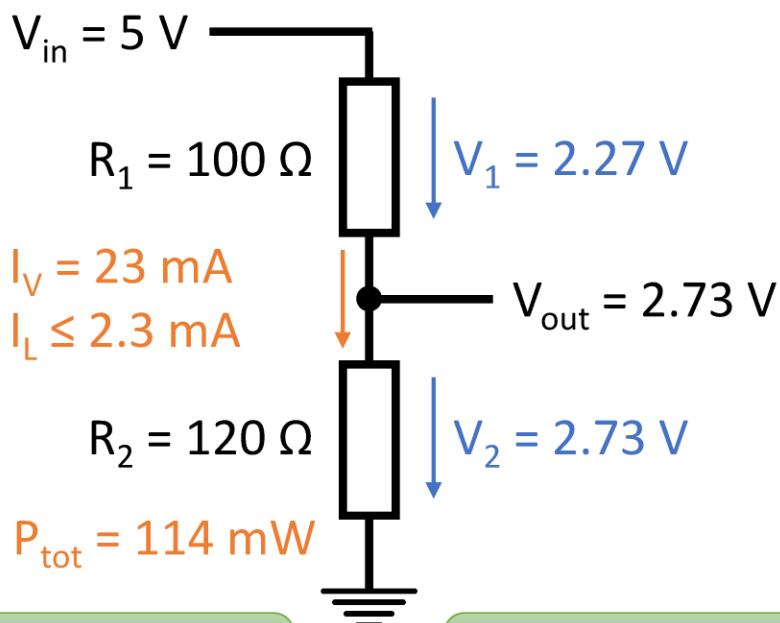
$$\begin{aligned} P_{tot} &= \frac{V_{in} \cdot V_{out}}{R_2} \\ &= \frac{5 \text{ V} \cdot 2.73 \text{ V}}{120 \Omega} \\ &= 114 \text{ mW} \end{aligned}$$



A loss of 114 mW is relatively high.

A load of 2.3 mA is relatively low.

Voltage Divider (6)

- Voltage Divider with Amplifier
 - Loaded voltage divider are difficult to handle
 - Current load may be unknown
 - Current load may vary
 - An amplifier can eliminate the load current

