


# Diodes

Digital Electronics

by Wolfgang Neff

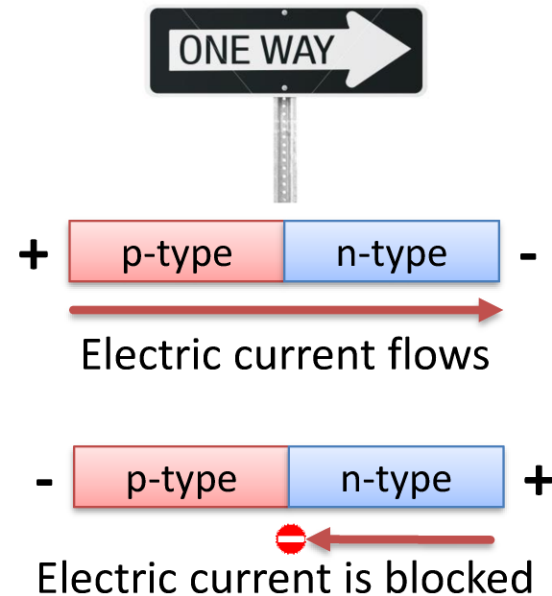
# Diodes (1)

- P–n junctions are diodes
  - Flow Control Valve
    - One-Way Road
  - Forward
    - P-type: +, n-type: -
    - Current flows
  - Reverse
    - P-type: -, n-type: +
    - Current gets blocked





# Diodes (2)

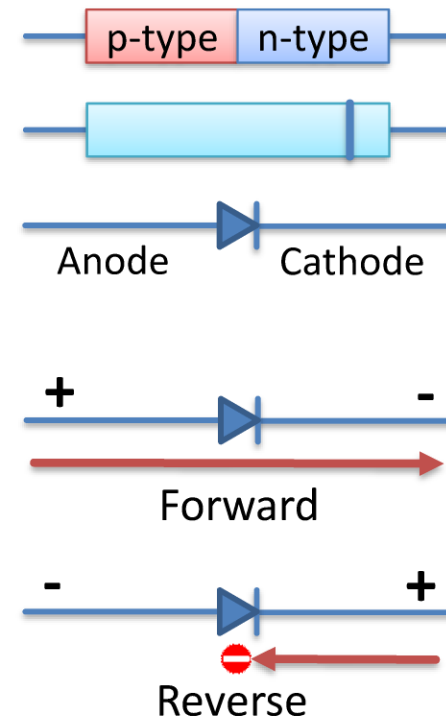- Example: 1N4148
  - Maximum forward current
    - $I_F = 300 \text{ mA}$
  - Maximum reverse voltage
    - $V_R = 100 \text{ V}$
  - Reverse Leakage
    - $I_R = 0.025 \text{ } \mu\text{A}$  ( $V_R = 20 \text{ V}$ )
    - $I_R = 5.0 \text{ } \mu\text{A}$  ( $V_R = 70 \text{ V}$ )



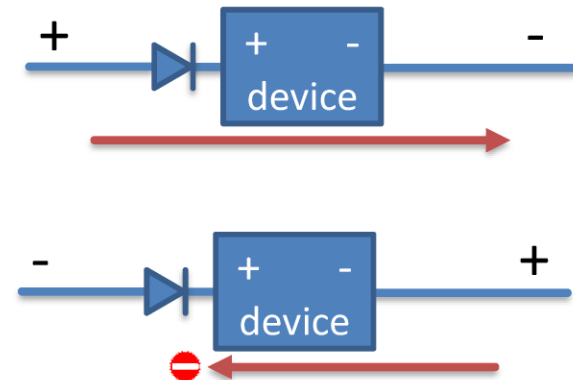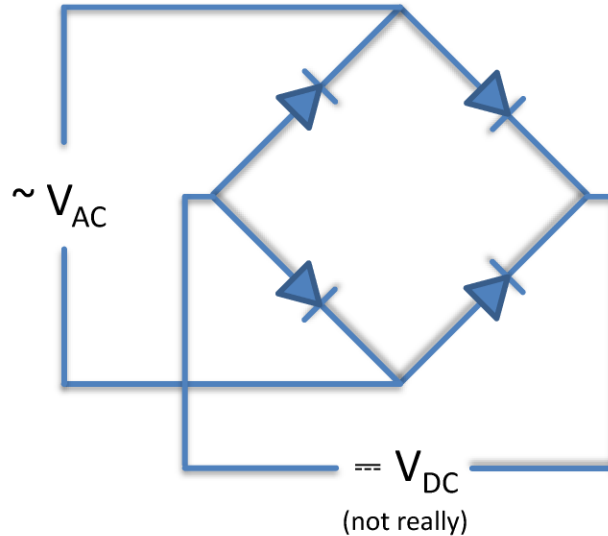
# Diodes (3)

- Applications
  - Reverse voltage protection
  - Rectifier (e. g. mobile phone charger)




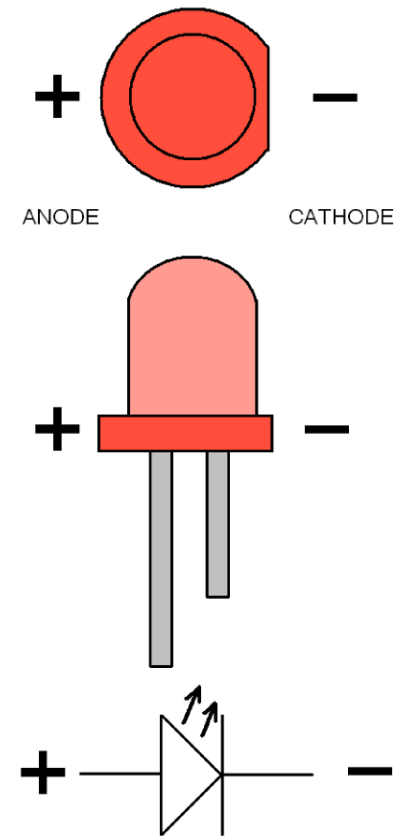
# Diodes (4)

- Light-emitting diodes
  - They emit light
  - They have different colors
- They have two leads
  - Long one: anode (+)
  - Short one: cathode (-)


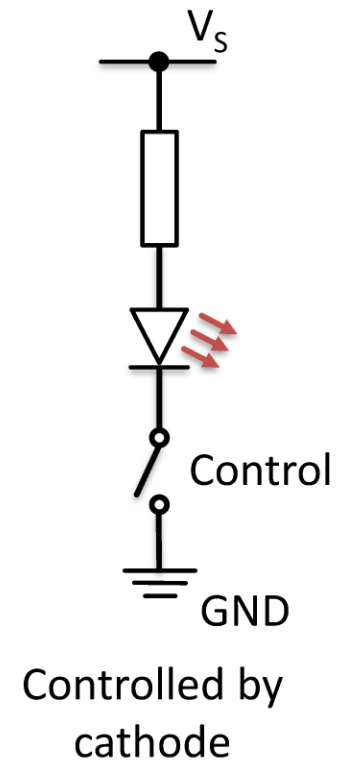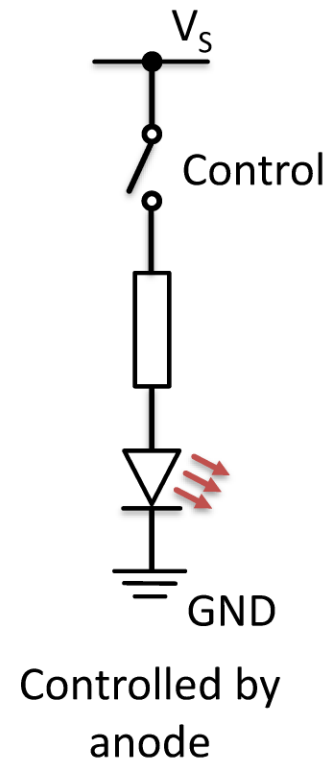
# Diodes (5)

- Control of LED
  - They can be switched on or off
  - There are two options
    - Control by anode
      - Cathode with GND
    - Control by cathode
      - Anode with PWR



# Diodes (6)

- Example: L-63ID
  - Typical wavelength
    - $\lambda = 627 \text{ nm}$  (red)
  - Typical forward voltage
    - $V_F = 1.9 \text{ V}$
  - Maximum forward current
    - $I_F = 30 \text{ mA}$



# Diodes (7)

- Series resistor

$$- I_R = I_F$$

$$- V_R = V_S - V_F$$

$$- R = \frac{V_R}{I_R} = \frac{V_S - V_F}{I_F}$$

$$- R = \frac{5\text{ V} - 1.9\text{ V}}{20\text{ mA}} = \frac{3.1\text{ V}}{0.02\text{ A}}$$

$$- R = 155\ \Omega \rightarrow 180\ \Omega$$

E12 Series of Resistors

