



neff.site

© W. Neff


Digital Circuits

Digital Electronics

Wolfgang Neff

Digital Circuits (1)

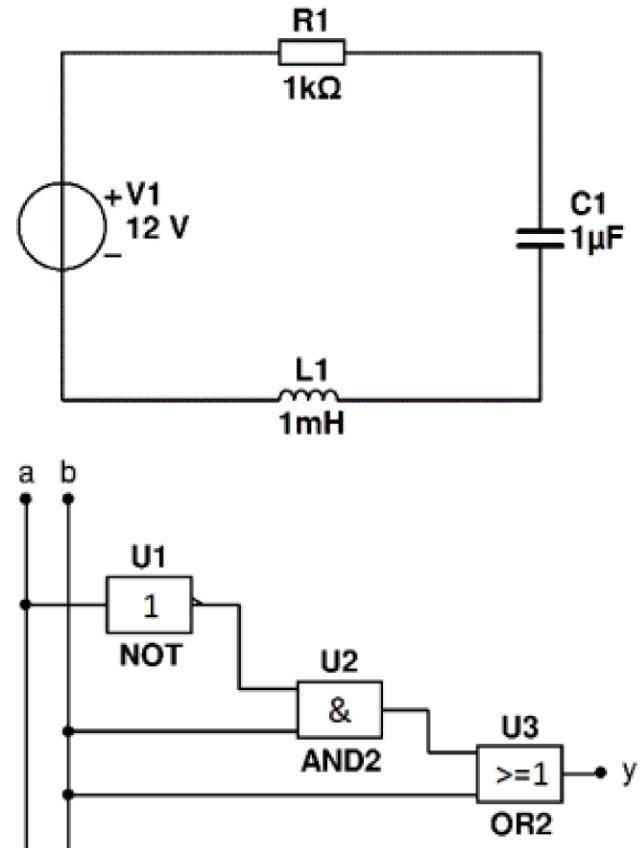- Analog and Digital
 - Analog Circuits
 - Any voltage level allowed
 - Digital Circuits
 - Two voltage levels allowed
 - + and –
 - 1 and 0
 - H and L




Digital Circuits (2)

- Basic Concept
 - Based on Boolean algebra
 - $0 \rightarrow$ Low voltage
 - $1 \rightarrow$ High voltage
 - Operator \rightarrow Symbol
 - Function \rightarrow Circuit
 - Terms
 - Logical functions \rightarrow Switching function
 - Truth table \rightarrow Switching table

Digital Circuits (3)

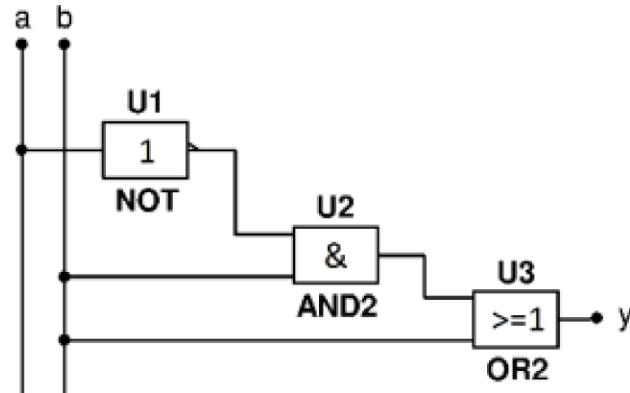
- Basic Concept (continued)
 - Truth function ...
 - $\phi(a,b) = (\neg a \wedge b) \vee b$
 - ... represented graphically



Digital Circuits (4)


- Graphic Symbols

- Buffer

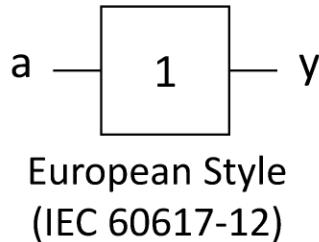

a	y=a
0	0
1	1

- Negation (NOT, \neg)

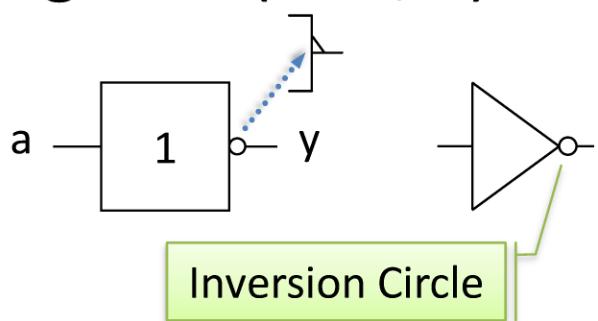


a	y= \neg a
0	1
1	0


Digital Circuits (5)

- Graphic Symbols (continued)

- Disjunction (OR, \vee)

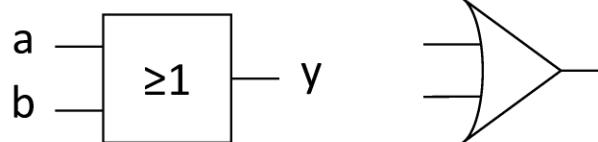

- Conjunction (AND, \wedge)

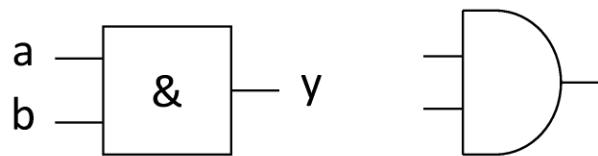



a	b	$y=a \vee b$
0	0	0
0	1	1
1	0	1
1	1	1

a	b	$y=a \wedge b$
0	0	0
0	1	0
1	0	0
1	1	1



Digital Circuits (6)

- Graphic Symbols (continued)

– NOR (\downarrow)

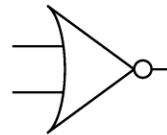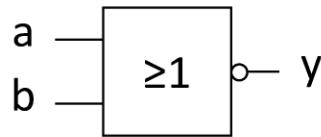

– NAND ($|$)

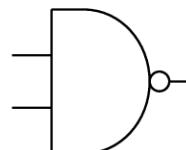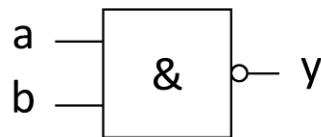


a	b	$y=a \downarrow b$
0	0	1
0	1	0
1	0	0
1	1	0

a	b	$y=a b$
0	0	1
0	1	1
1	0	1
1	1	0

Digital Circuits (7)

- Graphic Symbols (finished)

- XOR (\oplus)

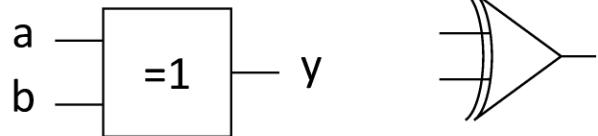


a	b	y=a⊕b
0	0	0
0	1	1
1	0	1
1	1	0

- Compound Gates

- AND-Gate

- $$y = a_0 \wedge a_1 \wedge a_2 \dots$$
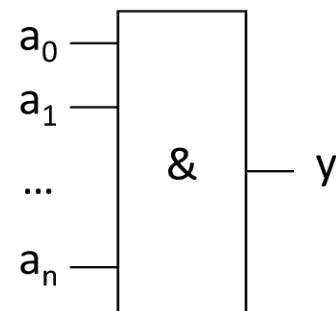
$$(a_0, a_1, \dots) \mapsto \begin{cases} 1 & \text{if each } a_i = 1 \\ 0 & \text{else} \end{cases}$$




Digital Circuits (8)

- Compound Gates (continued)

- OR-Gate

- $y = a_0 \vee a_1 \vee a_2 \dots$

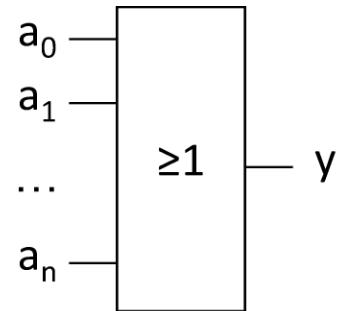
$$(a_0, a_1, \dots) \mapsto \begin{cases} 0 & \text{if each } a_i = 0 \\ 1 & \text{else} \end{cases}$$



- Composition

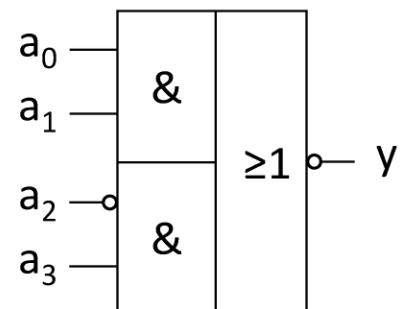- Example




- $\neg((a_0 \wedge a_1) \vee (\neg a_2 \wedge a_3))$



Digital Circuits (9)

- Building Blocks




$$- y = \neg a \wedge b$$

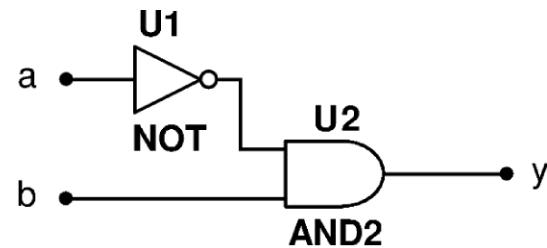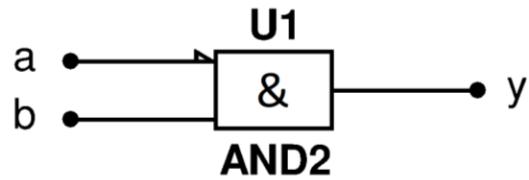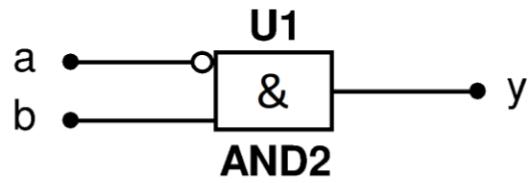

Digital Circuits (10)

- Building Blocks (continued)



$$- y = \neg(a \wedge b)$$

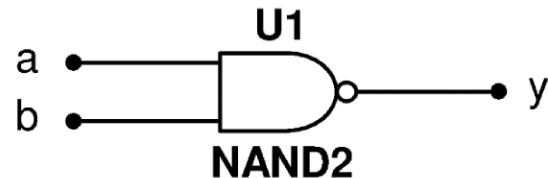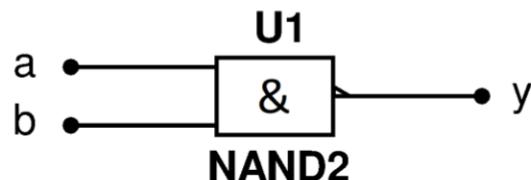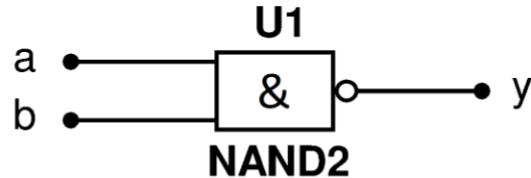

Digital Circuits (11)

- Building Blocks (continued)



$$- y = (a \wedge b) \vee c$$

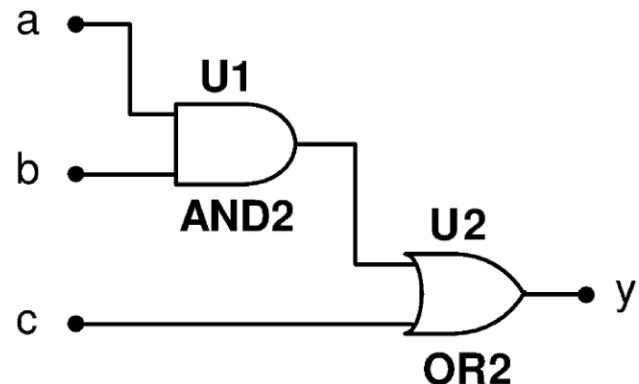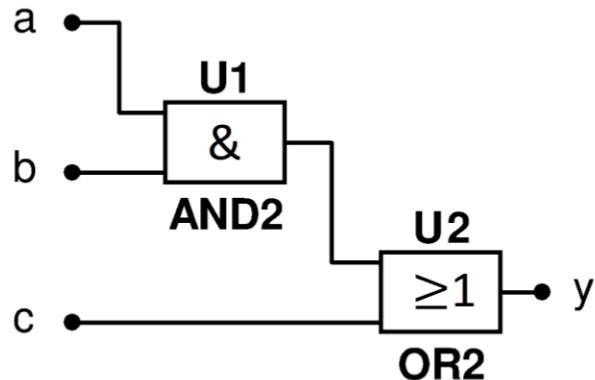

Digital Circuits (12)

- Building Blocks (finished)

$$- y = a \wedge (b \vee c)$$

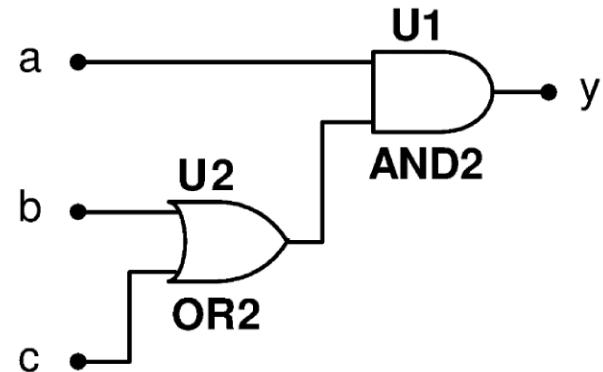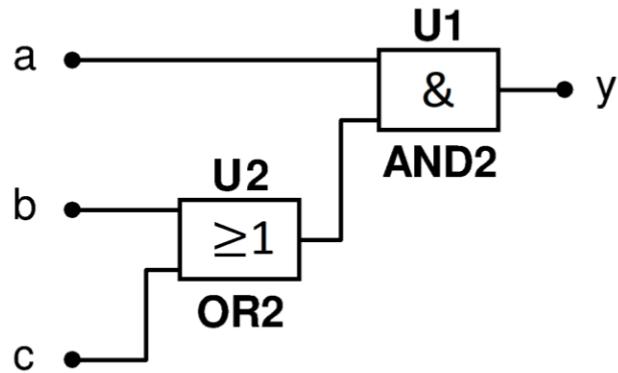

Digital Circuits (13)

- Example

$$y = (a \wedge \neg b) \vee \neg(c \wedge a) \vee c$$

