


# Prescalers

Digital Electronics

by Wolfgang Neff
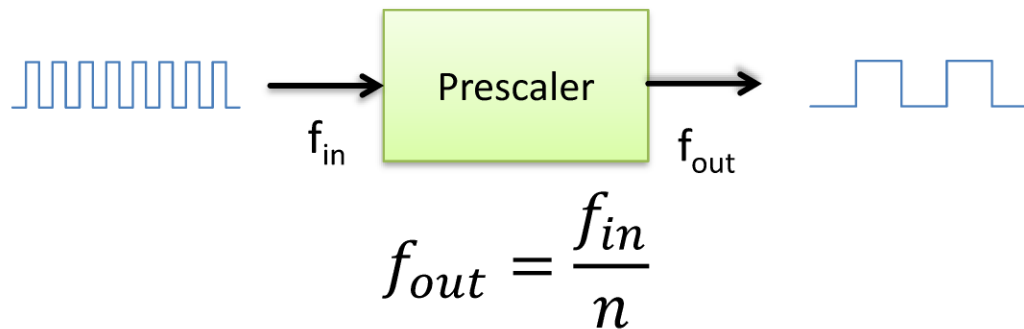
# Prescalers (1)

- Reduces the frequency of an input signal
  - Also called
    - Clock divider
    - Frequency divider
  - Divides the input frequency by a factor



# Prescalers (2)

- Frequency is Reduced by Counting

– Example


- Mod-8 counter  $\rightarrow$  3 binary digits ( $Q_0, Q_1, Q_2$ )

Ticks	0	1	2	3	4	5	6	7	Div						
Clock	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1
$Q_0$	0	1	0	1	0	1	0	1	0	1	0	1	0	1	2
$Q_1$	0	0	1	1	0	0	1	1	0	0	1	1	0	0	4
$Q_2$	0	0	0	0	1	1	1	1	0	0	1	1	0	0	8

# Prescalers (3)

- Implementation


- Use T flip-flops (toggles its state)

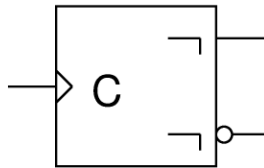

Q <sup>+</sup>	Action
-Q	Toggle state


- Cascade

- Example: 4 stage frequency divider

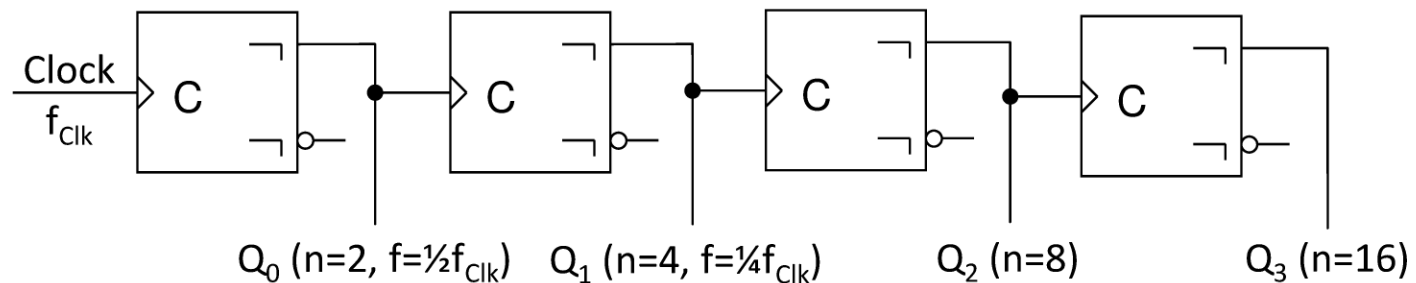

# Prescalers (4)

- 4024 – 7-stage frequency divider

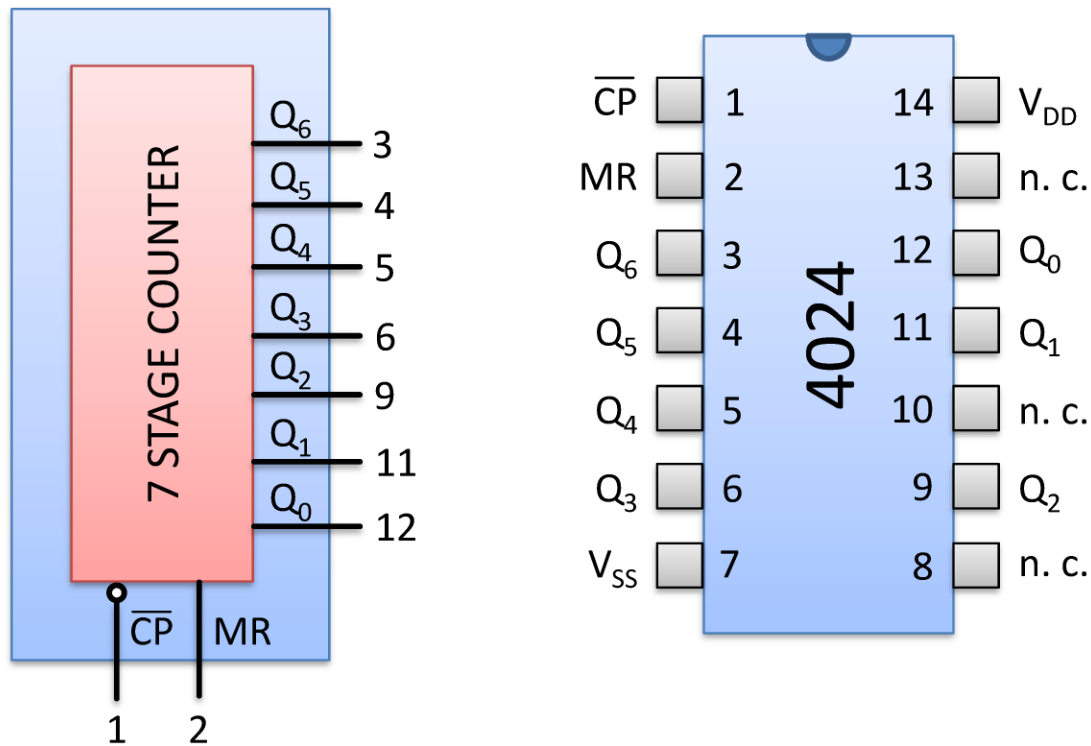

# Prescalers (5)

- 4024 – 7-stage frequency divider (continued)

Symbol	Pin	Description
$\overline{CP}$	1	clock input
MR	2	master reset input
$V_{SS}$	7	ground
n. c.	8, 10, 13	not connected
$Q_0, Q_1, Q_2, Q_3, Q_4, Q_5, Q_6$	12, 11, 9, 6, 5, 4, 3	buffered parallel outputs
$V_{DD}$	14	supply voltage