

Display Drivers

Digital Electronics

Wolfgang Neff

Indicator Lamps (1)

- Indicates information
 - Lamp itself has no information
 - Information comes from context




Okay



Error

Function
Indicator

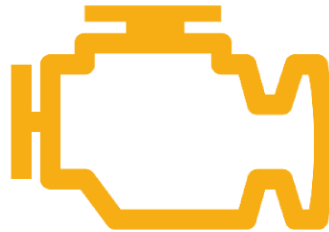

Engine Malfunction
Indicator Lamp




Third floor



Second floor



First floor


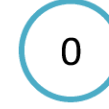


Basement floor

Elevator Floor
Indicator




Indicator Lamps (2)

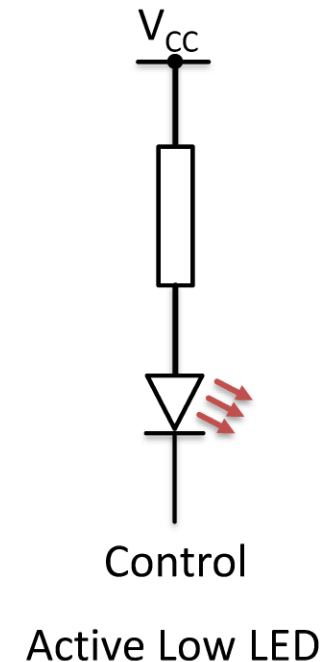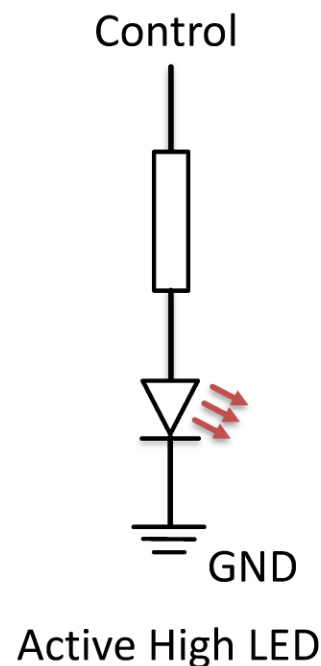- Light-Emitting Diodes
 - Switched on or off by control pin
 - Two operation
 - Active high (on = 1)
 - Active low (on = 0)





Indicator Lamps (3)

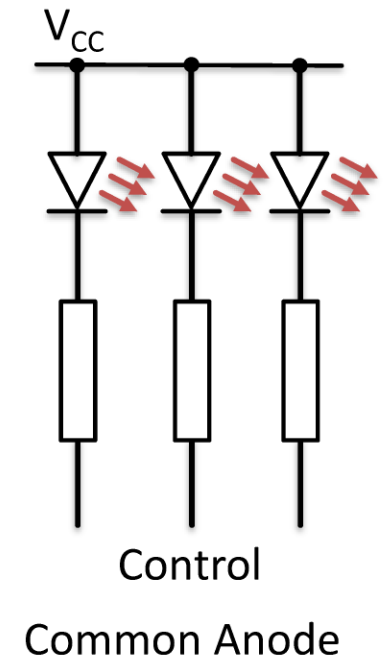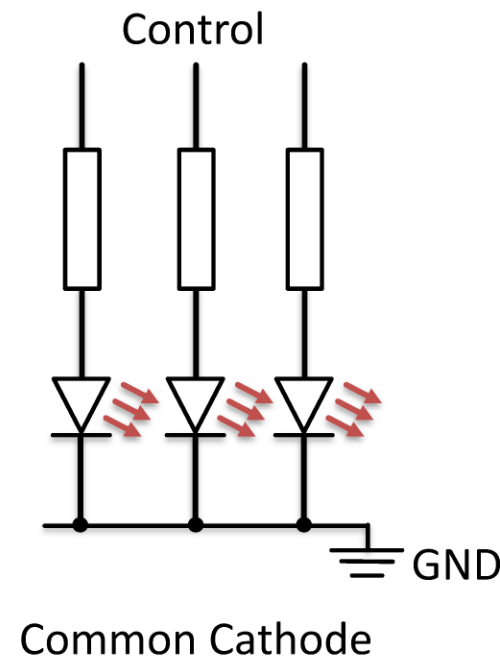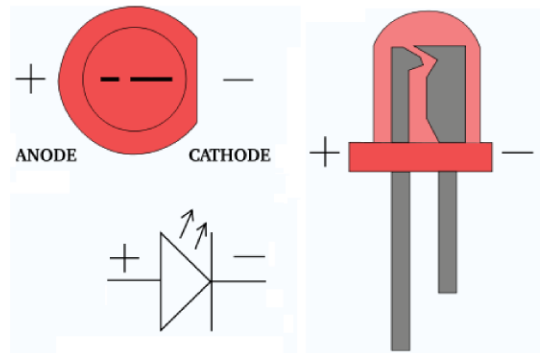- LEDs can be combined
 - Common Cathode
 - Active High
 - Common Anode
 - Active Low



Seven-Segment Displays (1)

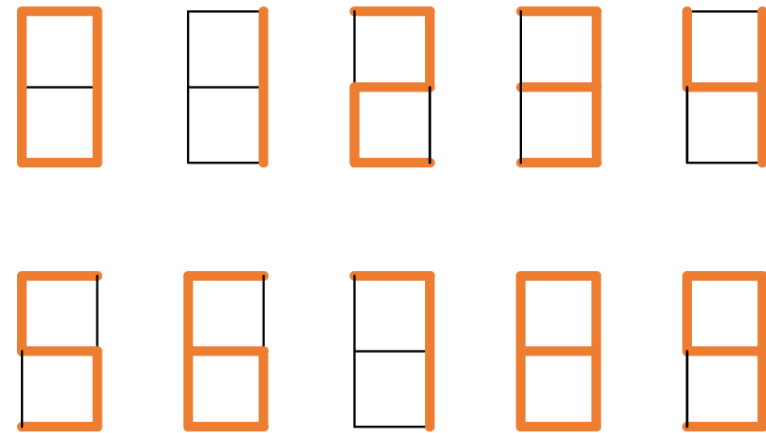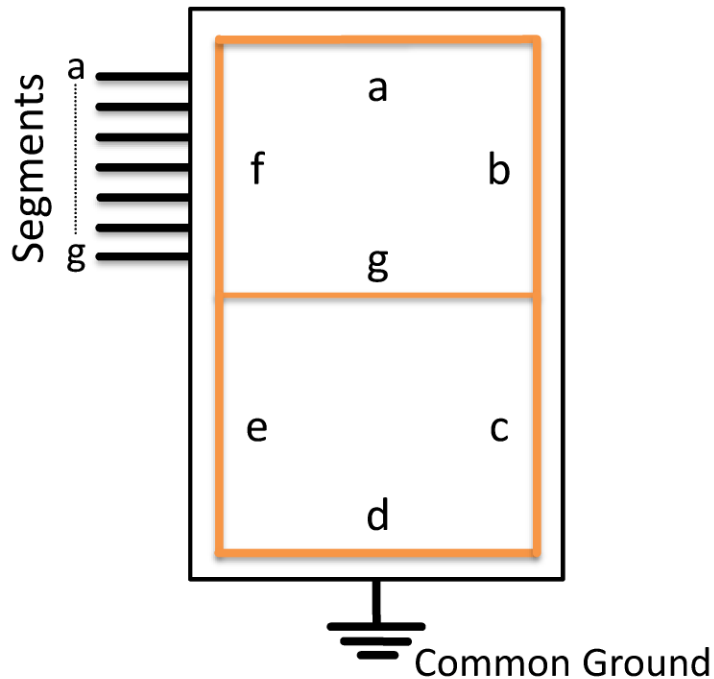
- Mode of Operation
 - Seven segments display a number



Number Representation

Seven-Segment Displays (2)

- Seven-Segment Driver

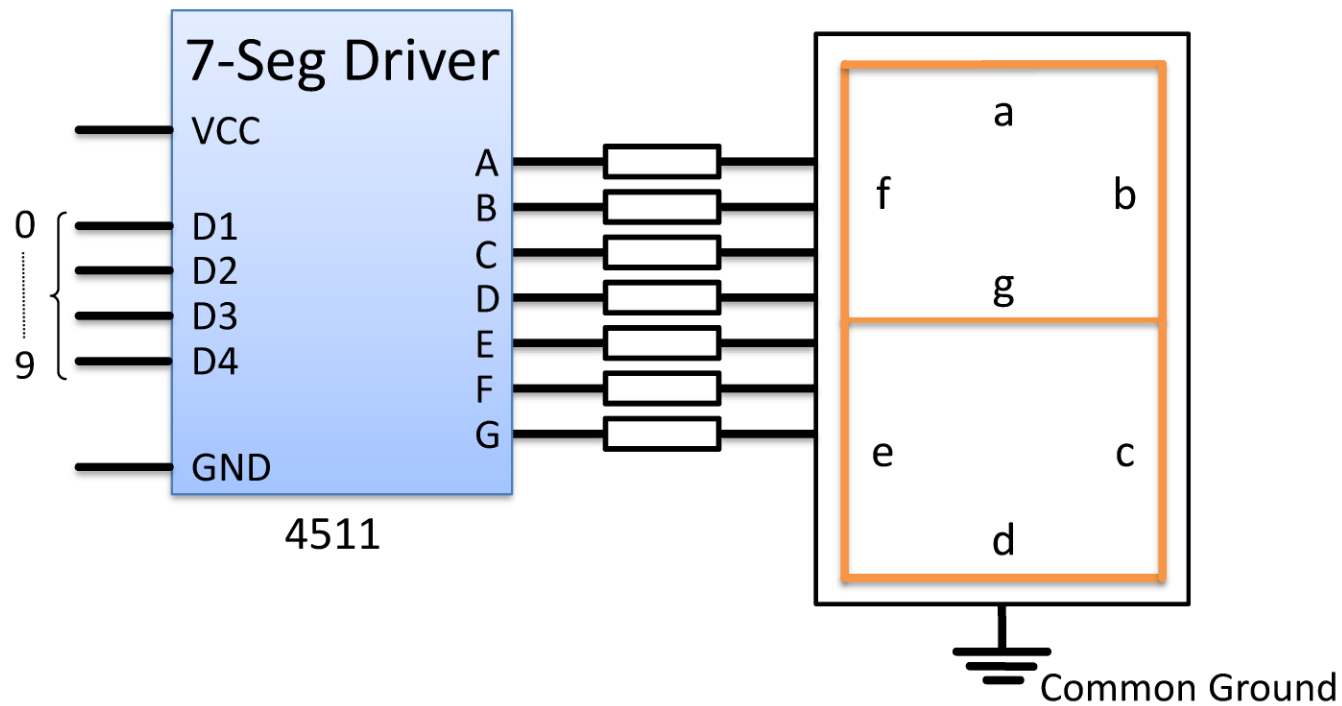

Dot-Matrix Displays (1)


- LEDs arranged in a block

- Arranged in

- Columns
 - Rows


- Example

- 8×8 dot-matrix 

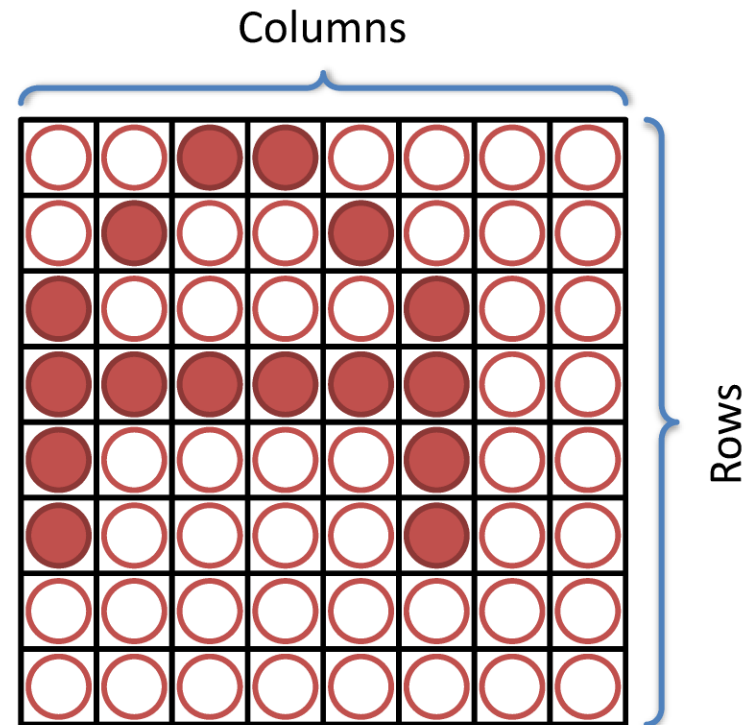


Dot-Matrix Displays (2)

- Electrical Setup

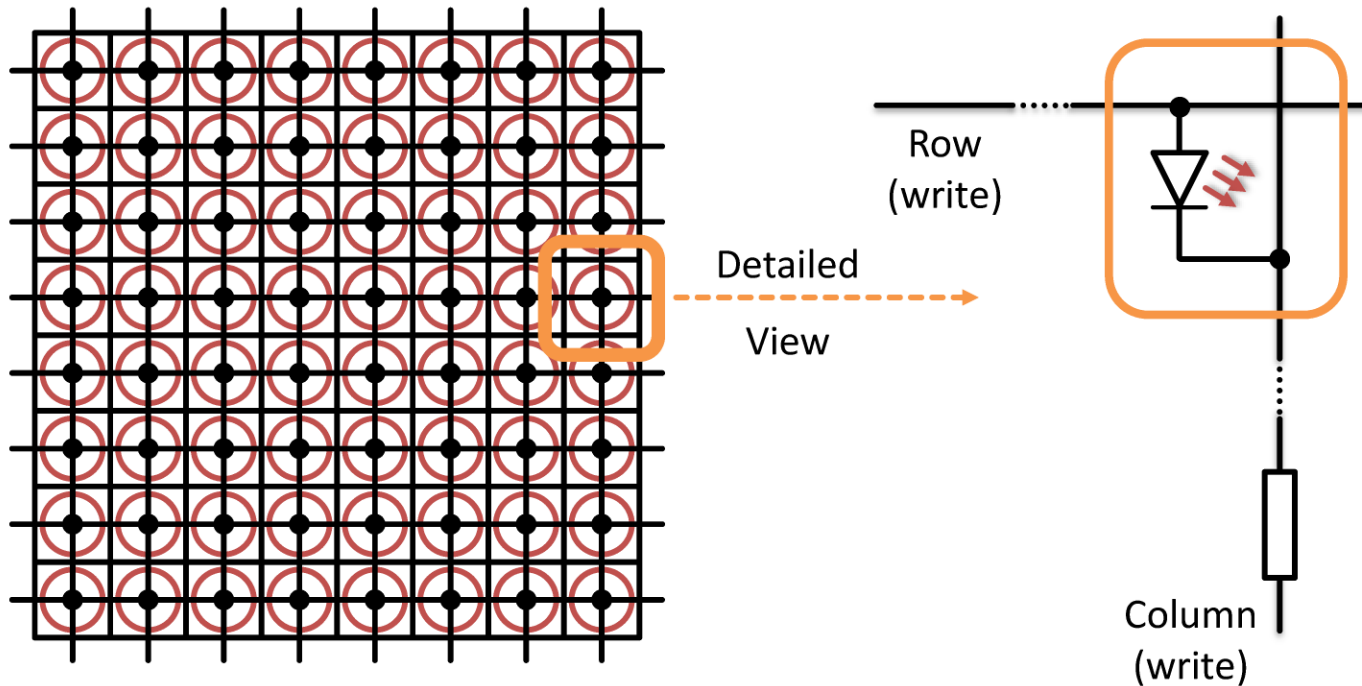


Dot-Matrix Displays (3)

- Dot-Matrix Controller

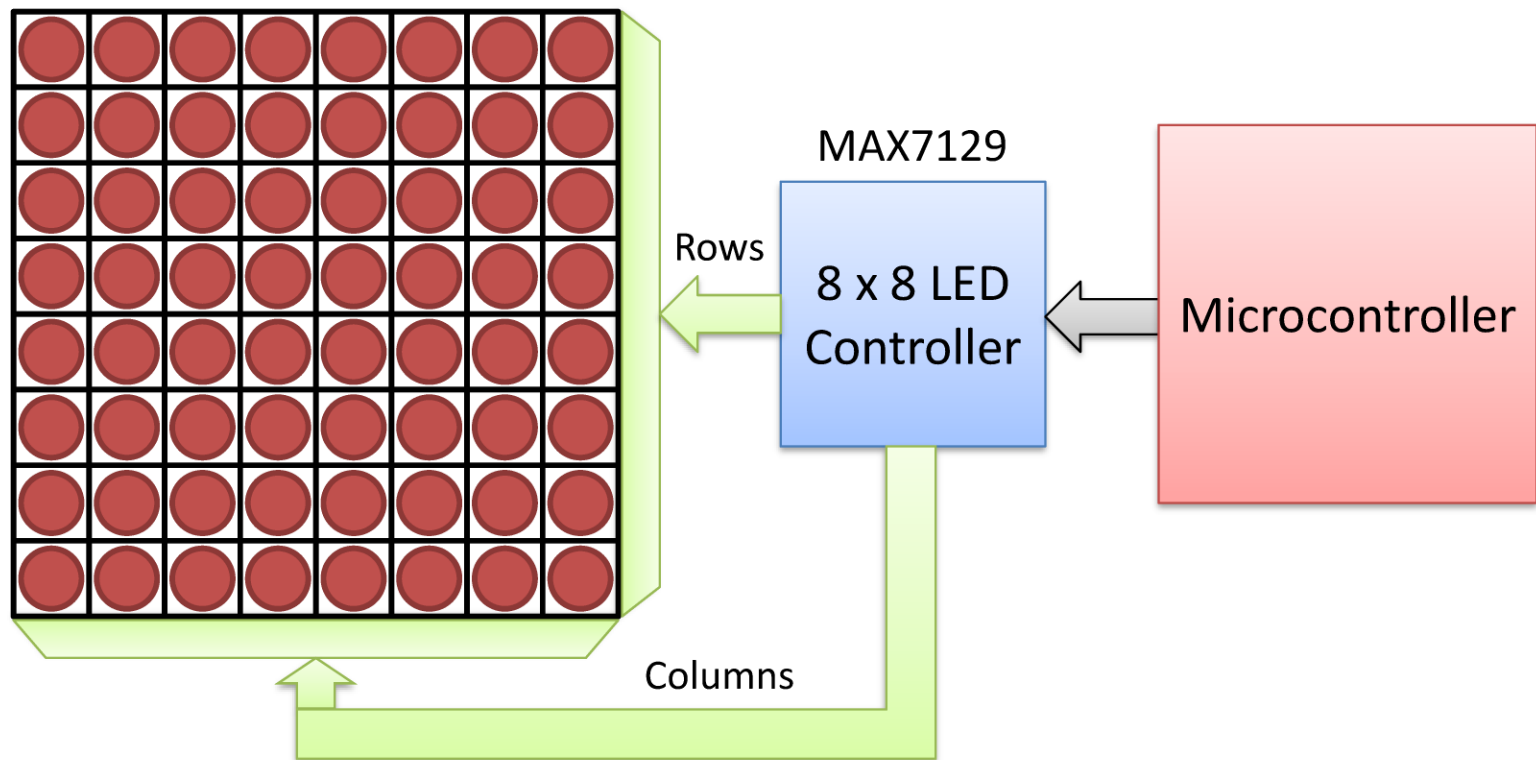

Liquid-Crystal Display (1)

- Functional Principle

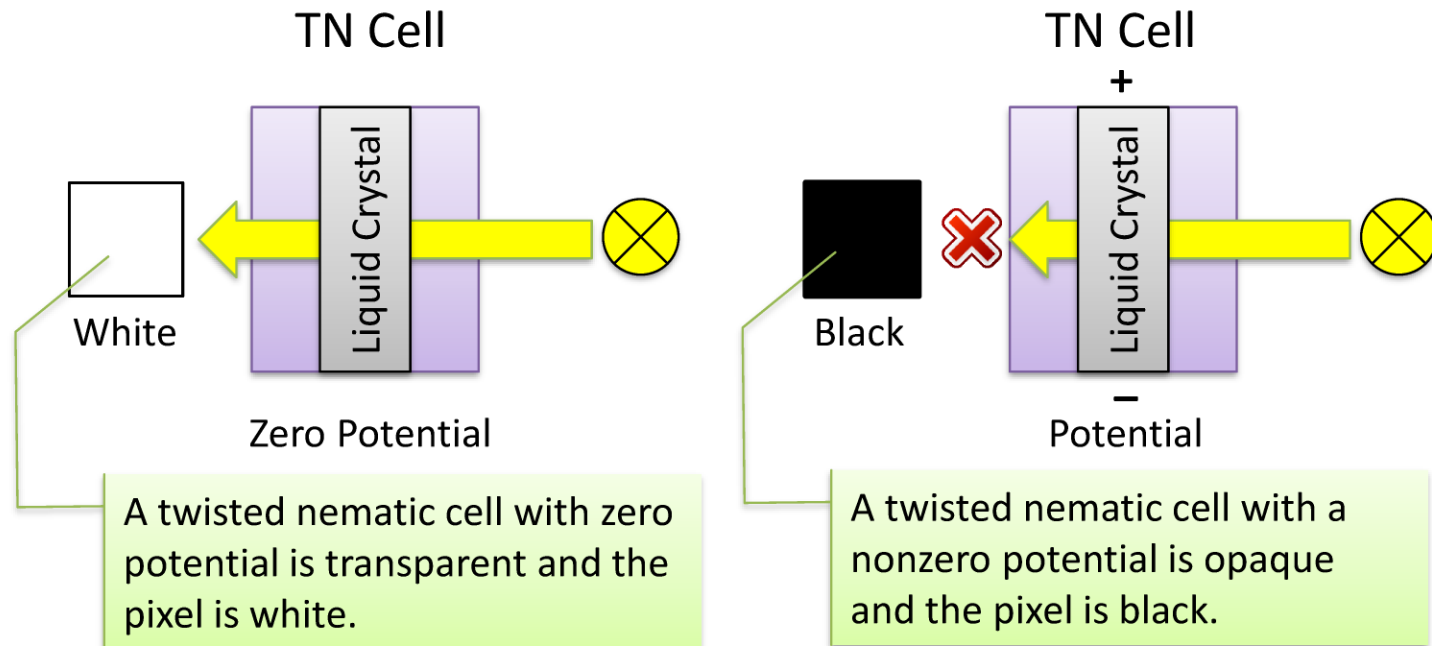

Liquid-Crystal Display (2)

- LCD Controller

