


# Counters

Digital Electronics

by Wolfgang Neff

 
# Counters (1)

- Count events
- Events are indicated by impulses


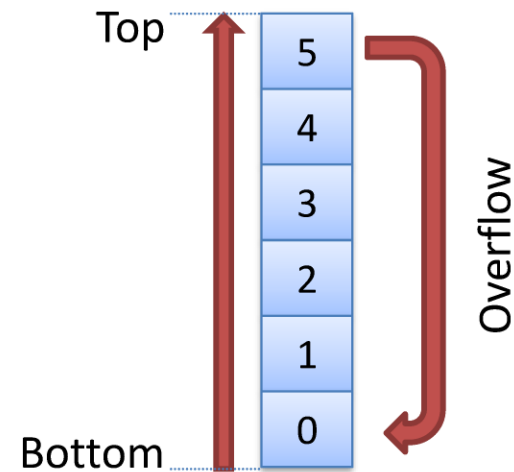
# Counters (2)

- Mod- $N$  counter
  - Counter have a range
    - 0 ...  $N-1$  (0 ... 5)
  - Counter overflow
    - $N-1 \rightarrow 0$  (0, 1, 2, 3, 4, 5, 0, 1, ...)
  - Modulo
    - Remainder of division
      - $5 \bmod 6 = 5$
      - $6 \bmod 6 = 0$
      - $7 \bmod 6 = 1$




# Counters (3)

- Features
  - Enable
    - Enables or disables clock
  - Reset
    - Resets counter value
  - Up/down
    - Changes the counting direction
      - Countdown


 
# Counters (4)


- Features *(continued)*
  - Overflow Indicator
    - Enables cascading *(see BCD)*
  - Preload
    - Sets a start value



Counter starts with provided start value. Reading is triggered by a load signal.


# BCD (1)

- Binary Coded Decimal

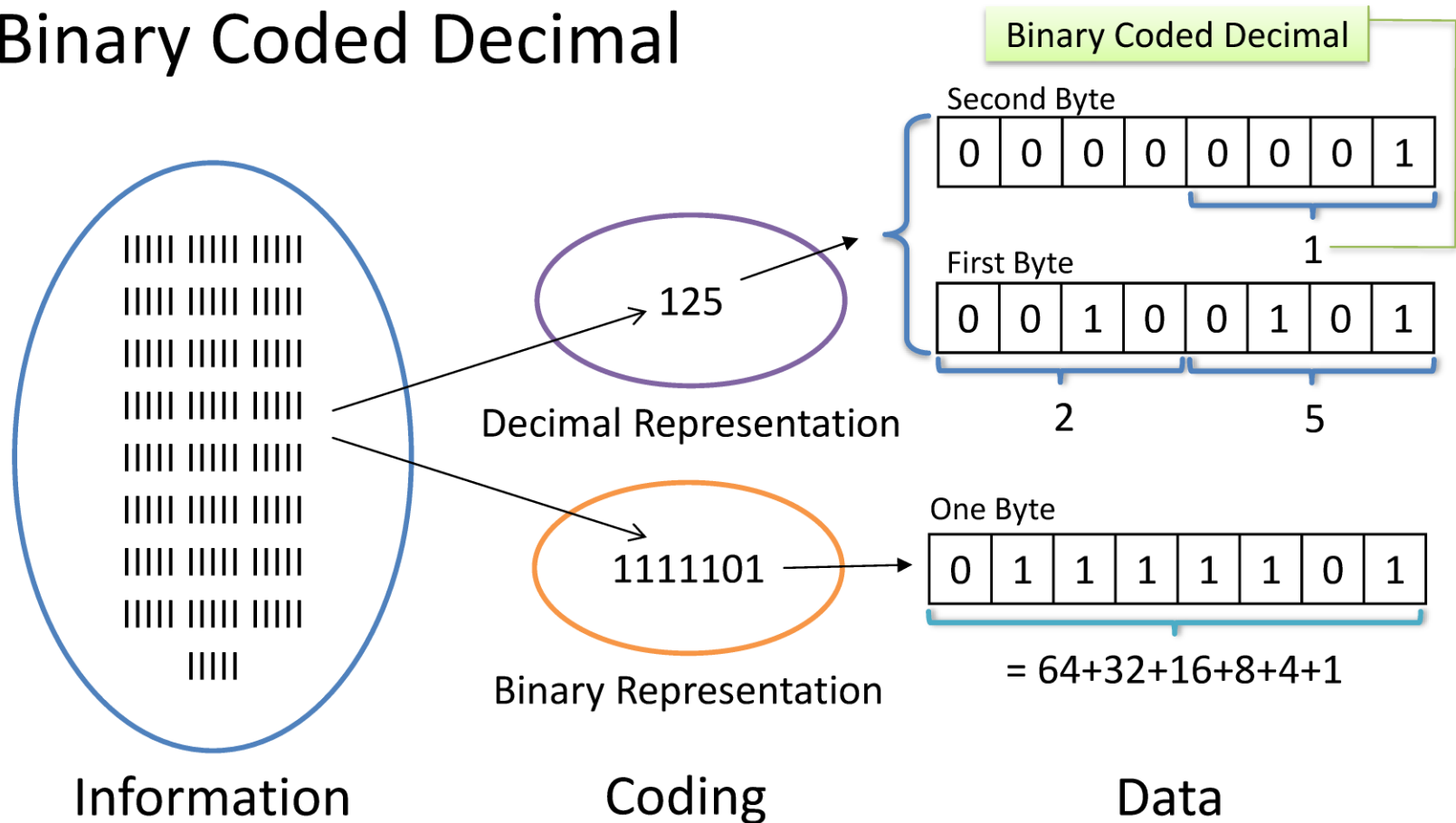

 
# BCD (2)

- BCD Counter (mod-10 counter)
- Position Cascading
  - Odometer (Mileage counter)



# Counters (5)

- 74193 – 4-bit binary up/down counter

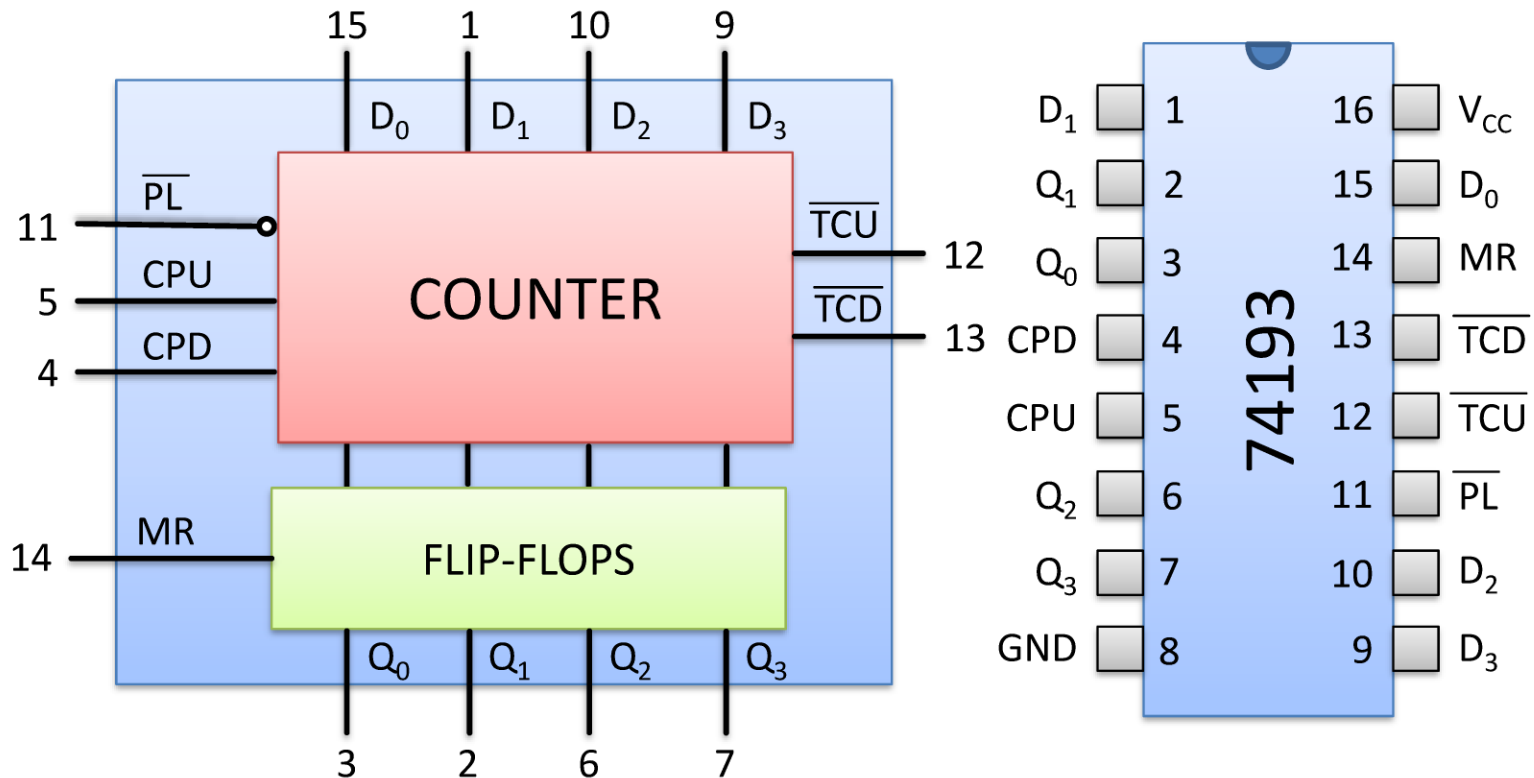




# Counters (6)

- 74193 – 4-bit binary up/down counter (continued)

Symbol	Pin	Description
$D_0, D_1, D_2, D_3$	15, 1, 10, 9	data input
$Q_0, Q_1, Q_2, Q_3$	3, 2, 6, 7	flip-flop output
CPD	4	count down clock input; L-to-H
CPU	5	count up clock input; L-to-H
GND	8	ground (0 V)
$\overline{\text{PL}}$	11	asynchronous parallel load input
$\overline{\text{TCU}}$	12	terminal count up (carry) output
TCD	13	terminal count down (carry) output
MR	14	asynchronous master reset input
$V_{\text{CC}}$	16	supply voltage

# Counters (7)

- 4516 – Binary up/down counter

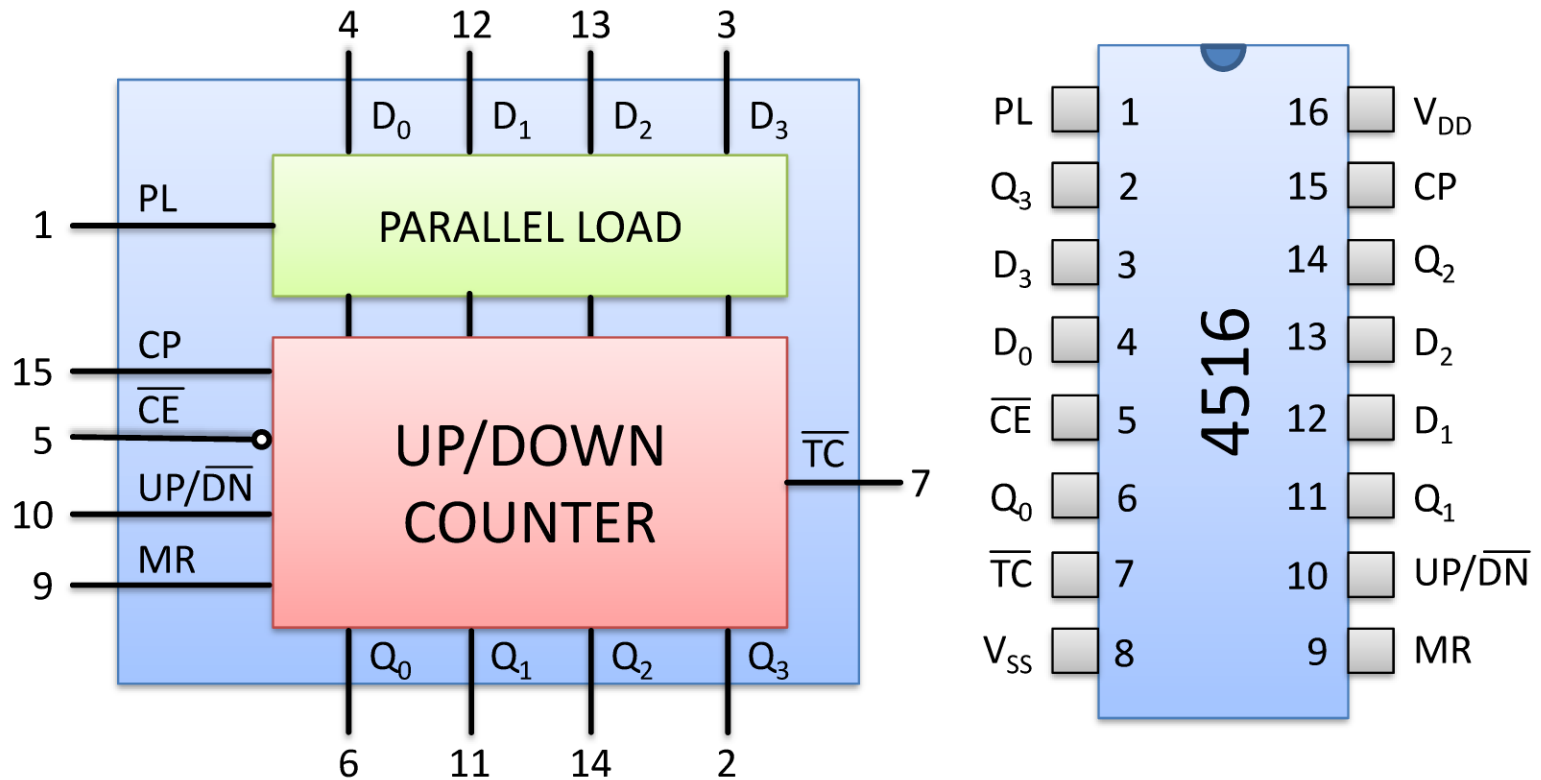

# Counters (8)

- 4516 – Binary up/down counter (continued)

Symbol	Pin	Description
PL	1	parallel load input
$D_0, D_1, D_2, D_3$	4, 12, 13, 3	parallel input
$\overline{CE}$	5	count enable input
$Q_0, Q_1, Q_2, Q_3$	6, 11, 14, 2	parallel output
$V_{SS}$	8	ground
$\overline{TC}$	7	terminal count output
MR	9	master reset input
UP/ $\overline{DN}$	10	up/down count control input
CP	15	clock pulse input
$V_{DD}$	16	supply voltage