

Operational Amplifiers

Scheme Outlines


Applied Mechatronics

Module 5.3.1

by Wolfgang Neff

Basics (1)

- Electronic Symbol

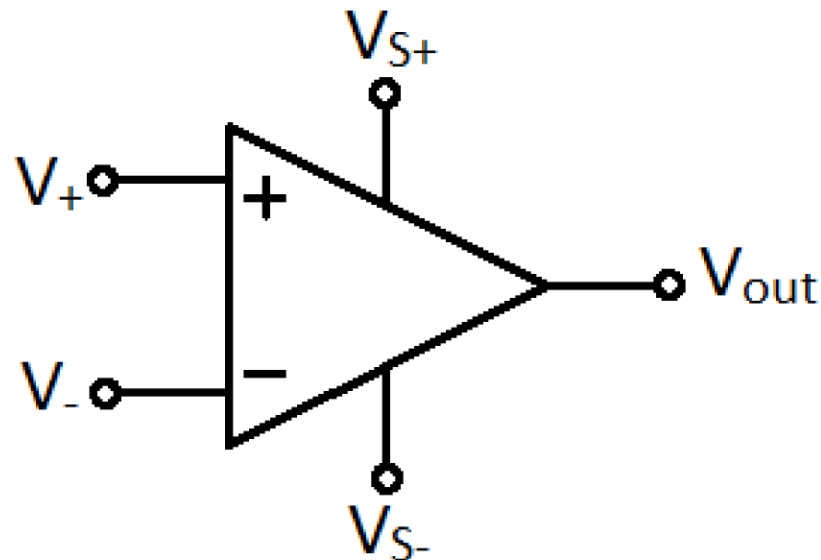


- V_+ : non-inverting input
- V_- : inverting input
- V_{out} : output
- V_{S+} : positive power supply
- V_{S-} : negative power supply

Basics (2)

- Terms


- Open-Loop

- Circuit without feedback

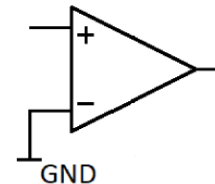

- Closed-Loop

- Circuit with feedback

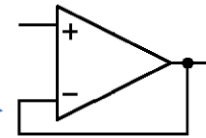

- Differential Input Voltage

- $V_d = V_+ - V_-$

- Gain of the Amplifier

- $A = \frac{V_{out}}{V_d}$

Basics (3)


- Characteristics (Ideal Op-Amp)
 - Open-Loop Gain
 - $A_{OL} \rightarrow \infty$
 - Closed-Loop Differential Voltage Input
 - $V_d = 0 \text{ V}$
 - Input Resistance
 - $R_{in} \rightarrow \infty$
 - Zero Input Current
 - $I_+ = 0 \text{ A}, I_- = 0 \text{ A}$

Basics (4)


- Characteristics (continued)
 - Output Resistance
 - $R_{out} = 0 \Omega$
 - Any load can be driven
 - Output Voltage
 - $V_{out} = \begin{cases} V_{S+}, & V_+ > V_- \\ V_{S-}, & V_+ < V_- \end{cases}$

Basics (5)

- Example: LM741

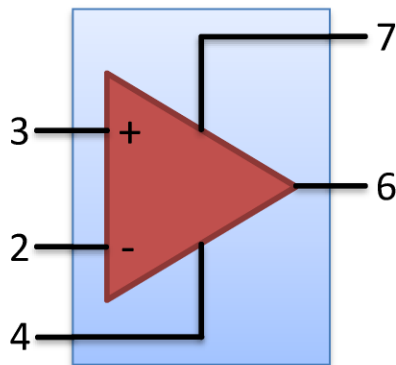

Block Diagram

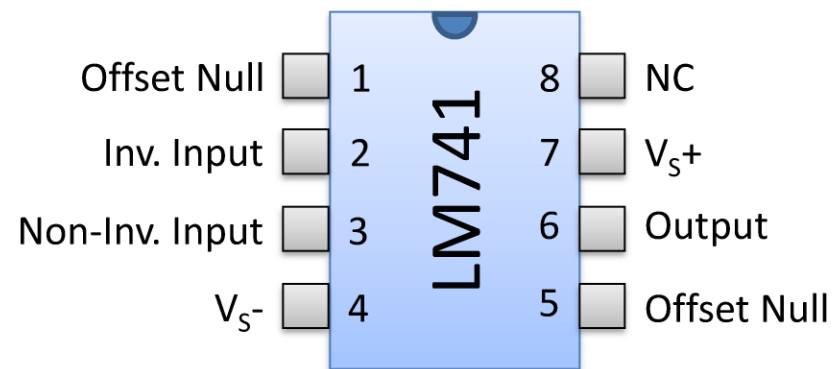

Pin Configuration

Voltage Comparator (1)

- Setup and Mode of Operation

Cf. NWES
Module 4.2.6


- Compares two Voltages

- V_{ref} : reference voltage
- V_{in} : probed voltage

- Output

- Logic Levels
 - $V_{CC} = 1, GND = 0$

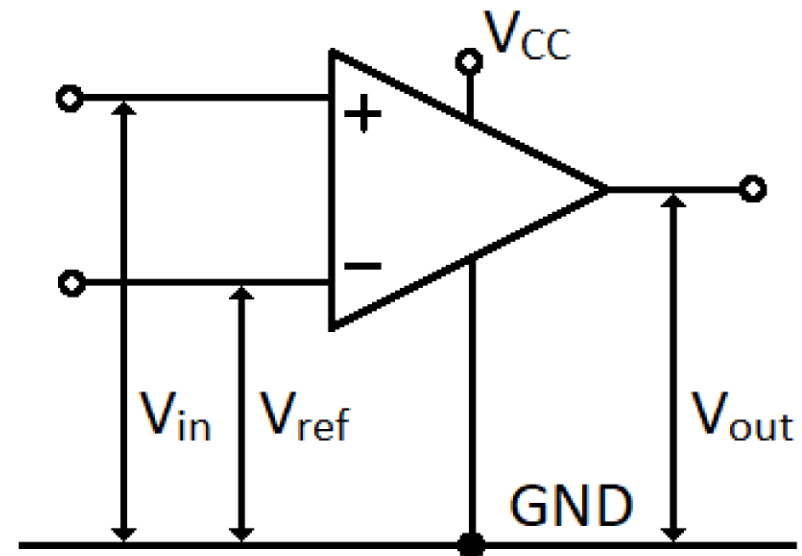- $$V_{out} = \begin{cases} 1, & V_{in} > V_{ref} \\ 0, & V_{in} < V_{ref} \end{cases}$$



Impedance Converter (1)


- Setup and Mode of Operation

- Basic Equations

- $V_d = V_+ - V_-$
 - $V_+ = V_{in}, V_- = V_{out}$

- Closed Loop

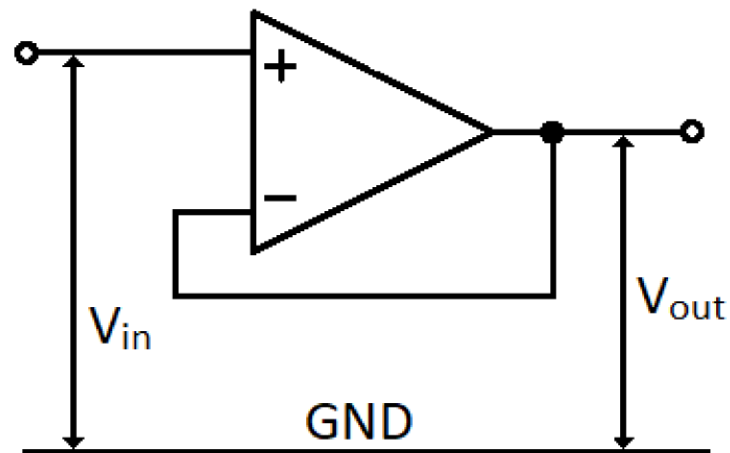- $V_d = 0\text{ V}$
 - $V_{out} = V_{in}$



Impedance Converter (2)

- Implications
 - Input and output voltage are equal
 - High input resistance
 - Low output resistance
- Application
 - Reduce internal resistance of power sources
 - Usually desired: $R_{\text{int}} \ll R_{\text{load}}$
 - Cf. [SEY14] Ch. 2.16: Innenwiderstand von Span.

Non-Inverting Amplifier (1)

- Setup and Mode of Operation

- Basic Equations

- $V_{out} = A_{CL} \cdot V_{in}$


- $A_{CL} = 1 + \frac{R_2}{R_1}$

- Implication

- Max amplification is 1

- Application

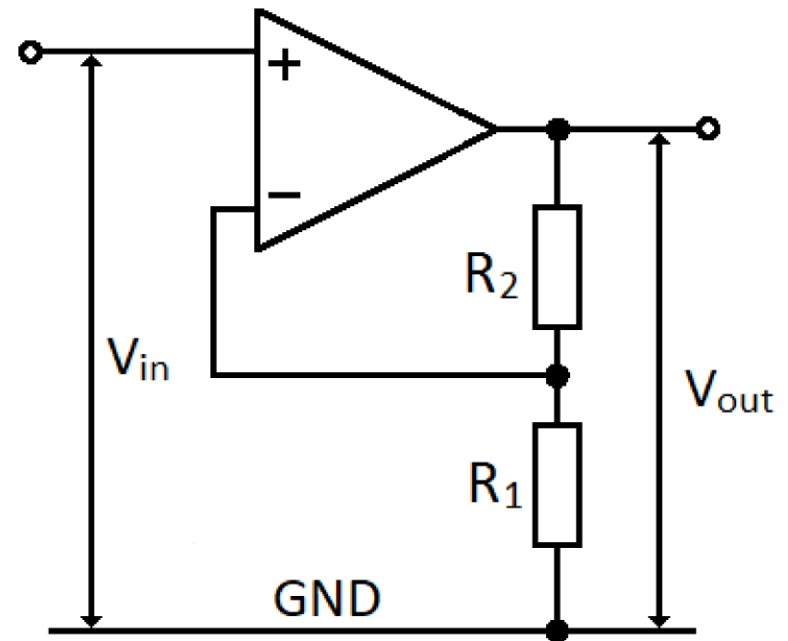- Control theory
 - Proportional controller



Inverting Amplifier (1)

- Setup and Mode of Operation


- Basic Equations

- $V_{out} = -A_{CL} \cdot V_{in}$

- $A_{CL} = \frac{R_2}{R_1}$

- Implications

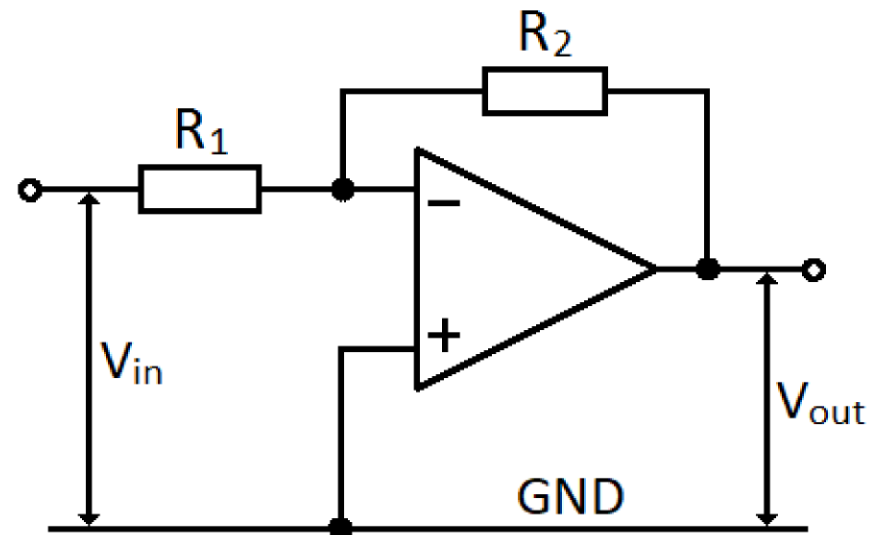- Input and Output have opposite sign.
- Amplification is adjustable at will.



Differential Amplifier (1)

- Setup and Mode of Operation


- Basic Equations

- $V_{out} = A_{CL} \cdot (V_{in+} - V_{in-})$

- $A_{CL} = \frac{R_2}{R_1}$

- Application

- Control theory
 - Comparing element

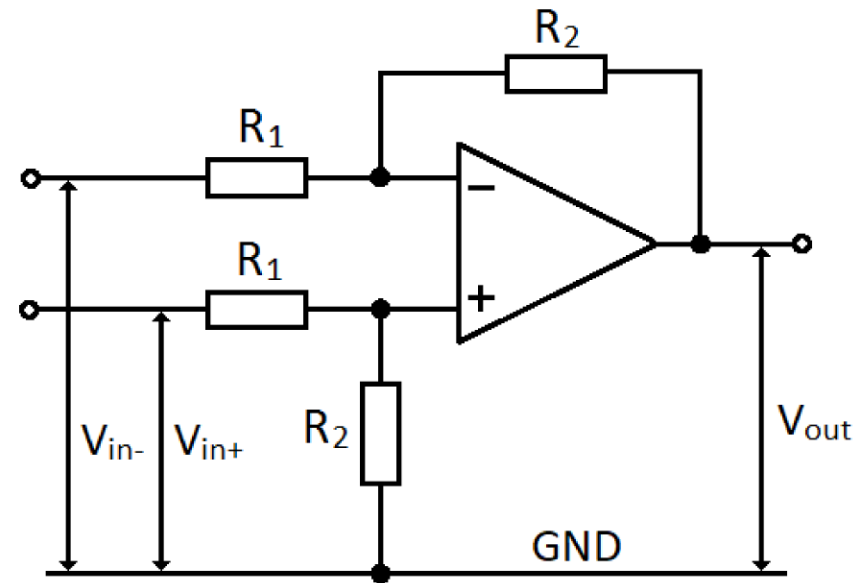

Schmitt Trigger (1)


- Setup (inverting)

- Terms

- V_{thr} : Threshold voltage
 - V_{HT} : High threshold
 - V_{LT} : Low threshold
 - Hysteresis: see below

- Applications


- Cf. NWES module 3.4.7

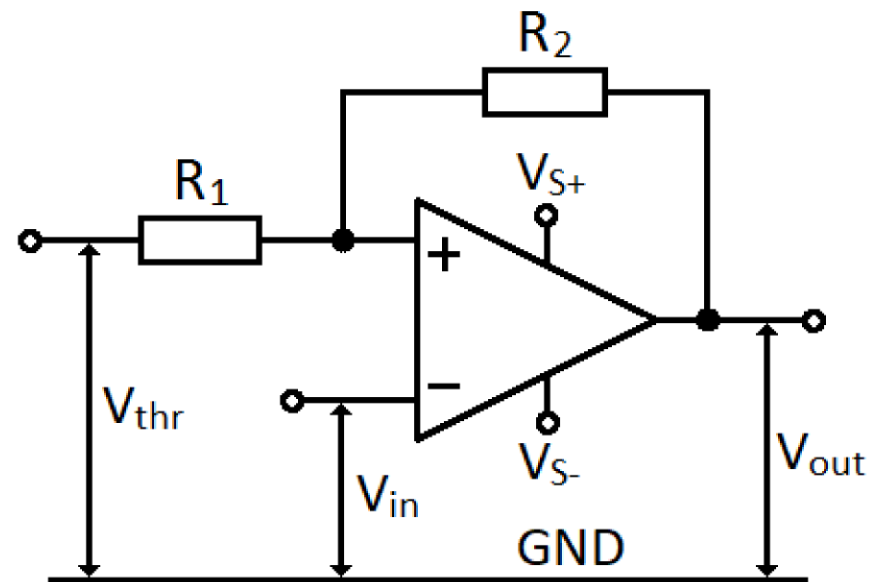

Schmitt Trigger (2)

- Mode of Operation

- Hysteresis

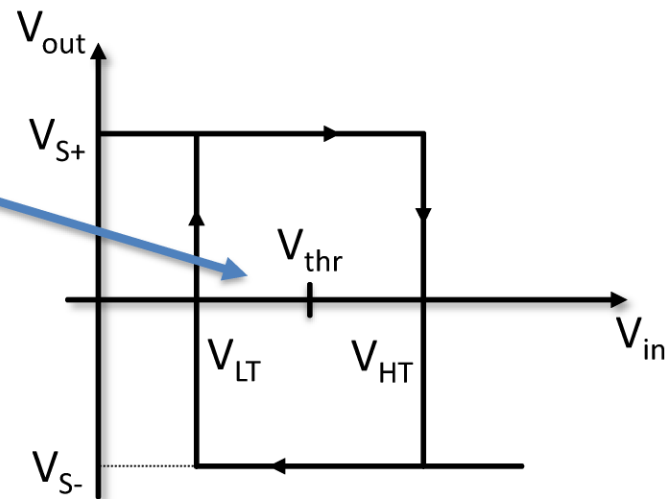


- Basic Equations

- $V_{HT} = V_{thr} + \frac{R_1}{R_1 + R_2} \cdot (V_{S+} - V_{thr})$

- $V_{LT} = V_{thr} + \frac{R_1}{R_1 + R_2} \cdot (V_{S-} - V_{thr})$

Schmitt Trigger (3)

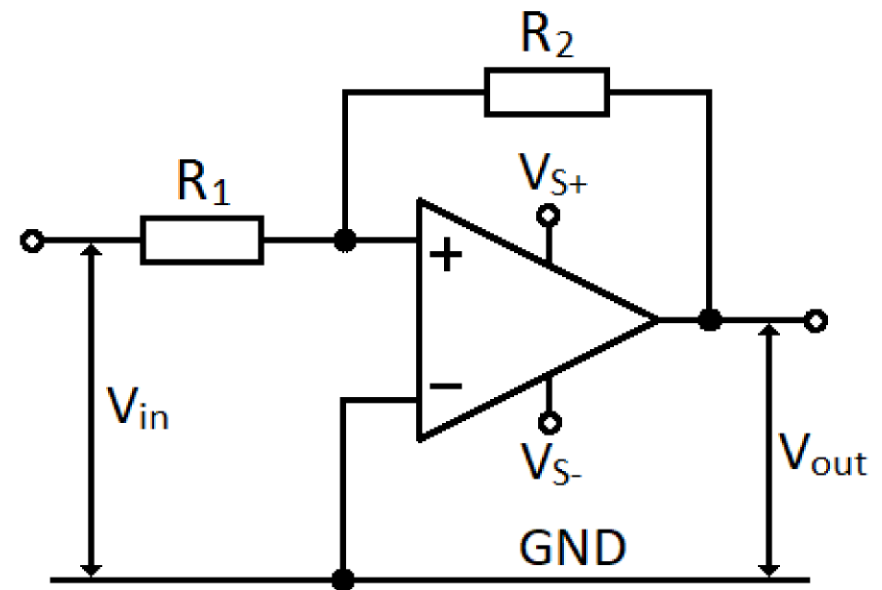- Setup (non-inverting)
 - Cf. [BRI13] Ch. 3.2.7
 - Basic Equations
 - $V_{HT} = -\frac{R_1}{R_2} \cdot V_{S+}$
 - $V_{LT} = -\frac{R_1}{R_2} \cdot V_{S-}$



Differentiator (1)

- Setup


- Basic Equations

- $V_{out} = -R \cdot C \cdot \frac{\Delta V_{in}}{\Delta t}$

Difference Quotient

- $v_{out}(t) = -R \cdot C \cdot \frac{dv_{in}(t)}{dt} = -\tau \cdot \dot{v}_{in}(t)$

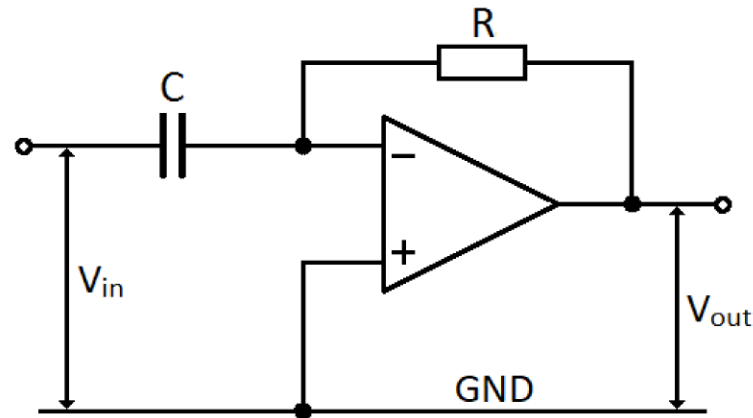Time Constant τ
Cf. [SEY14] Ch. 5.7
Kondensator an Gleichspannung



Differentiator (2)


- Mode of Operation

- Differential  AM V

- Slope of the tangent line of a function at a point

- Application

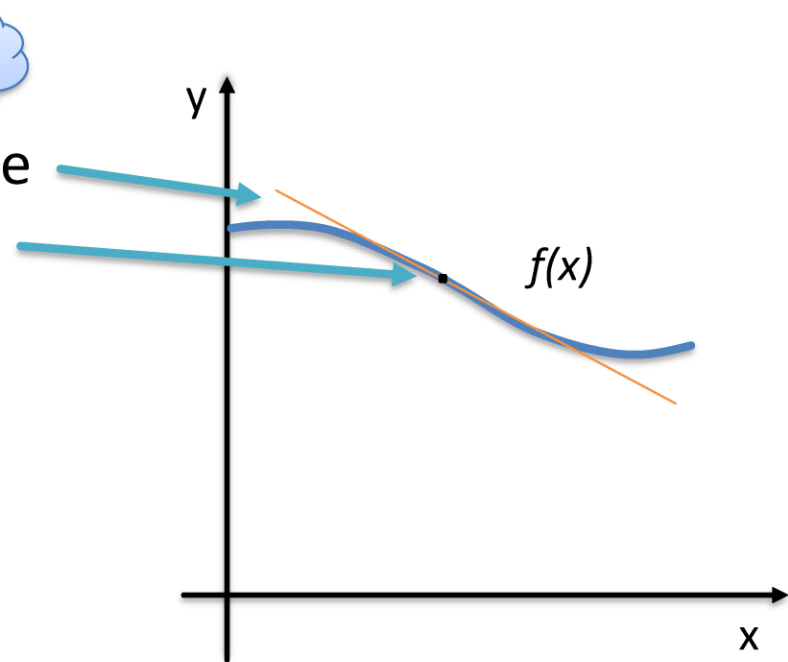- Control theory
 - Derivative controller



Integrator (1)

- Setup


- Basic Equations

- $\Delta V_{out} = -\frac{1}{R \cdot C} \cdot V_{in} \cdot \Delta t$

Riemann Summand

Integral

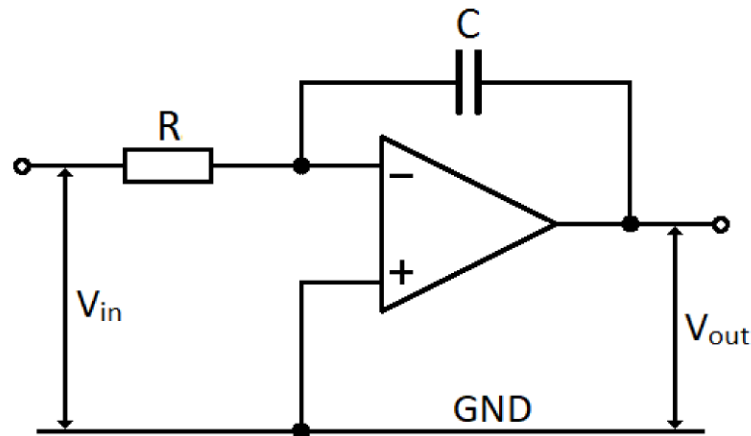- $v_{out}(t) = -\frac{1}{R \cdot C} \cdot \int_0^t v_{in}(t) dt + v_{out}(0)$



Integrator (2)

- Mode of Operation


- Integral

AM VI

- Area of a region bounded by a function graph

- Application

- Control theory
 - Integral controller

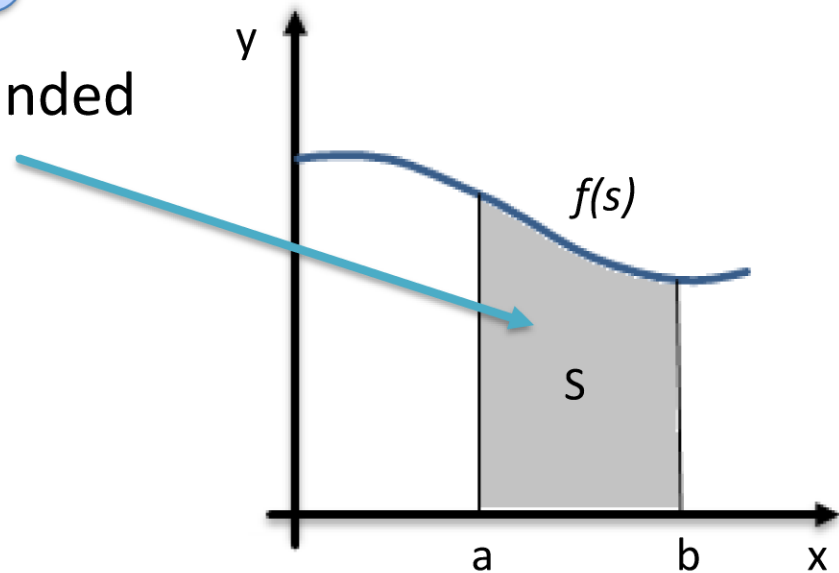

Addendum

- Further Information
 - [BRI13] Ch. 3.2.7 Operationsverstärker

Bibliography

- [SEY14]: SEYR, SIGURD and SCHWAIGER, HERBERT, 2014, Elektrotechnik Grundlagen mit angewandter Mathematik. Wien : Jugend & Volk. ISBN 978-3-7100-2873-1.
- [BRI13]: BRIEGLER, ADOLF and others, 2013, Elektrotechnik Fachkunde 1. Wien : Jugend & Volk. ISBN 978-3-7100-2911-0.