

# Operational Amplifiers

## Dimensioning

Applied Mechatronics

Module 5.3.2


by Wolfgang Neff

# Non-Inverting Amplifier (1)

- Derivation of the Basic Equations

- Known Quantities

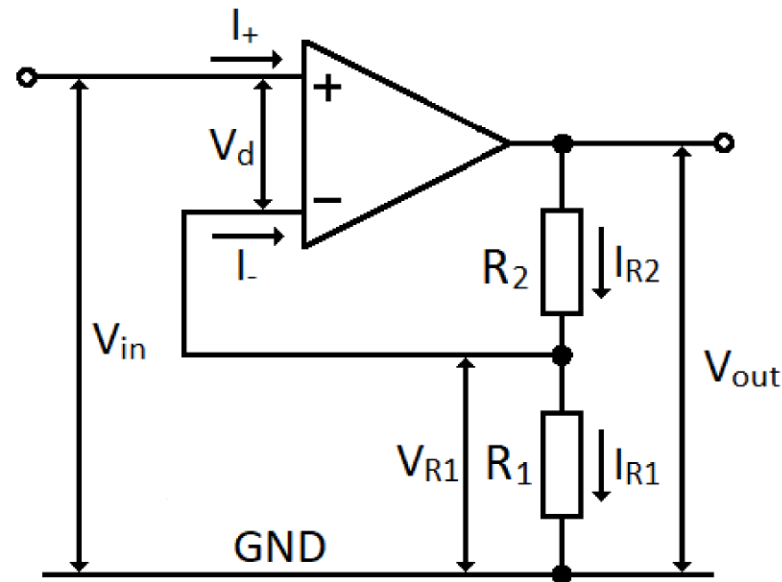- $V_d = 0 \text{ V}$
- $I_+ = 0 \text{ A}$
- $I_- = 0 \text{ A}$
- $V_+ = V_{in}$
- $V_- = V_{in}$
- $V_{R1} = V_{in}$
- $I_{R1} = I_{R2} = I_R$



Cf. [SEY14] Ch. 2.11  
Reihenschaltung von W.

# Non-Inverting Amplifier (2)

- Derivation of the Basic Equations (continued)

- Derivation

- $I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_{in}}{R_1}$

- $I_R = \frac{V_{out}}{R_1 + R_2}$

- $\frac{V_{in}}{R_1} = \frac{V_{out}}{R_1 + R_2} \rightarrow V_{out} = \frac{R_1 + R_2}{R_1} V_{in} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$

- $V_{out} = A_{CL} \cdot V_{in}$


- $A_{CL} = 1 + \frac{R_2}{R_1}$

# Inverting Amplifier (1)

- Derivation of the Basic Equations

- Known Quantities

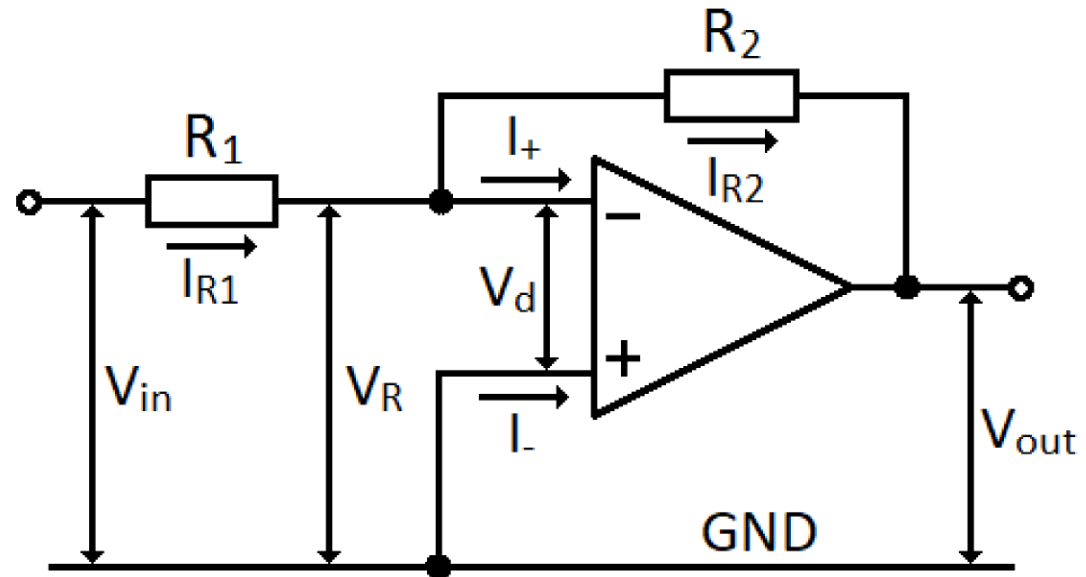- $V_d = 0 \text{ V}$
- $I_+ = 0 \text{ A}$
- $I_- = 0 \text{ A}$
- $V_+ = 0 \text{ V}$
- $V_- = 0 \text{ V}$
- $V_R = 0 \text{ V}$
- $I_{R1} = I_{R2}$



# Inverting Amplifier (2)

- Derivation of the Basic Equations (continued)

- Derivation

- $I_{R_1} = \frac{V_{in} - V_R}{R_1} = \frac{V_{in}}{R_1}$

- $I_{R_2} = \frac{V_R - V_{out}}{R_2} = \frac{-V_{out}}{R_2}$

- $\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2} \rightarrow V_{out} = -\frac{R_2}{R_1} V_{in}$

- $V_{out} = -A_{CL} \cdot V_{in}$


- $A_{CL} = \frac{R_2}{R_1}$

# Differential Amplifier (1)

- Derivation of the Basic Equations

- Known Quantities

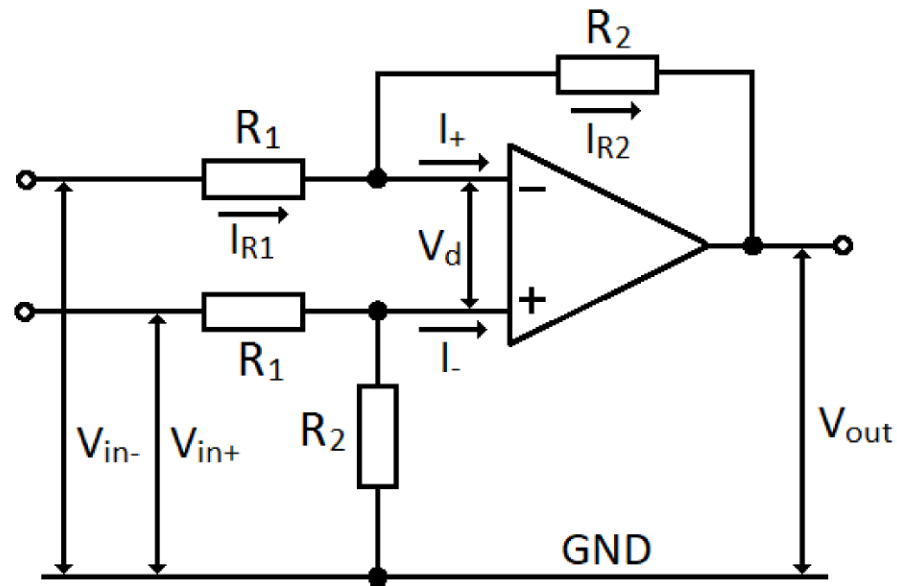- $V_d = 0 \text{ V}$
- $I_+ = 0 \text{ A}$
- $I_- = 0 \text{ A}$
- $V_- = V_+$
- $I_{R1} = I_{R2}$



# Differential Amplifier (2)

- Derivation of the Basic Equations (continued)
  - Derivation

Cf. [SEY14] Ch. 2.11 p. 36  
Spannungsteiler

- $V_+ = \frac{R_2}{R_1 + R_2} V_{in+}$

- $I_{R_1} = \frac{V_{in-} - V_+}{R_1}; I_{R_2} = \frac{V_+ - V_{out}}{R_2}$

- $\frac{V_{in-} - V_+}{R_1} = \frac{V_+ - V_{out}}{R_2} \rightarrow \frac{R_2}{R_1} (V_{in-} - V_+) = V_+ - V_{out}$

- $V_{out} = V_+ - \frac{R_2}{R_1} (V_{in-} - V_+) = V_+ + \frac{R_2}{R_1} V_+ - \frac{R_2}{R_1} V_{in-}$

- $V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_+ - \frac{R_2}{R_1} V_{in-}$

# Differential Amplifier (3)

- Derivation of the Basic Equations (finished)

- Derivation

- $$V_{out} = \left(1 + \frac{R_2}{R_1}\right) \frac{R_2}{R_1 + R_2} V_{in+} - \frac{R_2}{R_1} V_{in-}$$

- $$V_{out} = \frac{R_1 + R_2}{R_1} \frac{R_2}{R_1 + R_2} V_{in+} - \frac{R_2}{R_1} V_{in-}$$

- $$V_{out} = \frac{R_2}{R_1} V_{in+} - \frac{R_2}{R_1} V_{in-} = \frac{R_2}{R_1} (V_{in+} - V_{in-})$$

- $$V_{out} = A_{CL} (V_{in+} - V_{in-})$$

- $$A_{CL} = \frac{R_2}{R_1}$$




# Schmitt Trigger (1)

- Derivation of the Basic Equations

- Known Quantities

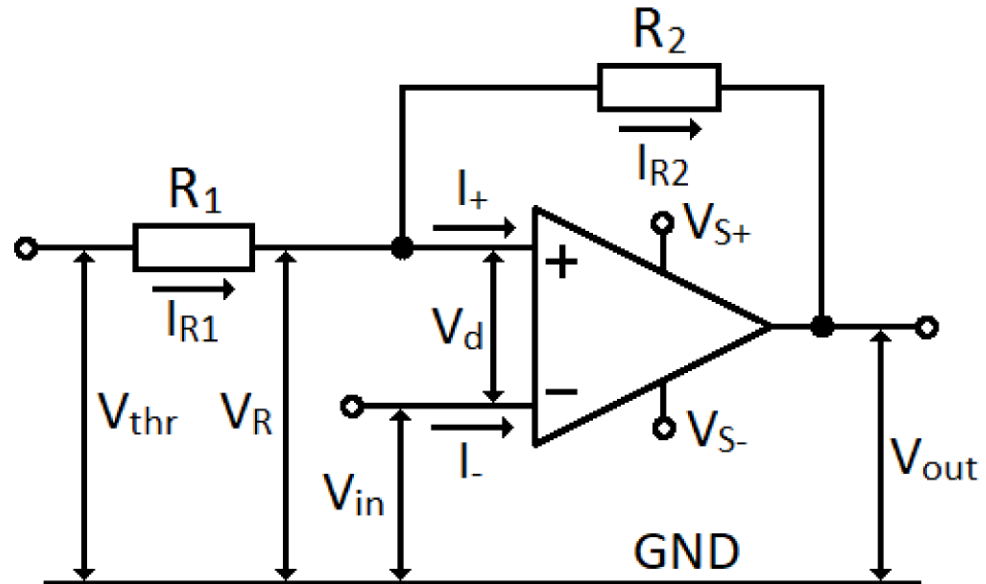- $V_d = 0 \text{ V}$
- $I_+ = 0 \text{ A}$
- $I_- = 0 \text{ A}$
- $V_R = V_{in}$
- $I_{R1} = I_{R2} = I_R$



# Schmitt Trigger (2)

- Derivation of the Basic Equations (continued)

- Derivation

- $I_{R_1} = \frac{V_{thr} - V_R}{R_1}$ ;  $I_R = \frac{V_{thr} - V_{out}}{R_1 + R_2}$

- $\frac{V_{thr} - V_{in}}{R_1} = \frac{V_{thr} - V_{out}}{R_1 + R_2}$

- Case 1:

- $V_{in} = V_{HT} \rightarrow V_{out} = V_{S+}$

- $\frac{V_{thr} - V_{HT}}{R_1} = \frac{V_{thr} - V_{S+}}{R_1 + R_2} \rightarrow V_{HT} = V_{thr} - \frac{R_1}{R_1 + R_2} (V_{thr} - V_{S+})$

- $V_{HT} = V_{thr} + \frac{R_1}{R_1 + R_2} (V_{S+} - V_{thr})$

# Schmitt Trigger (3)

- Derivation of the Basic Equations (finished)

- Derivation

- Case 2:

- $V_{in} = V_{LT} \rightarrow V_{out} = V_{S-}$

- $V_{HT} \rightarrow V_{LT}; V_{S+} \rightarrow V_{S-}$


- $V_{LT} = V_{thr} + \frac{R_1}{R_1+R_2} (V_{S-} - V_{thr})$

# Integrator (1)

- Derivation of the Basic Equations

- Known Quantities

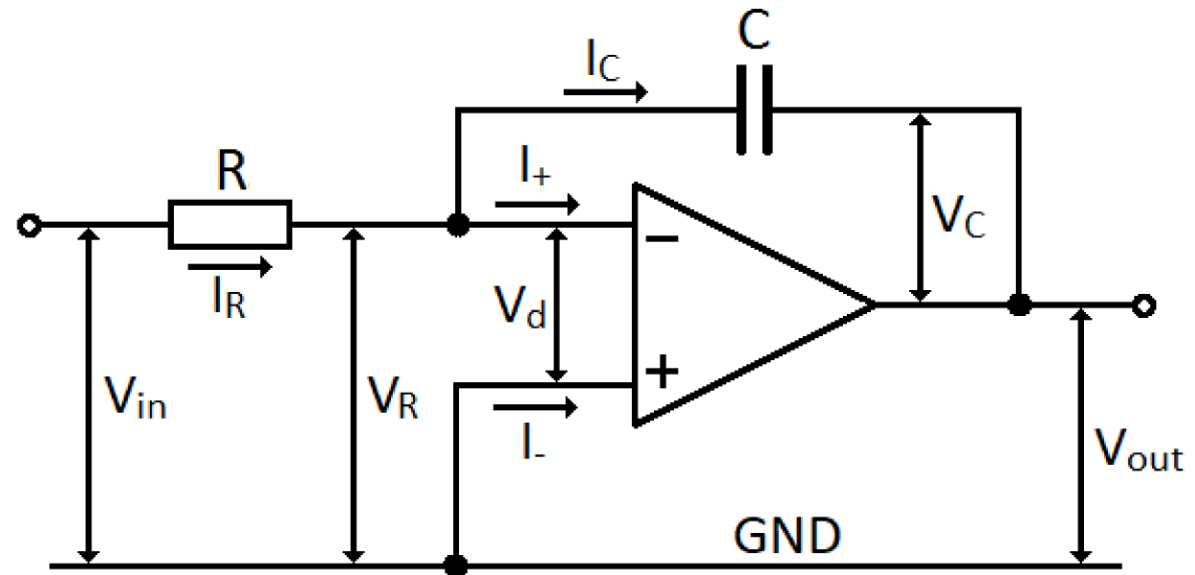- $V_d = 0 \text{ V}$
- $I_+ = 0 \text{ A}$
- $I_- = 0 \text{ A}$
- $V_R = 0 \text{ V}$
- $I_C = I_R$



# Integrator (2)

- Derivation of the Basic Equations (continued)

- Fundamentals

- $Q = I \cdot t$

Cf. [SEY14] Ch. 5.1  
Elektrische Ladung

- $V = \frac{Q}{C}$

Cf. [SEY14] Ch. 5.7  
Kondensator an Gleichsp.

- Derivation

- $\Delta Q = I_R \cdot \Delta t$

- $Q = Q_0 + \Delta Q$

- $I_R = \frac{V_{in}}{R}$

# Integrator (3)

- Derivation of the Basic Equations (finished)

- Derivation

- $V_C = \frac{Q}{C} = \frac{Q_0 + \Delta Q}{C} = \frac{Q_0}{C} + \frac{I_R \cdot \Delta t}{C} = V_{C_0} + \frac{V_{in}}{R \cdot C} \cdot \Delta t$

- $V_C = V_R - V_{out} = -V_{out}$

- $-V_{out} = V_{C_0} + \frac{V_{in}}{R \cdot C} \cdot \Delta t \rightarrow V_{out} - V_{out_0} = -\frac{1}{R \cdot C} V_{in} \cdot \Delta t$

- $\Delta V_{out} = -\frac{1}{R \cdot C} V_{in} \cdot \Delta t$

$V_{in}$  depends on time  $\rightarrow$   
Integral calculus needed


- $v_{out}(t) = -\frac{1}{R \cdot C} \cdot \int_0^t v_{in}(t) dt + v_{out}(0)$

# Differentiator (1)

- Derivation of the Basic Equations

- Known Quantities

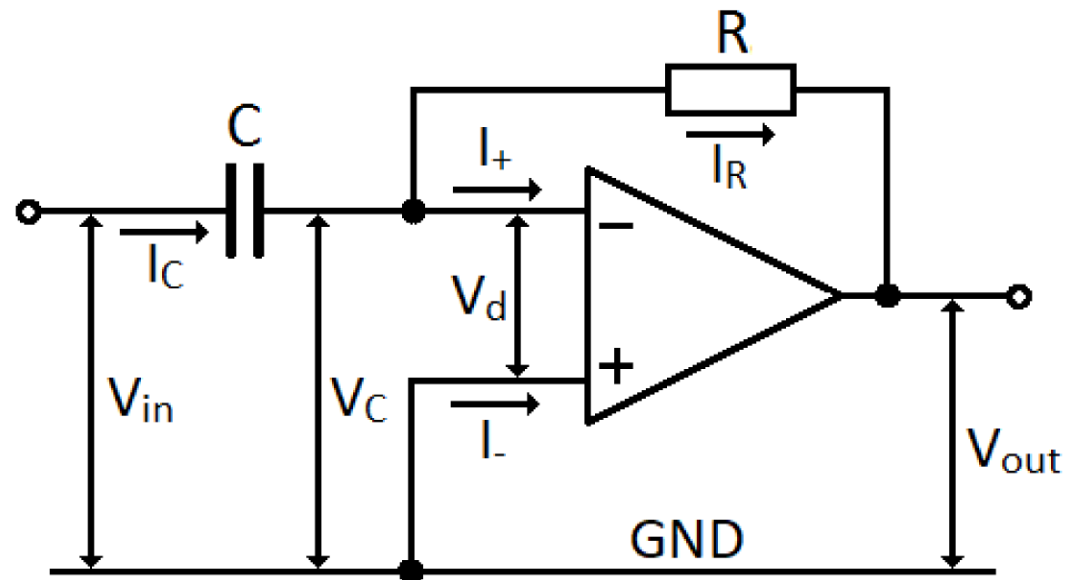- $V_d = 0 \text{ V}$
- $I_+ = 0 \text{ A}$
- $I_- = 0 \text{ A}$
- $V_C = 0 \text{ V}$
- $I_C = I_R$



# Differentiator (2)

- Derivation of the Basic Equations (continued)

- Derivation

- $\Delta V_{in} = \frac{\Delta Q}{C} \rightarrow \Delta Q = C \cdot \Delta V_{in}$

- $\Delta Q = I_C \cdot \Delta t \rightarrow I_C = \frac{\Delta Q}{\Delta t}$

- $I_C = I_R = \frac{V_C - V_{out}}{R} = -\frac{V_{out}}{R} \rightarrow -\frac{V_{out}}{R} = \frac{C \cdot \Delta V_{in}}{\Delta t}$

- $V_{out} = -R \cdot C \cdot \frac{\Delta V_{in}}{\Delta t}$

- $v_{out}(t) = -R \cdot C \cdot \frac{dv_{in}(t)}{dt}$

$V_{in}$  depends on time  $\rightarrow$   
Differential calculus needed



# Bibliography

- [SEY14]: SEYR, SIGURD and SCHWAIGER, HERBERT, 2014, Elektrotechnik Grundlagen mit angewandter Mathematik. Wien : Jugend & Volk. ISBN 978-3-7100-2873-1.
- [BRI13]: BRIEGLER, ADOLF and others, 2013, Elektrotechnik Fachkunde 1. Wien : Jugend & Volk. ISBN 978-3-7100-2911-0.