

Noninverting Amplifiers

Please do the following exercises individually.

Example

A sensor produces a measuring signal between 0 V and 10 mV. The amplified signal must not exceed 1 V. Please choose adequate resistors taken from the E12-series: 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820. What is the real output?

Exercise 1

An operational amplifier increases an input voltage of 5 mV to 1 V. Please determine the amplification factor.

Exercise 2

An operational amplifier has a 15 k Ω grounding resistor R_1 and a 120 k Ω series resistor R_2 . Please determine the amplification factor.

Exercise 3

The input voltage of an operational amplifier with $R_1 = 10$ k Ω and $R_2 = 100$ k Ω is 1.5 V. Please determine the output voltage.

Exercise 4

A non-inverting amplifier has an amplification factor of 250. The grounding resistor R_1 is 8.2 k Ω . Please determine the resistance of the series resistor R_2 .

Exercise 5

The output voltage of an op amp must not be above 5 V. Please determine the maximum input voltage if $R_1 = 12$ k Ω and $R_2 = 320$ k Ω .

Noninverting Amplifiers

Please do the following exercises individually.

Example

A sensor produces a measuring signal between 0 V and 10 mV. The amplified signal must not exceed 1 V. Please choose adequate resistors taken from the E12-series: 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820. What is the real output?

Known Quantities: $V_{in} = 10 \text{ mV}$, $V_{out} = 1 \text{ V}$

Assumption: $R_1 = 10 \text{ k}\Omega$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{1 \text{ V}}{0.01 \text{ V}} = 100$$

$$A_{CL} = 1 + \frac{R_2}{R_1} \rightarrow R_2 = (A_{CL} - 1)R_1 = 99 \cdot R_1 = 990 \text{ k}\Omega \xrightarrow{E12} 820 \text{ k}\Omega \rightarrow A_{CLE12} = 1 + \frac{R_2}{R_1} = 82$$

$$V_{out} = A_{CL} \cdot V_{in} = 82 \cdot 10 \text{ mV} = 820 \text{ mV}$$

Exercise 1

An operational amplifier increases an input voltage of 5 mV to 1 V. Please determine the amplification factor.

$$A_{CL} = 200$$

Exercise 2

An operational amplifier has a 15 k Ω grounding resistor R_1 and a 120 k Ω series resistor R_2 . Please determine the amplification factor.

$$A_{CL} = 9$$

Exercise 3

The input voltage of an operational amplifier with $R_1 = 10 \text{ k}\Omega$ and $R_2 = 100 \text{ k}\Omega$ is 1.5 V. Please determine the output voltage.

$$V_{out} = 16.5 \text{ V}$$

Exercise 4

A non-inverting amplifier has an amplification factor of 250. The grounding resistor R_1 is 8.2 k Ω . Please determine the resistance of the series resistor R_2 .

$$R_2 = 2 \text{ M}\Omega$$

Exercise 5

The output voltage of an op amp must not be above 5 V. Please determine the maximum input voltage if $R_1 = 12 \text{ k}\Omega$ and $R_2 = 320 \text{ k}\Omega$.

V_{in} must not exceed 180 mV.

Inverting Amplifiers

Please do the following exercises individually.

Example

An operational amplifier has an output range from -12 V to +12 V. You want to measure an alternating current with a voltage of 140 mV. The input resistor R_1 has 4.7 k Ω . Please determine the resistance of the feedback resistor R_2 .

Exercise 1

An operational amplifier increases an input voltage of 5 mV to -1 V. Please determine the amplification factor.

Exercise 2

An operational amplifier has a 15 k Ω input resistor R_1 and a 120 k Ω feedback resistor R_2 . Please determine the amplification factor.

Exercise 3

The input voltage of an operational amplifier with $R_1 = 10$ k Ω and $R_2 = 100$ k Ω is 1.5 V. Please determine the output voltage.

Exercise 4

An inverting amplifier has an amplification factor of 250. The input resistor R_1 is 8.2 k Ω . Please determine the resistance of the feedback resistor R_2 .

Exercise 5

The output voltage of an op amp must not be below -5 V. Please determine the maximum input voltage if $R_1 = 2.7$ k Ω and $R_2 = 390$ k Ω .

Inverting Amplifiers

Please do the following exercises individually.

Example

An operational amplifier has an output range from -12 V to +12 V. You want to measure an alternating current with a voltage of 140 mV. The input resistor R_1 has 4.7 k Ω . Please determine the resistance of the feedback resistor R_2 .

Known quantities: $V_{rms} = 140 \text{ mV}$, $V_{out} = \pm 12 \text{ V}$, $R_1 = 4.7 \text{ k}\Omega$

$$V_{in} = \hat{V} = \sqrt{2} \cdot V_{rms} = 198 \text{ mV} \approx 0.2 \text{ V}$$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{12 \text{ V}}{0.2 \text{ V}} = 60$$

$$A_{CL} = \frac{R_2}{R_1} \rightarrow R_2 = A_{CL} \cdot R_1 = 60 \cdot 4.7 \text{ k}\Omega = 282 \text{ k}\Omega$$

Exercise 1

An operational amplifier increases an input voltage of 5 mV to -1 V. Please determine the amplification factor.

$$A_{CL} = 200$$

Exercise 2

An operational amplifier has a 15 k Ω input resistor R_1 and a 120 k Ω feedback resistor R_2 . Please determine the amplification factor.

$$A_{CL} = 8$$

Exercise 3

The input voltage of an operational amplifier with $R_1 = 10 \text{ k}\Omega$ and $R_2 = 100 \text{ k}\Omega$ is 1.5 V. Please determine the output voltage.

$$V_{out} = -15 \text{ V}$$

Exercise 4

An inverting amplifier has an amplification factor of 250. The input resistor R_1 is 8.2 k Ω . Please determine the resistance of the feedback resistor R_2 .

$$R_2 = 2 \text{ M}\Omega$$

Exercise 5

The output voltage of an op amp must not be below -5 V. Please determine the maximum input voltage if $R_1 = 2.7 \text{ k}\Omega$ and $R_2 = 390 \text{ k}\Omega$.

$$V_{in} = 35 \text{ mV}$$

Differential Amplifiers

Please do the following exercises individually.

Example

There are 5 mV on the non-inverting input of a differential amplifier and 1.8 mV on the inverting one. The input resistor has 10 k Ω . You need an output of about 4 V. Please determine the resistance of the other resistor. Choose a value from the E12-series: 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820. What is the actual output voltage?

Exercise 1

A differential amplifier has an input resistor of 47 k Ω and a feedback resistor of 560 k Ω . What is the close loop amplification of the circuit?

Exercise 2

You need an amplification of 350. Which resistors will you use?

Exercise 3

The input voltages of a differential amplifier with $R_1 = 470$ k Ω and $R_2 = 82$ k Ω are 1.2 V and 3.0 V. Please determine the two possible output voltages.

Exercise 4

The output voltage of a differential amplifier with an amplification factor of 100 is 7.5 V. The voltage at the inverting input is 50 mV. What is the voltage at the non-inverting input?

Exercise 5

The amplification factor of a differential amplifier is 50. The input resistor has 15 k Ω . What is the resistance of the other resistor?

Differential Amplifiers

Please do the following exercises individually.

Example

There are 5 mV on the non-inverting input of a differential amplifier and 1.8 mV on the inverting one. The input resistor has 10 kΩ. You need an output of about 4 V. Please determine the resistance of the other resistor. Choose a value from the E12-series: 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820. What is the actual output voltage?

Known quantities: $V_{in+} = 5 \text{ mV}$, $V_{in-} = 1.8 \text{ mV}$, $R_1 = 1 \text{ k}\Omega$, $V_{out} = 4 \text{ V}$

$$V_{out} = A_{CL}(V_{in+} - V_{in-}) \rightarrow A_{CL} = \frac{V_{out}}{V_{in+} - V_{in-}} = \frac{4 \text{ V}}{0.005 \text{ V} - 0.0018 \text{ V}} = 1250$$

$$A_{CL} = \frac{R_2}{R_1} \rightarrow R_2 = A_{CL} \cdot R_1 = 1250 \cdot 1 \text{ k}\Omega = 1250 \text{ k}\Omega = 1.25 \text{ M}\Omega \xrightarrow{E12} 1.2 \text{ M}\Omega \rightarrow A_{CL} = \frac{R_2}{R_1} = 1200$$

$$V_{out} = A_{CL}(V_{in+} - V_{in-}) = 1200 \cdot (0.005 \text{ V} - 0.0018 \text{ V}) = 3.84 \text{ V}$$

Exercise 1

A differential amplifier has an input resistor of 47 kΩ and a feedback resistor of 560 kΩ. What is the close loop amplification of the circuit?

$$A_{CL} = 12$$

Exercise 2

You need an amplification of 350. Which resistors will you use?

$$R_2 = 350 \text{ k}\Omega$$

Exercise 3

The input voltages of a differential amplifier with $R_1 = 470 \text{ k}\Omega$ and $R_2 = 82 \text{ k}\Omega$ are 1.2 V and 3.0 V. Please determine the two possible output voltages.

$$V_{out} = \pm 0.31 \text{ V}$$

Exercise 4

The output voltage of a differential amplifier with an amplification factor of 100 is 7.5 V. The voltage at the inverting input is 50 mV. What is the voltage at the non-inverting input?

$$V_{out} = 125 \text{ mV}$$

Exercise 5

The amplification factor of a differential amplifier is 50. The input resistor has 15 kΩ. What is the resistance of the other resistor?

$$R_2 = 750 \text{ k}\Omega$$

Schmitt Trigger

Please do the following exercises individually.

Example

The threshold voltage of a Schmitt Trigger is 0 V. The supply voltages are $\pm V_S$. Where are the switching levels of the circuit?

Exercise 1

The input resistor of a Schmitt trigger has 10 k Ω and the feedback resistor 82 k Ω . The threshold voltage is 0 V and the supply voltages are ± 5 V. At which input voltages flips the output?

Exercise 2

The input resistor of a Schmitt trigger has 8.2 k Ω and the feedback resistor 15 k Ω . The threshold voltage is 2.5 V and the supply voltages are 5 V and 0 V. Where are the switching points of the circuit?

Exercise 3

A voltage comparator has a supply voltage of 12 V. The reference input is connected with 5 V. What is the physical and logical output of the comparator if the voltages 0 V, 3 V, 4,9 V und 5,1 V are probed?

Schmitt Trigger

Please do the following exercises individually.

Example

The threshold voltage of a Schmitt Trigger is 0 V. The supply voltages are $\pm V_S$. Where are the switching levels of the circuit?

Known quantities: $V_{thr} = 0 \text{ V}$, $V_{S+} = +V_S$, $V_{S-} = -V_S$

$$V_{HT} = V_{thr} + \frac{R_1}{R_1 + R_2} (V_{S+} - V_{thr}) = \frac{R_1}{R_1 + R_2} \cdot V_S$$

$$V_{LT} = V_{thr} + \frac{R_1}{R_1 + R_2} (V_{S-} - V_{thr}) = \frac{R_1}{R_1 + R_2} \cdot -V_S = -\frac{R_1}{R_1 + R_2} \cdot V_S$$

Exercise 1

The input resistor of a Schmitt trigger has 10 k Ω and the feedback resistor 82 k Ω . The threshold voltage is 0 V and the supply voltages are $\pm 5 \text{ V}$. At which input voltages flips the output?

$V_{HT} = 0.54 \text{ V}$, $V_{LT} = -0.54 \text{ V}$

Exercise 2

The input resistor of a Schmitt trigger has 8.2 k Ω and the feedback resistor 15 k Ω . The threshold voltage is 2.5 V and the supply voltages are 5 V and 0 V. Where are the switching points of the circuit?

$V_{HT} = 2.88 \text{ V}$, $V_{LT} = 1.62 \text{ V}$

Exercise 3

A voltage comparator has a supply voltage of 12 V. The reference input is connected with 5 V. What is the physical and logical output of the comparator if the voltages 0 V, 3 V, 4,9 V und 5,1 V are probed?

V_{in}	0 V	3 V	4.9 V	5.1 V
V_{out}	0	0	0	1

Integrator

Please do the following exercises individually.

Example

The output voltage increases by 2 V per ms when an input voltage of -1 V is provided. Please determine the time constant of the circuit. Select an adequate resistor and capacitor from the E12-series: 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820. What is the actual time constant then?

Exercise 1

An integrator has a resistor with 56 k Ω and a capacitor with 12 nF. It is connected with a constant 1 V power source. What is the change in output voltage after 3 ms?

Exercise 2

An integrator which is constructed by means of an op amp has an input resistor of 27 k Ω . At the input, there is a constant voltage of 3 V. The output voltage drops 1.2 V per ms. Determine the capacity of the feedback capacitor.

Exercise 3

At the beginning input and output voltage of an integrator are 1V. 2 milliseconds later the output voltage has doubled. What is the time constant of the device?

Integrator

Please do the following exercises individually.

Example

The output voltage increases by 2 V per ms when an input voltage of -1 V is provided. Please determine the time constant of the circuit. Select an adequate resistor and capacitor from the E12-series: 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820. What is the actual time constant then?

Known quantities: $\Delta V_{out} = 2 \text{ V}$, $V_{in} = -1 \text{ V}$

Assumption: $R = 1 \text{ k}\Omega$

$$\Delta V_{out} = -\frac{1}{\tau} \cdot V_{in} \cdot \Delta t \rightarrow \tau = -\frac{V_{in} \cdot \Delta t}{\Delta V_{out}} = \frac{1 \text{ V} \cdot 0.001 \text{ s}}{2 \text{ V}} = 0.0005 \text{ s} = 0.5 \text{ ms}$$

$$\tau = R \cdot C \rightarrow C = \frac{\tau}{R} = \frac{0.0005 \text{ s}}{1000 \Omega} = 0.5 \cdot 10^{-6} \text{ F} = 0.5 \mu\text{F} \xrightarrow{E12} 0.47 \mu\text{F} \text{ or } 0.56 \mu\text{F}$$

$$\tau = R \cdot C = 1 \cdot 10^3 \Omega \cdot 0.47 \cdot 10^{-6} \text{ F} = 0.47 \cdot 10^{-3} \text{ s} = 0.47 \text{ ms} \text{ or } 0.56 \mu\text{F} \rightarrow 0.56 \text{ ms}$$

Exercise 1

An integrator has a resistor with 56 k Ω and a capacitor with 12 nF. It is connected with a constant 1 V power source. What is the change in output voltage after 3 ms?

$$\Delta V_{out} = 44.64 \text{ V}$$

Exercise 2

An integrator which is constructed by means of an op amp has an input resistor of 27 k Ω . At the input, there is a constant voltage of 3 V. The output voltage drops 1.2 V per ms. Determine the capacity of the feedback capacitor.

$$C = 92.6 \text{ nF}$$

Exercise 3

At the beginning input and output voltage of an integrator are 1V. 2 milliseconds later the output voltage has doubled. What is the time constant of the device?

$$T = 0.2 \text{ ms}$$

Differentiator

Please do the following exercises individually.

Example

The input voltage of a differentiator is constant 1.2 V for 5 ms. Then it drops to 0.5 V within 0.5 ms. Afterwards it remains constant again. The resistor of the differentiator has 12 k Ω , the capacitor 100 nF. Please determine the output voltage as a function of time.

Exercise 1

A differentiator has a resistor with 2.2 k Ω and a capacitor with 56 nF. What is the time constant of the differentiator?

Exercise 2

A differentiator has a 10 μ F capacitor. Its time constant is 2 ms. What is the resistance of the resistor?

Exercise 3

The input voltage of a differentiator is recorded. In the time range from 3 ms til 6 ms the voltage drops from 5 V to 1V. The differentiator is constructed with a 27 k Ω resistor and a 47 nF capacitor. Please determine the output voltage during this period.

Exercise 4

While the input voltage of a differentiator with $R = 220$ k Ω and 8.2 μ F drops from +6V to -1V, the has constantly 4 V. Please calculate the duration of the voltage drop.

Differentiator

Please do the following exercises individually.

Example

The input voltage of a differentiator is constant 1.2 V for 5 ms. Then it drops to 0.5 V within 0.5 ms. Afterwards it remains constant again. The resistor of the differentiator has 12 k Ω , the capacitor 100 nF. Please determine the output voltage as a function of time.

Facts: $V_{in} = 1.2 \text{ V}$ const for 5 ms, $\Delta V_{in} = -0.7$ for 0.5 ms, $V_{in} = 0.5 \text{ V}$ const then
 Known quantities: $\Delta V_{in} = -0.7$, $\Delta t = 0.5 \text{ ms}$, $R = 12 \text{ k}\Omega$, $C = 100 \text{ nF}$

$$V_{out} = -R \cdot C \cdot \frac{\Delta V_{in}}{\Delta t} = -12 \cdot 10^3 \Omega \cdot 100 \cdot 10^{-9} \text{ F} \cdot \frac{0.7 \text{ V}}{0.5 \cdot 10^{-3} \text{ s}} = 1.68 \text{ V}$$

$$V_{out}(t) = \begin{cases} 0 \text{ V}, & t < 5 \text{ ms} \\ 1.68 \text{ V}, & 5 \text{ ms} \leq t \leq 5.5 \text{ ms} \\ 0 \text{ V}, & t > 5.5 \text{ ms} \end{cases}$$

Exercise 1

A differentiator has a resistor with 2.2 k Ω and a capacitor with 56 nF. What is the time constant of the differentiator?

$$\tau = 123 \mu\text{s}$$

Exercise 2

A differentiator has a 10 μF capacitor. Its time constant is 2 ms. What is the resistance of the resistor?

$$R = 200 \Omega$$

Exercise 3

The input voltage of a differentiator is recorded. In the time range from 3 ms til 6 ms the voltage drops from 5 V to 1V. The differentiator is constructed with a 27 k Ω resistor and a 47 nF capacitor. Please determine the output voltage during this period.

$$V_{out} = 1.69 \text{ V}$$

Exercise 4

While the input voltage of a differentiator with $R = 220 \text{ k}\Omega$ and 8.2 μF drops from +6V to -1V, the has constantly 4 V. Please calculate the duration of the voltage drop.

$$\Delta t = 3.16 \text{ ms}$$