

Digital Circuits


Networks and Embedded Software

Module 3.2.3

by Wolfgang Neff


Digital Circuits (1)

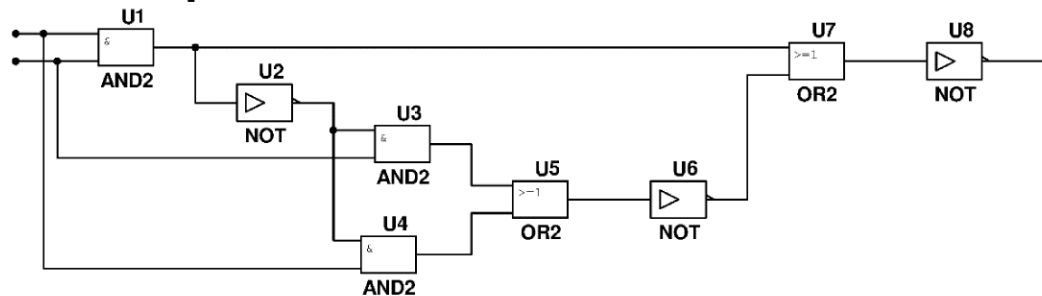- Based on Boolean algebra
 - Logical operators are represented by symbols
 - Logical values are represented voltages
 - Positive logic: 0 → Low voltage, 1 → High voltage
 - Negative logic: 0 → High voltage, 1 → Low voltage
- Graphical representation of truth functions




Graphic Symbols (1)

- Buffer

 


European Style
(IEC 60617-12)

 


American Style
(Mil-STD-806)

a	y=a
0	0
1	1

- Negation (NOT, \neg)

 


Inversion Circle

 

a	y= \neg a
0	1
1	0


Graphic Symbols (2)

- Disjunction (OR, \vee)

 

a	b	$y=a\vee b$
0	0	0
0	1	1
1	0	1
1	1	1


- Conjunction (AND, \wedge)

 

a	b	$y=a\wedge b$
0	0	0
0	1	0
1	0	0
1	1	1


Graphic Symbols (3)

- NOR (\downarrow)

 

a	b	$y=a\downarrow b$
0	0	1
0	1	0
1	0	0
1	1	0


- NAND ($|$)

 

a	b	$y=a b$
0	0	1
0	1	1
1	0	1
1	1	0

Graphic Symbols (4)


- XOR (\oplus)

 

a	b	$y=a\oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

- Threshold Gate
 
$$(a_0, a_1, \dots, a_n) \alpha \begin{cases} 1 & \text{if at least } m \ a_i = 1 \\ 0 & \text{else} \end{cases}$$




Graphic Symbols (5)

- Compound AND-Gate

$$- y = a_0 \wedge a_1 \wedge a_2 \dots = \bigwedge_{i=0}^n a_i$$

 
$$- (a_0, a_1, K) \alpha \begin{cases} 1 \text{ if each } a_i = 1 \\ 0 \text{ else} \end{cases}$$



- Compound OR-Gate

$$- y = a_0 \vee a_1 \vee a_2 \dots = \bigvee_{i=0}^n a_i$$


 
$$- (a_0, a_1, K) \alpha \begin{cases} 0 \text{ if each } a_i = 0 \\ 1 \text{ else} \end{cases}$$





Digital Circuits (2)

- Examples

– $y = a \wedge b$

  

– $y = \neg(a \wedge b) \vee c$

  

Digital Circuits (3)

- Examples (continued)

$$- y = (a \wedge \neg b) \vee \neg(c \wedge a) \vee a$$

