

Flip-flops


Networks and Embedded Software

Module 3.3.4 (optional)

by Wolfgang Neff

Latches (1)

 - Implementation of a SR latch
 - Based on two NOR gates with feedback




Latches (2)


- Truth table

a	b	y_1	y_2	y_1^+	y_2^+
0	0	0	0	1	1
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
0	1	1	1	0	0

instable



a	b	y_1	y_2	y_1^+	y_2^+
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0




Latches (3)


- Characteristics of a stable SR latch
 - $a=0, b=0$
stable only if $y_1 \neq y_2$ or $y_1 = \neg y_2$
 - $a=0, b=1$
always stable and $y_1 = 1$ (set)
 - $a=1, b=0$
always stable and $y_1 = 0$ (reset)
 - $a=1, b=1$
invalid since $y_1 = y_2$

Latches (4)

- Symbol, state table and state diagram

 


S	R	Q ⁺	Action
0	0	Q	Store
0	1	0	Reset
1	0	1	Set
1	1	X	Invalid

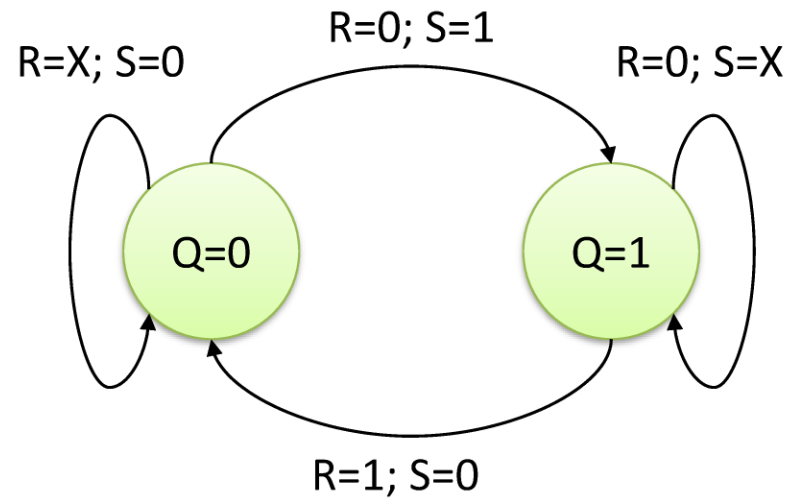


Latches (5)

 - Synchronous SR latch
 - $C=0$: R und S may change, Q is stable
 - $C=1$: R und S must be stable, Q may change



Latches (6)

 
- Symbol and state table of a sync SR latch



C	S	R	Q ⁺	Action
0	X	X	Q	Store
1	0	0	Q	Store
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	X	Invalid


Latches (7)

 - Time diagram of a synchronous SR latch
 - Active state: level 1




Flip-flop (1)

 - Input and output are decoupled
 - Edge triggered flip-flops
 - Master-slave flip-flop




Flip-flop (2)

- The JK flip-flop has no invalid state

 

J	K	Q ⁺	Action
0	0	Q	Store
0	1	0	Reset
1	0	1	Set
1	1	$\neg Q$	Toggle

- The D flip-flop is used to store data

 

D	Q ⁺	Action
0	0	Reset
1	1	Set