

Counters


Networks and Embedded Software

Module 3.4.2

by Wolfgang Neff


Counters (1)

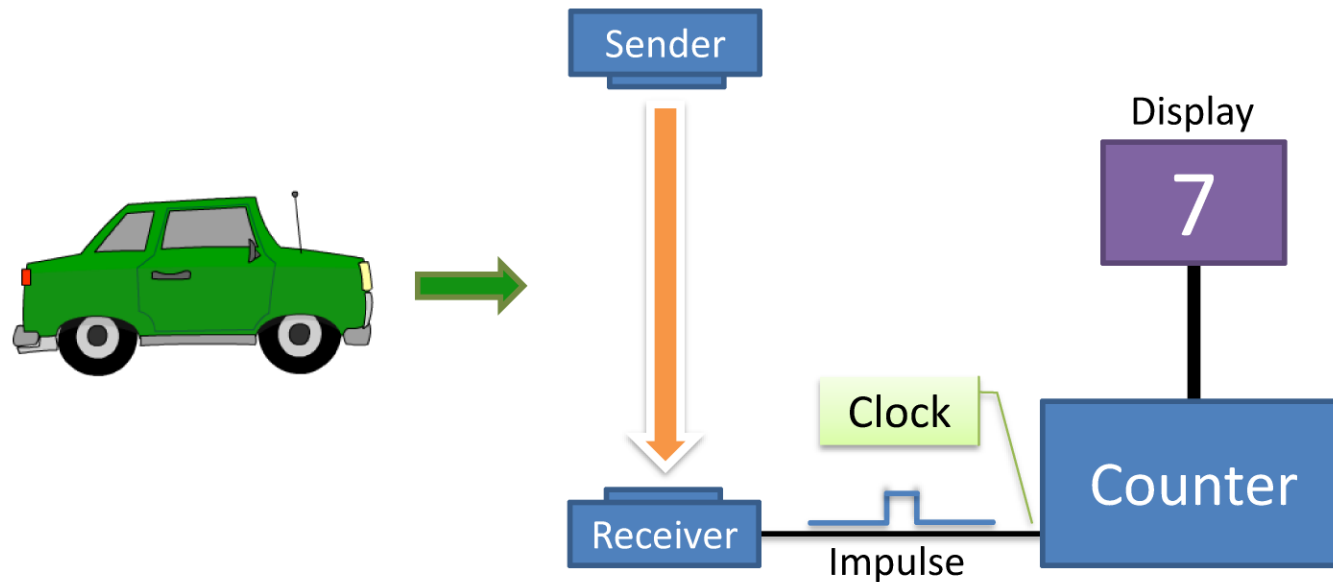- Count events
- Events are indicated by impulses



Counters (2)

 - Mod- N counter
 - Counter have a range
 - 0 ... $N-1$ (0 ... 5)
 - Counter overflow
 - $N-1 \rightarrow 0$ (0, 1, 2, 3, 4, 5, 0, 1, ...)
 - Modulo
 - Remainder of division
 - $5 \bmod 6 = 5$
 - $6 \bmod 6 = 0$
 - $7 \bmod 6 = 1$




Counters (3)

- Features
 - Enable
 - Enables or disables clock
 - Reset
 - Resets counter value
 - Up/down
 - Changes the counting direction
 - Countdown



Counters (4)

 
- Features [\(continued\)](#)
 - Overflow Indicator
 - Enables cascading [\(see BCD\)](#)
 - Preload
 - Sets a start value



Counter starts with provided start value. Reading is triggered by a load signal.


BCD (1)

- Binary Coded Decimal

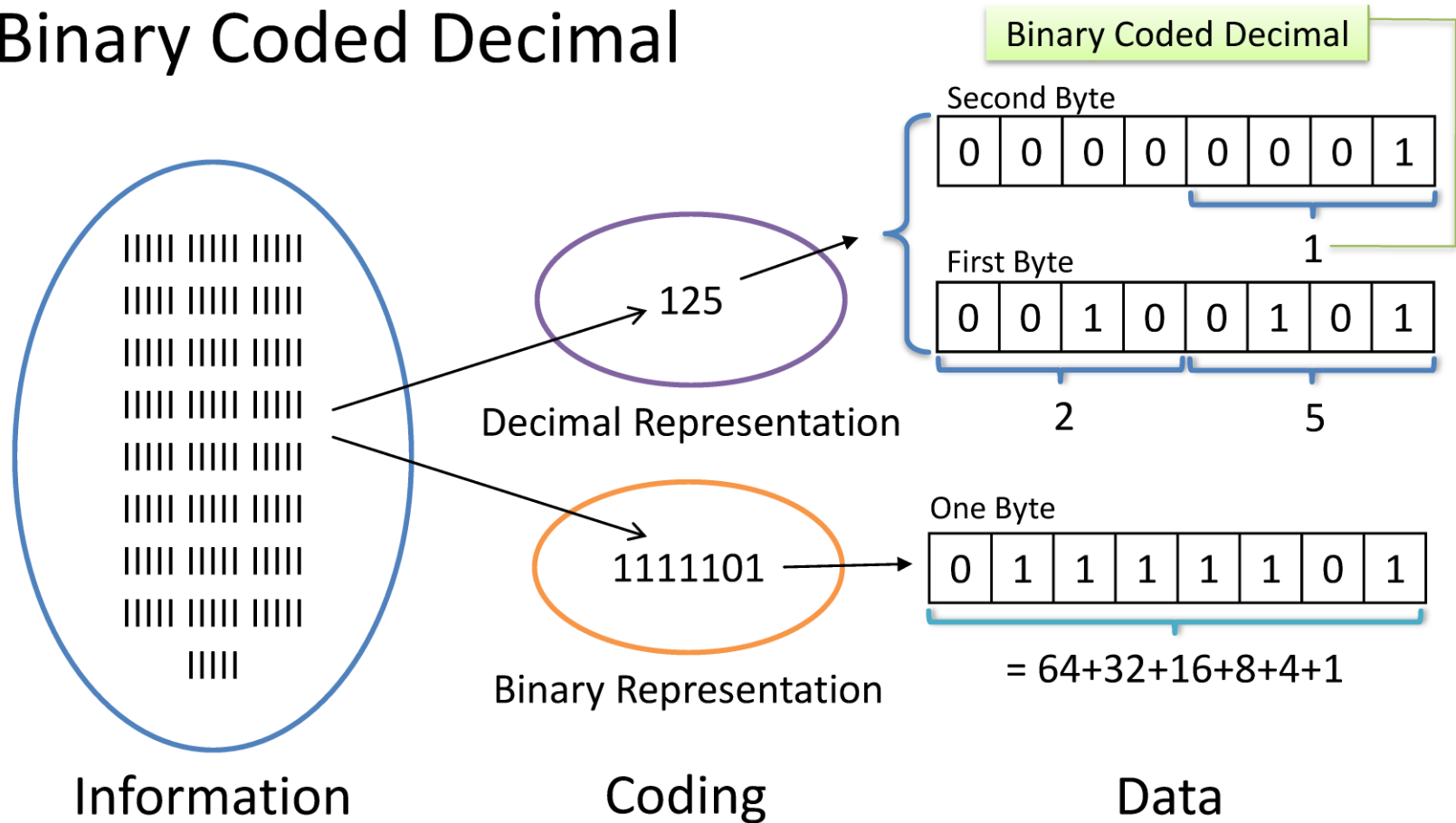


BCD (2)

 - BCD Counter (mod-10 counter)
- Position Cascading
 - Odometer (Mileage counter)



Counters (5)

- 4516 – Binary up/down counter

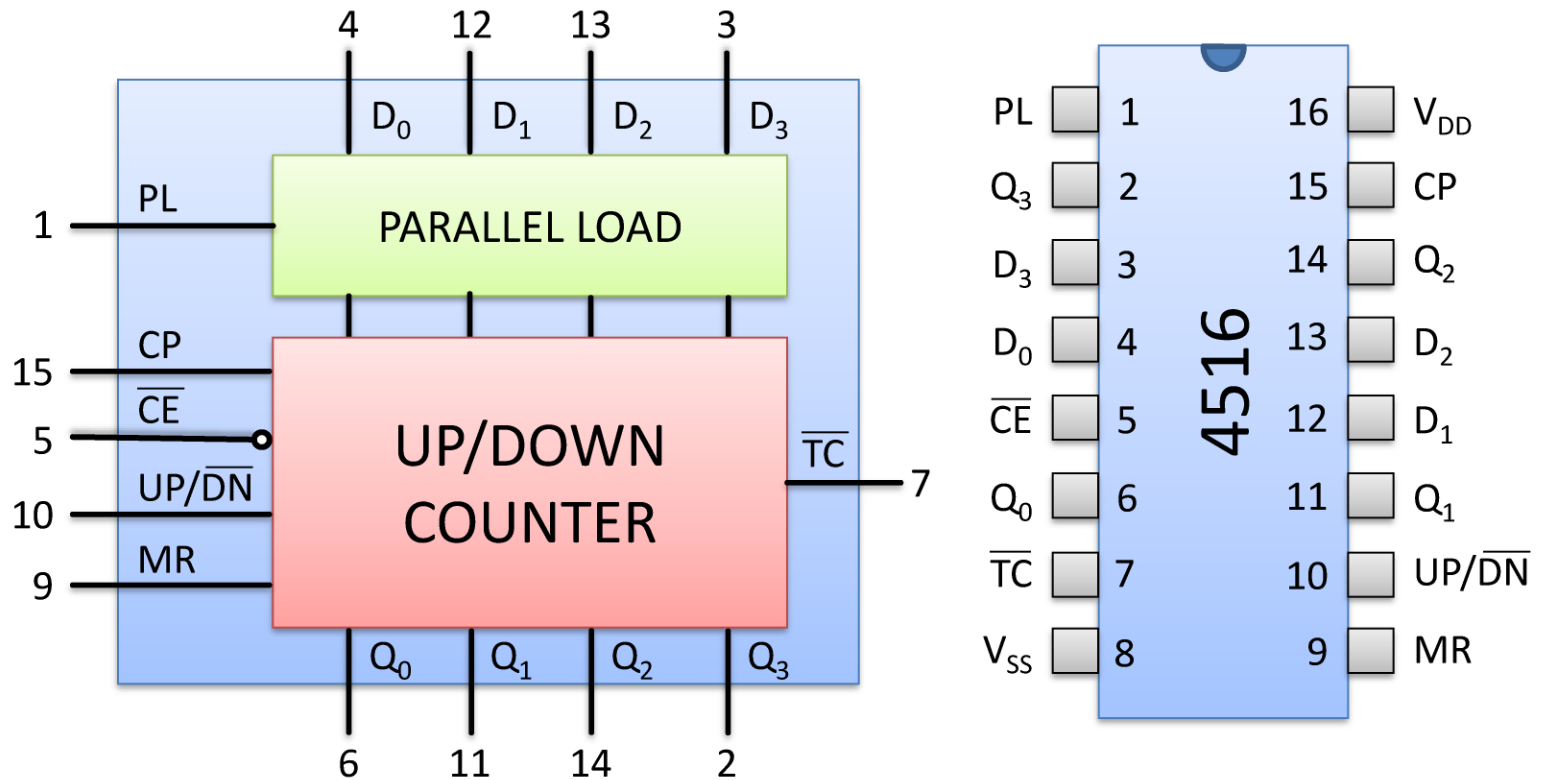

Counters (6)

- 4516 – Binary up/down counter (continued)

Symbol	Pin	Description
PL	1	parallel load input
D_0, D_1, D_2, D_3	4, 12, 13, 3	parallel input
\overline{CE}	5	count enable input
Q_0, Q_1, Q_2, Q_3	6, 11, 14, 2	parallel output
V_{SS}	8	ground
\overline{TC}	7	terminal count output
MR	9	master reset input
UP/ \overline{DN}	10	up/down count control input
CP	15	clock pulse input
V_{DD}	16	supply voltage